

## Lab Assignment 8

Given the following problems:

- (i) Let  $R = 1 \text{ k}\Omega$ ,  $C = 1 \text{ }\mu\text{F}$ , find
  - (a)  $v_C(t)$  for a series  $RC$  circuit with  $v_C(0^-)=0$  and voltage source  $V_s(0^+) = u(t)$  V.
  - (b)  $v_C(t)$  for a parallel  $RC$  circuit with  $v_C(0^-)=0$  and current source  $I_s(0^+) = u(t)$  A.
- (ii) Let  $R = 1 \text{ }\Omega$ ,  $L = 1 \text{ mH}$ , find
  - (c)  $i_L(t)$  for a series  $RL$  circuit with  $i_L(0^-)=0$  and voltage source  $V_s(0^+) = u(t)$ .
  - (d)  $i_L(t)$  for a parallel  $RL$  circuit with  $i_L(0^-)=0$  and current source  $I_s(0^+) = u(t)$ .
- (iii) Repeat problem (i) with source changed to triangular pulse of height 1 and width 1 ms.
- (iv) Repeat problem (ii) with source changed to triangular pulse of height 1 and width 1 ms.

Write codes using the following methods to solve them:

- (i) Euler      (ii) mid-point    (iii) RK2      (iv) RK4

### **NOTE:**

1.  $u(t-a)$  denotes the unit step function given by:

$$u(t-a) = \begin{cases} 1 & t \geq a \\ 0 & t < a \end{cases}$$

2. Continue computations until systems reach “steady” states.