

## Lab Assignment 9

Given the following problems:

(i) Let  $R = 2 \text{ k}\Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = .1 \text{ }\mu\text{F}$ , find

$v_C(t)$  for a series  $RLC$  circuit with  $v_C(0^-)=0$ ,  $i_C(0^-) = 0$  and voltage source  $V_s(0^+) = u(t)$

Then repeat the problem with  $C$  changed to  $1 \text{ }\mu\text{F}$  and  $10 \text{ nF}$ , respectively.

(ii) Repeat problem (i) with source changed to triangular pulse of height 1 and width 4 ms.

(iii) Let  $R = 0.8 \text{ k}\Omega$ ,  $L = 0.1 \text{ H}$ ,  $C = .1 \text{ }\mu\text{F}$ , find

$i_L(t)$  for a parallel  $RLC$  circuit with  $v_L(0^-)=0$ ,  $i_L(0^-) = 0$  and current source  $I_s(0^+) = u(t)$ .

Then repeat the problem with  $C$  changed to  $1 \text{ }\mu\text{F}$  and  $10 \text{ nF}$ , respectively.

(iv) Repeat problem (iii) with source changed to triangular pulse of height 1 and width 4 ms.

Write codes using the following methods to solve them:

(i) Euler            (ii) RK2