
 


CMOS Technology

- NMOS
- PMOS
- CMOS
- Logic Gates using CMOS
- Layout


NMOS Structure

 - Gate (Metal -> Polysilicon)
- Insulator (Oxide -> Silicon dioxide)
- Substrate (Semiconductor : Si, SiGe)




Schematic Icon



NMOS Operations

 

 
(a) When $V_{GS} = 0\text{ V}$, the transistor is off



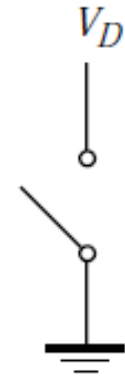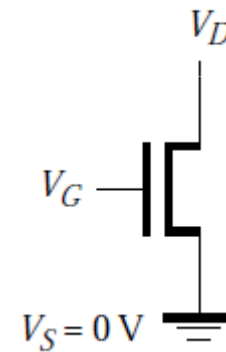(b) When $V_{GS} = 5\text{ V}$, the transistor is on





Open switch
when $V_G = 0\text{ V}$

 



Closed switch
when $V_G = V_{DD}$

[Adapted from Fundamentals of Digital Logic by Brown & Vranesic]


PMOS structure & operations

  

Schematic Icon

  


Open switch
when $V_G = V_{DD}$

 


Closed switch
when $V_G = 0\text{ V}$

Switch-Level View of NMOS & PMOS

Symbols

 


(a)

 


(d)

Switch Characteristics

 

(b)

 

(c)





(f)




[Adapted from Principles of CMOS VLSI Design by Weste & Eshraghian]

Decorative graphic on the right side of the page featuring overlapping circles and a blue dot on a gold background.

- 

  


CMOS Logic Gates

 


x	T_1	T_2	f
0	on	off	1
1	off	on	0

Inverter

 

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

NAND

 


x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

NOR


Required Conditions

- **NAND:**
 - PUN : consider $f = 1$ (i.e., $f = (x_1 x_2)'$) when $x_1 = 0$ or $x_2 = 0$, thus inputs x_1, x_2 “in parallel”
 - PDN : consider $f = 0$ (i.e., $f' = x_1 x_2$) when $x_1 = 1$ and $x_2 = 1$, thus x_1, x_2 “in series”
- **NOR: the opposite to NAND**
 - PUN : consider $f = 1$ (i.e., $f = (x_1 + x_2)'$) when both $x_1 = 0$ and $x_2 = 0$, thus inputs x_1, x_2 “in series”
 - PDN : consider $f = 0$ (i.e., $f' = x_1 + x_2$) when $x_1 = 1$ or $x_2 = 1$, thus x_1, x_2 “in parallel”
- Note that AND $\rightarrow$ “series”, OR $\rightarrow$ “parallel”.

CMOS Circuits

 


AND

 


$$f = \bar{x}_1 + \bar{x}_2 \bar{x}_3$$

Stick Diagram & Layout

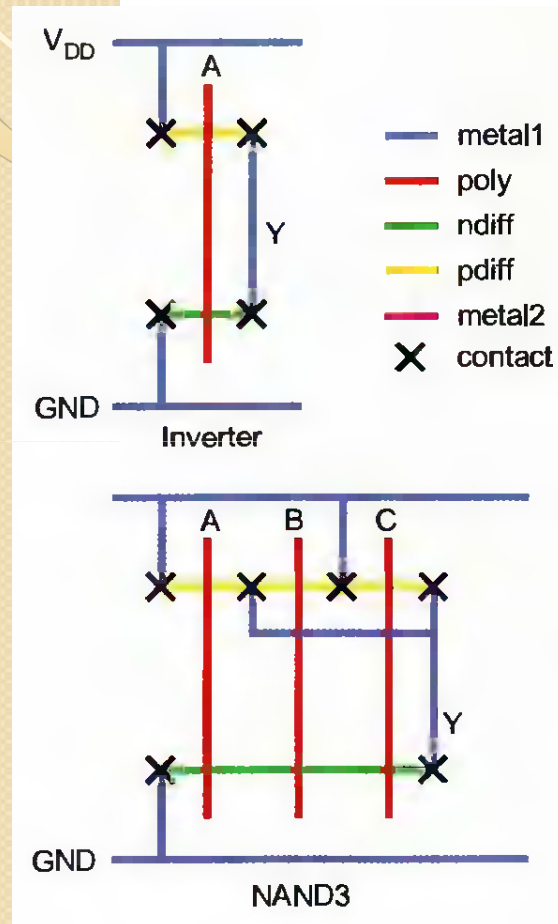


Stick Diagram

 



Layout

CMOS Inverter Layout

 

[Adapted from <http://infopad.eecs.berkeley.edu/~icdesign/>. Copyright 1996 UCB]

4-Input NAND Gate

  

[Adapted from <http://infopad.eecs.berkeley.edu/~icdesign/>. Copyright 1996 UCB]