



Combinational Circuit Design

- Part I: Design Procedure and Examples
- Part II : Arithmetic Circuits
- Part III : Multiplexer, Decoder, Encoder, Hamming Code

Combinational Circuits



A combinational circuit has:

- n Boolean inputs (1 or more),
- m Boolean outputs (1 or more)
- logic gates mapping the inputs to the outputs

Design Procedure

1. Specification

- ❖ Write a complete specification for the circuit
- ❖ Specify/Label input and output

2. Formulation

- ❖ Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification
- ❖ Apply hierarchical design if appropriate

3. Optimization

- ❖ Apply 2-level and multiple-level optimization (Boolean Algebra, K-Map, software)
- ❖ Draw a logic diagram for the resulting circuit using necessary logic gates.

Design Procedure (Cont.)

4. Technology Mapping

- Map the logic diagram to the implementation technology selected (e.g. map into NANDs)

5. Verification

- Verify the correctness of the final design manually or using a simulation tool

Practical Considerations:

- Cost of gates (Number)
- Maximum allowed delay
- Fan-in/Fan-out (# of Input ports/Output ports provided by devices)

Example 1

- **Question:** Design a circuit that has a 3-bit binary input and a single output (f) specified as follows:
 - $F = 0$, when the input is less than $(5)_{10}$
 - $F = 1$, otherwise
- **Solution:**
- Step 1 (Specification):
- Label the inputs (3 bits) as X, Y, Z
 - X is the most significant bit, Z is the least significant bit
- The output (1 bit) is F:
 - $F = 1 \rightarrow (101)_2, (110)_2, (111)_2$
 - $F = 0 \rightarrow$ other inputs

Example 1 (cont.)

Step 2 (Formulation)

Obtain Truth table

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Boolean Expression:
 $F = XY'Z + XYZ' + XYZ$

Step 3 (Optimization)

$$\begin{aligned} F &= XY'Z + XYZ' + XYZ \\ &= XY'Z + XYZ' + XYZ + XZ + XY \\ &= XZ + XY \end{aligned}$$

(Use consensus theorem)

Circuit Diagram

 

Example 2

- **Question (BCD to Excess-3 Code Converter)**
- Code converters convert from one code to another (BCD to Excess-3 in this example)
- The inputs are defined by the code that is to be converted (BCD in this example)
- The outputs are defined by the converted code (Excess-3 in this example)
- Excess-3 code is a decimal digit plus three converted into binary, i.e., 0 is 0011, 1 is 0100, etc.

Example 2 (cont.)

Step 1 (Specification)

- 4-bit BCD input (A,B,C,D)
- 4-bit E-3 output (W,X,Y,Z)

Step 2 (Formulation)

Obtain Truth table

	BCD Input				Excess 3 Output			
Decimal	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0
10-15	All other inputs				X	X	X	8X

Example 2 (cont.)

Step 3 (Optimization)

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$W = A + BC + BD$$

AB \ CD	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X


$$X = B'C + BC'D' + B'D'$$

AB \ CD	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

$$Y = CD + C'D'$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X


$$Z = D'$$

 

source: Mano's book

Example 3

Question (BCD-to-Seven-Segment Decoder)

 



src: Mano's book

- A seven-segment display is digital readout found in electronic devices like clocks, TVs, etc.
 - Made of seven light-emitting diodes (LED) segments; each segment is controlled separately.
- **A BCD-to-Seven-Segment decoder** is a combinational circuit
 - Accepts a decimal digit in BCD (input)
 - Generates appropriate outputs for the segments to display the input decimal digit (output)

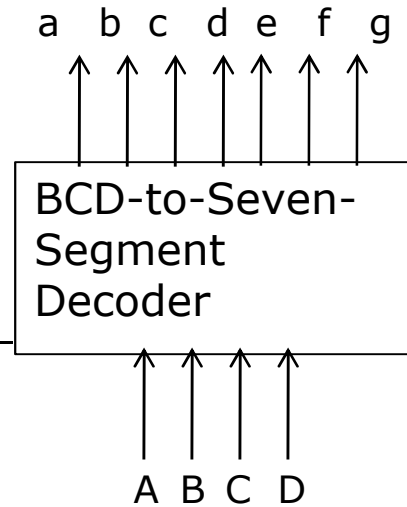 Example 3 (cont.)

Step 1 (Specification):

- 4 inputs (A, B, C, D)
- 7 outputs (a, b, c, d, e, f, g)



Step 2 (Formulation)

Decimal	BCD Input				7 Segment Decoder						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
10-15	All Other Inputs				0	0	0	0	0	0	0

Invalid
BCD
codes
=
No Light

Example 3 (cont.)

Step 3 (Optimization)

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	0	0	0
10	1	1	0	0

a

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	0	1	0
11	0	0	0	0
10	1	1	0	0

b

AB \ CD	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	0	0	0	0
10	1	1	0	0

c

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	0	0	0	0
10	1	1	0	0

d

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	0	0	0	0
10	1	0	0	0

e

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	0	0	0	0
10	1	1	0	0

f

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	0	1
11	0	0	0	0
10	1	1	0	0

g

Example 3 (cont.)

Step 3 (Optimization) (cont.)

$$a = A'C + A'BD + AB'C' + B'C'D'$$

$$b = A'B' + A'C'D' + A'CD + B'C'$$

$$c = A'B + B'C' + A'C' + A'D$$

$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

$$e = A'CD' + B'C'D'$$

$$f = A'BC' + A'C'D' + A'BD' + AB'C'$$

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$

Exercise: Draw the circuit



Part II Arithmetic Circuits

- Adder
- Subtractor
- Carry Look Ahead Adder
- BCD Adder
- Multiplier

Half Adder

Design a half-Adder for 1-bit numbers



- 1. **Specification:**
Optimization/Circuit

2 inputs (X,Y)
2 outputs (C,S)

- 2. **Formulation:**

x	y	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- 3. **Logic Diagram**

  

Graphical Symbol

Full Adder

A combinational circuit that adds 3 input bits (x_i, y_i, c_{in}) to generate a Sum bit and a Carry-out bit

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 s_i &= (\bar{x}_i y_i + x_i \bar{y}_i) \bar{c}_i + (\bar{x}_i \bar{y}_i + x_i y_i) c_i \\
 &= (x_i \oplus y_i) \bar{c}_i + \overline{(x_i \oplus y_i)} c_i \\
 &= (x_i \oplus y_i) \oplus c_i
 \end{aligned}$$


$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$


$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


Full Adder Logic Diagram

 

Full Adder = 2 Half Adders

 

Block diagram

 


Circuit

Exercise : Verify this full-adder implementation.

Bigger Adders

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? 9 inputs
 - Outputs ? 5 outputs
 - What is the size of the truth table?
512 rows!
 - How many functions to optimize? 5 functions

Ripple Carry Adder

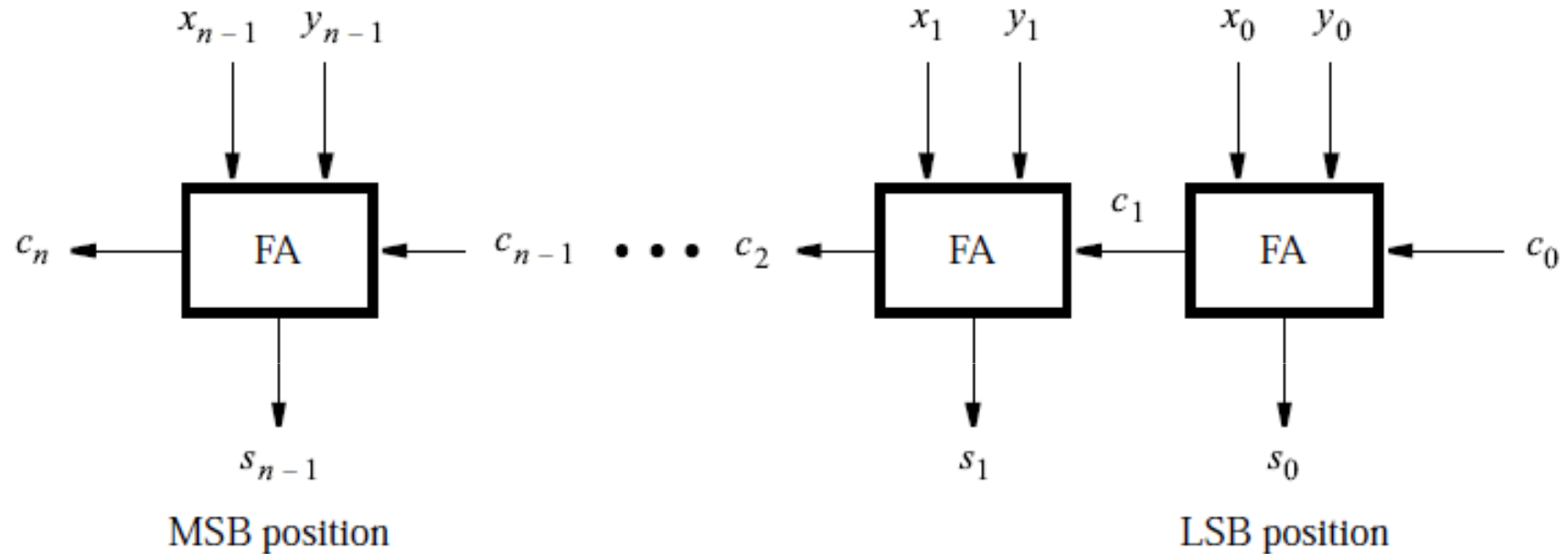


Note:

- Carry signal "ripples" through the full-adder stages.
- Delay can be an issue.

Subtraction (2's Complement)

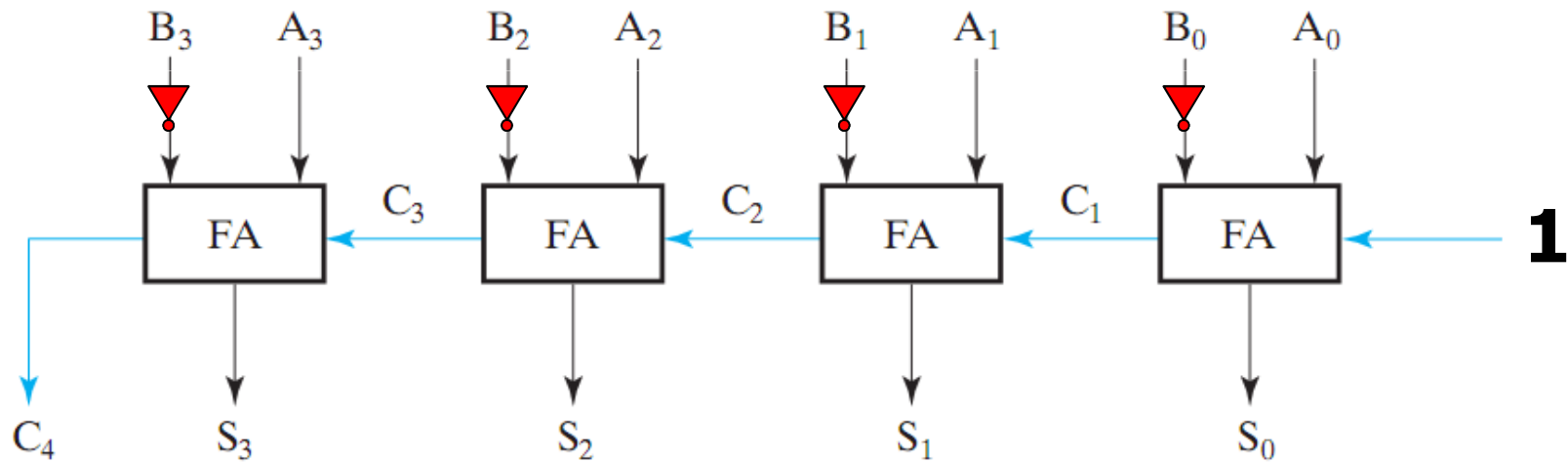
- How to build a subtractor using 2's complement?



Src: Mano's Book

$$S = A + (-B)$$


Adder/Subtractor

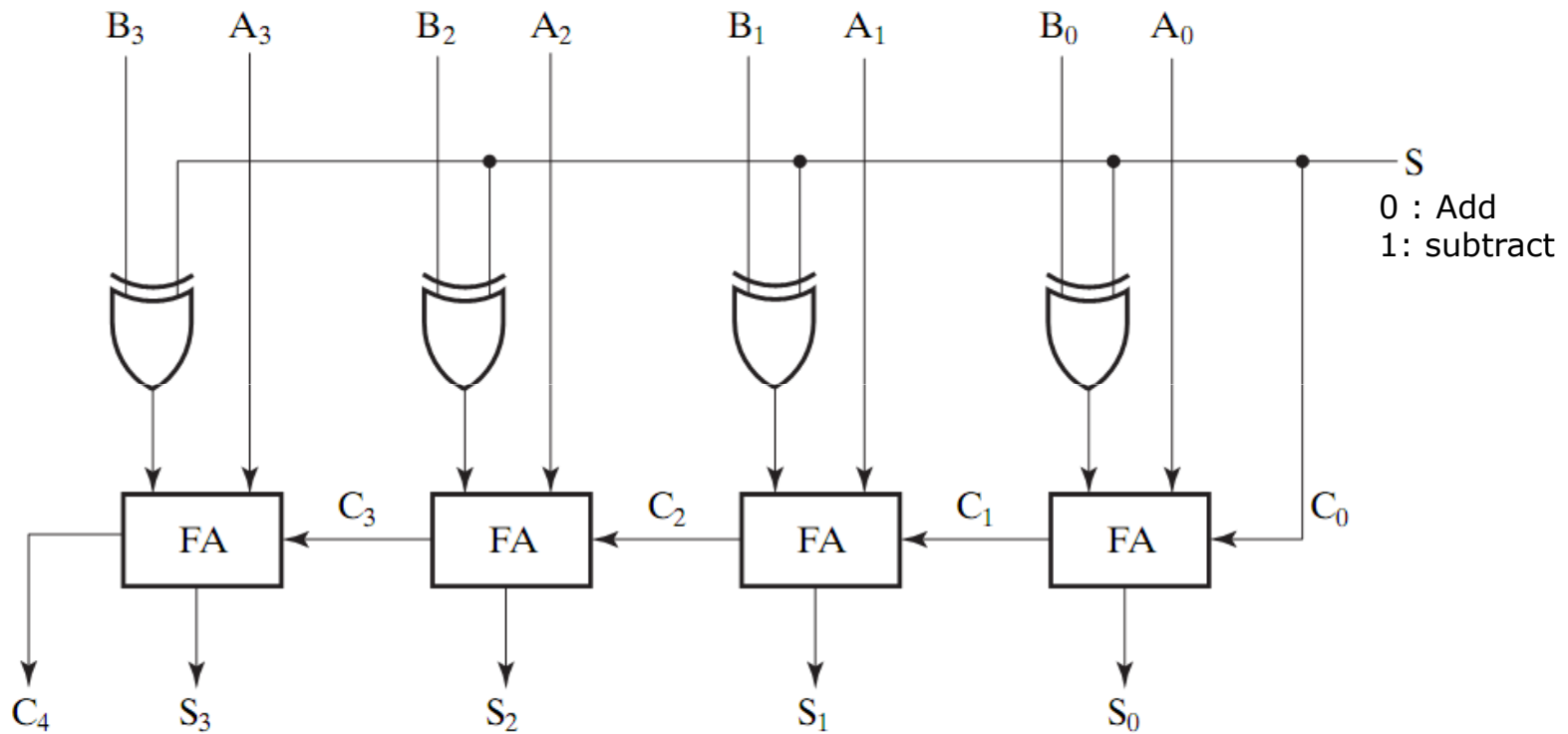

Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!

Full-Adder (Review)

 

$$s_i = x_i \oplus y_i \oplus c_i; c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Carry-Lookahead Adder (CLA)

Define $g_i = x_i y_i$; $p_i = x_i + y_i$

Then $c_{i+1} = g_i + p_i c_i$

- g_i is called “*generate*” function and p_i is called “*propagate*” function.
- Rewriting c_{i+1} in terms of $i-1$ terms yields

$$\begin{aligned}c_{i+1} &= g_i + p_i (g_{i-1} + p_{i-1} c_{i-1}) \\ &= g_i + p_i g_{i-1} + p_i p_{i-1} c_{i-1}\end{aligned}$$


CLA (cont.)

- Repeating until 0 term yields

$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \cdots + p_i p_{i-1} \cdots p_2 p_1 g_0 \\ + p_i p_{i-1} \cdots p_2 p_1 p_0 c_0$$

- c_{i+1} can be implemented in 2-level AND-OR circuits.
- A Carry-Lookahead Adder is based on this expression.

Ripple-carry Adder Delay

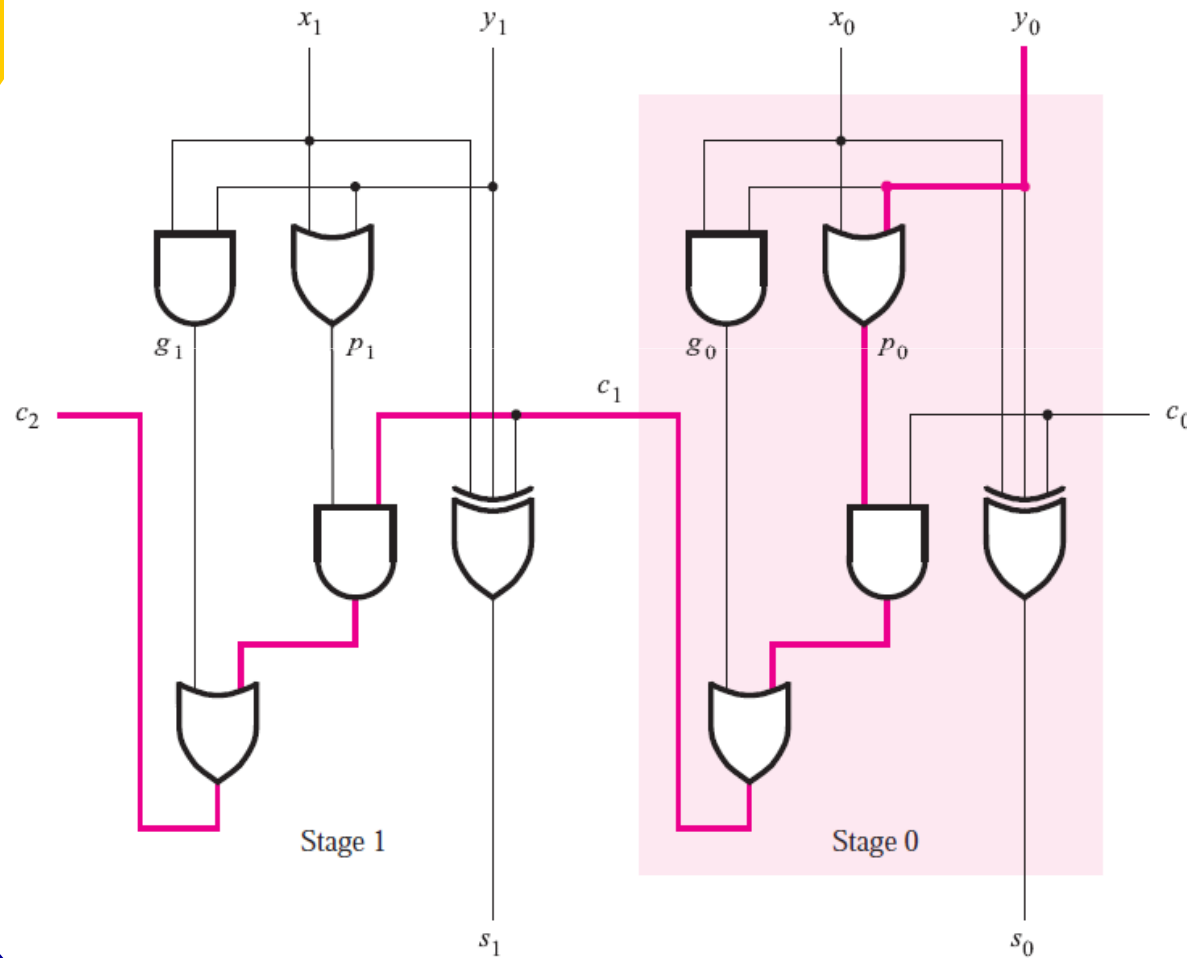


Only First 2
stages shown

LSB:
 $(x_0, y_0) = (0, 1)$

Delay: 5 gates

For n stages:
Delay: $2n+1$ gates

CLA Delay

 

Only First 2 stages shown

LSB:

$$(x_0, y_0) = (0, 1)$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$$


Delay: 3 gates

For n stages:

Delay: 3 gates

CLA Implementation

 - Total delay : 4 gates (1 for all g_i, p_i , 2 for all carry, 1 for the final XOR to compute all s_i)
- Becomes very complex when n large.
- Hierarchical CLA with ripple-carry



CLA : A better implementation

Consider c_8 out of block 0:

$$c_8 = g_7 + p_7g_6 + p_7p_6g_5 + \cdots + p_7p_6 \cdots p_2p_1g_0 \\ + p_7p_6 \cdots p_2p_1p_0c_0$$

Recall that $c_1 = g_0 + p_0c_0$

If define $P_0 = p_7p_6p_5p_4p_3p_2p_1p_0$

$$G_0 = g_7 + p_7g_6 + p_7p_6g_5 + \cdots + p_7p_6 \cdots p_2p_1g_0$$


Then can write $c_8 = G_0 + P_0c_0$

Likewise $c_{16} = G_1 + P_1G_0 + P_1P_0c_0$

$$c_{16} = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0c_0$$

$$c_{32} = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0c_0$$

CLA : A better implementation

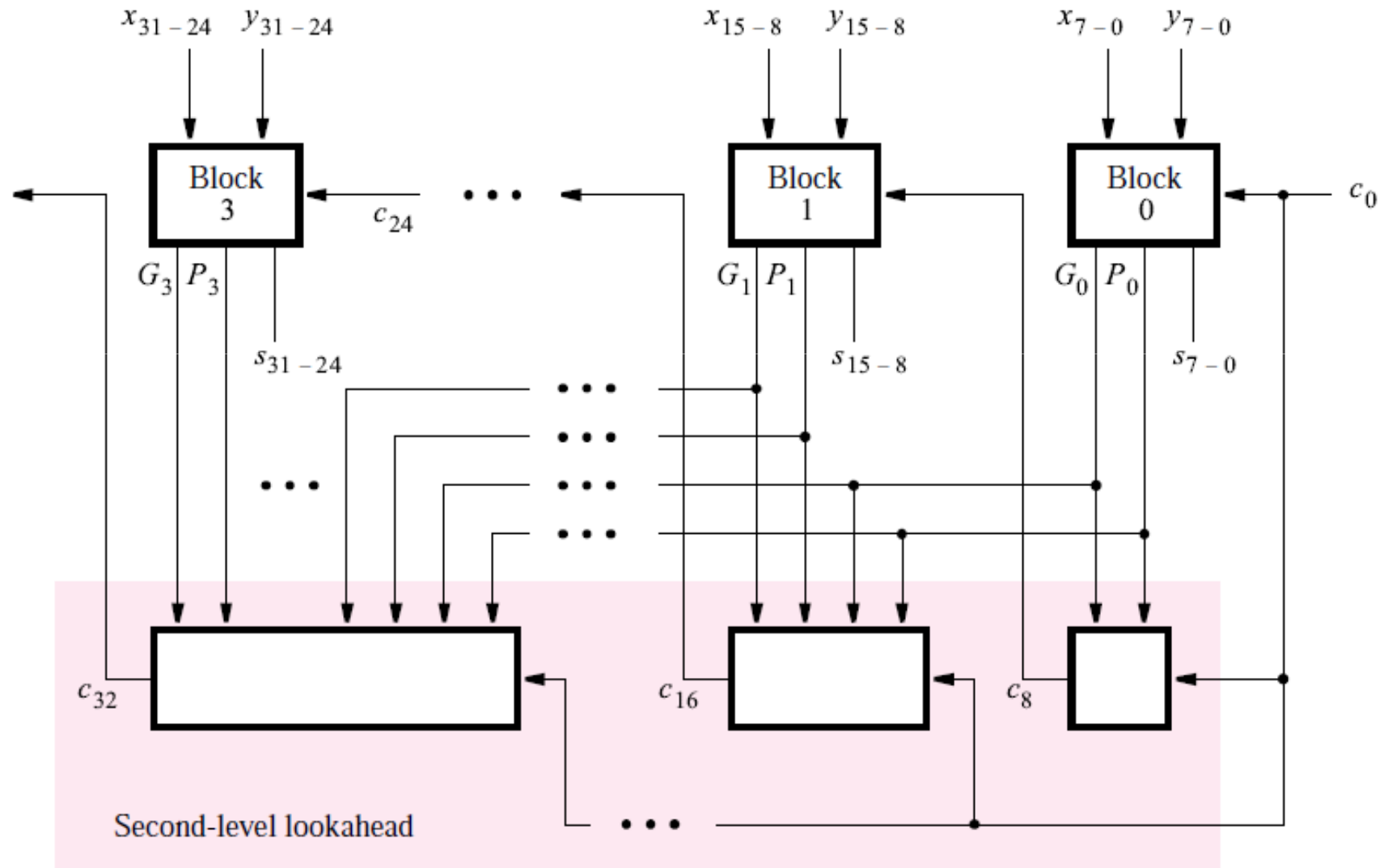

BCD Addition

$$Z = X + Y$$


If $Z \leq 9$, then $S = Z$ and carry-out = 0

if $Z > 9$, then $S = Z + 6$ and carry-out = 1


Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

X	0 1 1 1	7	X	1 0 0 0	8
+ Y	+ 0 1 0 1	+ 5	+ Y	+ 1 0 0 1	+ 9
Z	1 1 0 0	12	Z	1 0 0 0 1	17
	+ 0 1 1 0			+ 0 1 1 0	
carry →	1 0 0 1 0		carry →	1 0 1 1 1	
	⏟			⏟	
	S = 2			S = 7	

BCD Adder

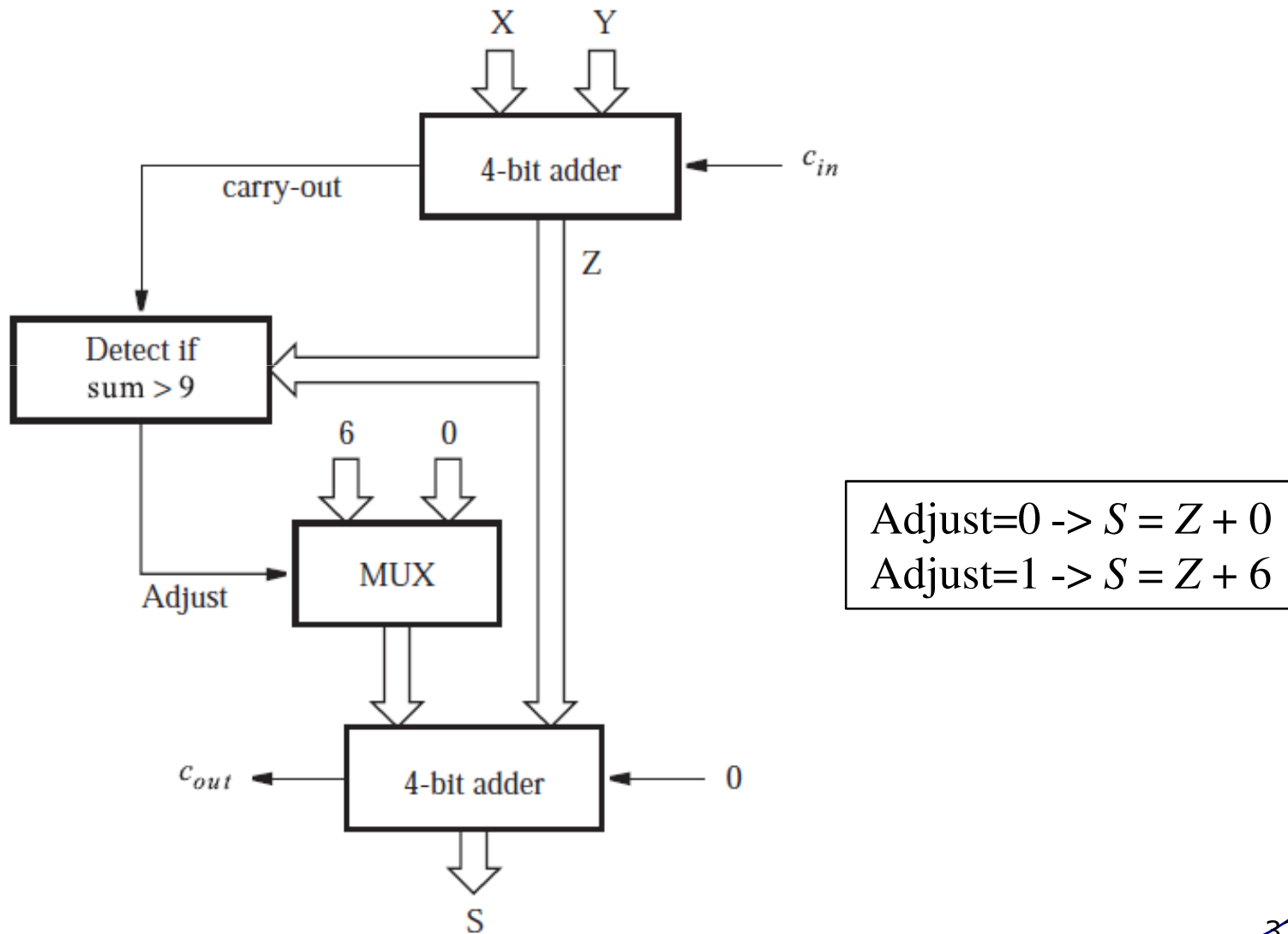

4-bit Comparator

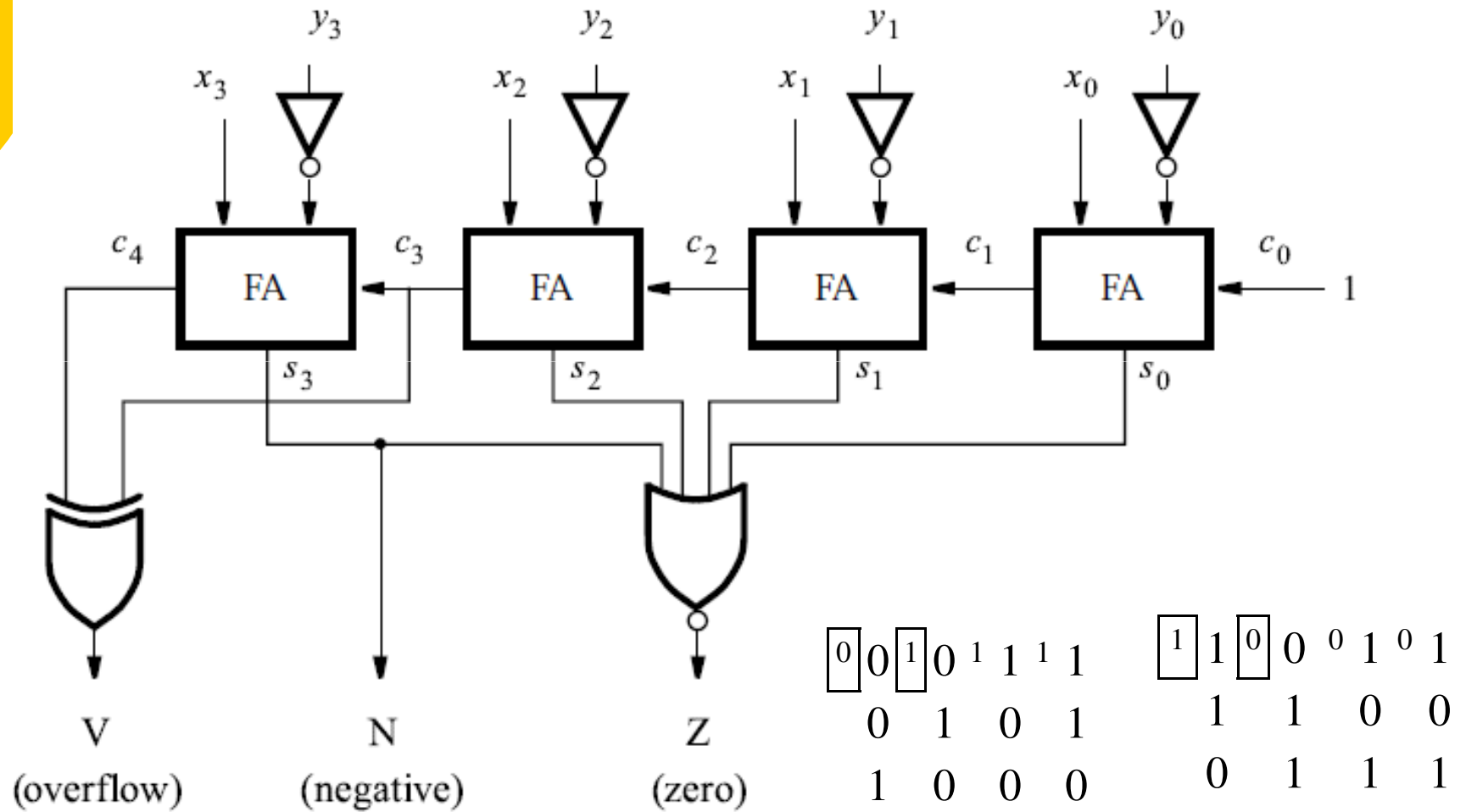

$3 - (-5) = -8$


$-5 - 4 = 7$

4-bit Comparator

- $X < Y$
 - Same sign: No overflow ($V=0$) and $N=1$
 - Different sign: $V=0 \ \&\& \ N=1$, OR $V=1$ (overflow) $\ \&\& \ N=0$ (positive)
 - Thus, condition is $N \oplus V = 1$.
- $X = Y \rightarrow Z = 1$
- $X > Y$
 - Same sign: No overflow ($V=0$) and $N=0$
 - Different sign: $V=0 \ \&\& \ N=0$, OR $V=1$ (overflow) $\ \&\& \ N=1$ (negative)
 - Thus, condition is $N \oplus V = 0$, i.e., the complement of $N \oplus V$, $(N \oplus V)'$.

2-to-1 Multiplexer (MUX)

 
Multiplexer has multiple inputs and one output; it passes the signal on one input to the output.




Symbol

s	f
0	w_0
1	w_1

Truth Table

 


SOP circuit

 


Circuit with transmission gates

4-to-1 Multiplexer

 
$$f = s_1' s_0' w_0 + s_1' s_0 w_1 + s_1 s_0' w_2 + s_1 s_0 w_3$$




s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

 

4-to-1 Multiplexer

 



4-to-1 mux using
2-to-1 mux

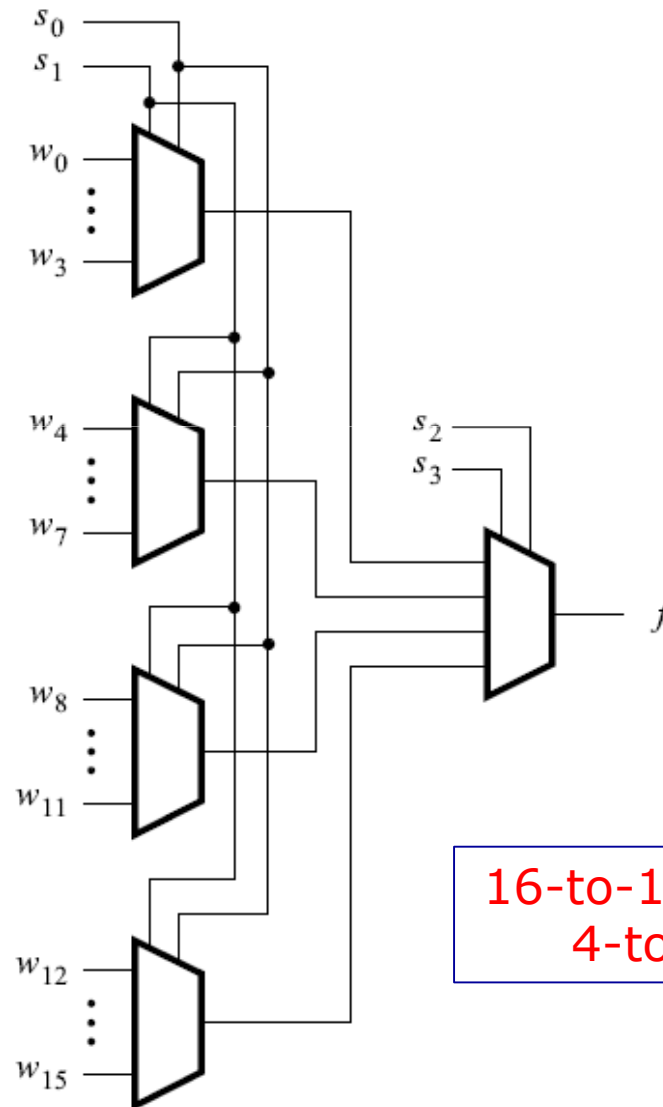

16-to-1 mux using
4-to-1 mux

2×2 crossbar switch

  
- 2 inputs, 2 outputs
- $s = 0$ -> connect $x_1 \rightarrow y_1$, $x_2 \rightarrow y_2$
- $s = 1$ -> connect $x_1 \rightarrow y_2$, $x_2 \rightarrow y_1$




Synthesis of Logic Functions

$$f = w_1 \oplus w_2$$

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

w_1	w_2	f		w_1	f
0	0	0	}	0	w_2
0	1	1		1	\bar{w}_2
1	0	1	}		
1	1	0			

 


3-input XOR

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$w_2 \oplus w_3$

$\overline{w_2 \oplus w_3}$

 

Using 2-to-1 MUX


w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

w_3

$\overline{w_3}$

$\overline{w_3}$

w_3

 


Using 4-to-1 MUX

3-input Majority Function

- Get 3 inputs and output 1 if # of 1's greater than # of 0's.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	w_2	f
0	0	0
0	1	w_3
1	0	w_3
1	1	1

 

Shannon's Expansion

- Shannon's Expansion Theorem

$$\begin{aligned} f(w_1, w_2, \dots, w_n) &= w_1' f(0, w_2, \dots, w_n) + w_1 f(1, w_2, \dots, w_n) \\ &= w_1' f_{w_1'} + w_1 f_{w_1} \quad \boxed{f_{w_1'}, f_{w_1} : \text{cofactors}} \end{aligned}$$

- Example : 3-input majority function

$$f = w_1' w_2 w_3 + w_1 w_2' w_3 + w_1 w_2 w_3' + w_1 w_2 w_3 = w_1 w_2 + w_2 w_3 + w_1 w_3$$

Can be rewritten as


$$f = w_1 w_2 + w_2 w_3 + w_1 w_3 = w_1' (w_2 w_3) + w_1 (w_2 + w_3)$$

Shannon's Expansion

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

Using
2-to-1 MUX

 

- 3-input XOR

$$f = w_1 \oplus w_2 \oplus w_3 = w_1'(w_2 \oplus w_3) + w_1(w_2 \oplus w_3)'$$

Shannon's Expansion

- In general : expand by w_i

$$\begin{aligned}f(w_1, w_2, \dots, w_n) &= w_i' f(w_1, w_2, \dots, 0, \dots, w_n) + w_i f(w_1, w_2, \dots, 1, \dots, w_n) \\ &= w_i' f_{w_i'} + w_i f_{w_i}\end{aligned}$$

- 2-variable expansion:

$$\begin{aligned}f(w_1, w_2, \dots, w_n) &= w_1' w_2' f(0, 0, w_3, \dots, w_n) + w_1' w_2 f(0, 1, w_3, \dots, w_n) \\ &\quad + w_1 w_2' f(1, 0, w_3, \dots, w_n) + w_1 w_2 f(1, 1, w_3, \dots, w_n)\end{aligned}$$


which can be implemented by a 4-to-1 MUX.

Example 1


$$f = w_1'w_3' + w_1w_2 + w_1w_3$$

$$= w_1'w_3' + w_1(w_2 + w_3)$$
 
$$= w_1'w_2'w_3' + w_1'w_2w_3' + w_1w_2'w_3 + w_1w_2(1)$$



Using
2-to-1 MUX

 


Using
4-to-1 MUX

3-input majority function

$$f = w_1w_2 + w_2w_3 + w_1w_3 = w_1'(w_2w_3) + w_1(w_2 + w_3)$$


Let $g = w_2w_3$, $h = w_2 + w_3$, then
 
$$g = w_2'(0) + w_2w_3; h = w_2'w_3 + w_2(1)$$




Decoder

- Main function: decode "encoded" data.

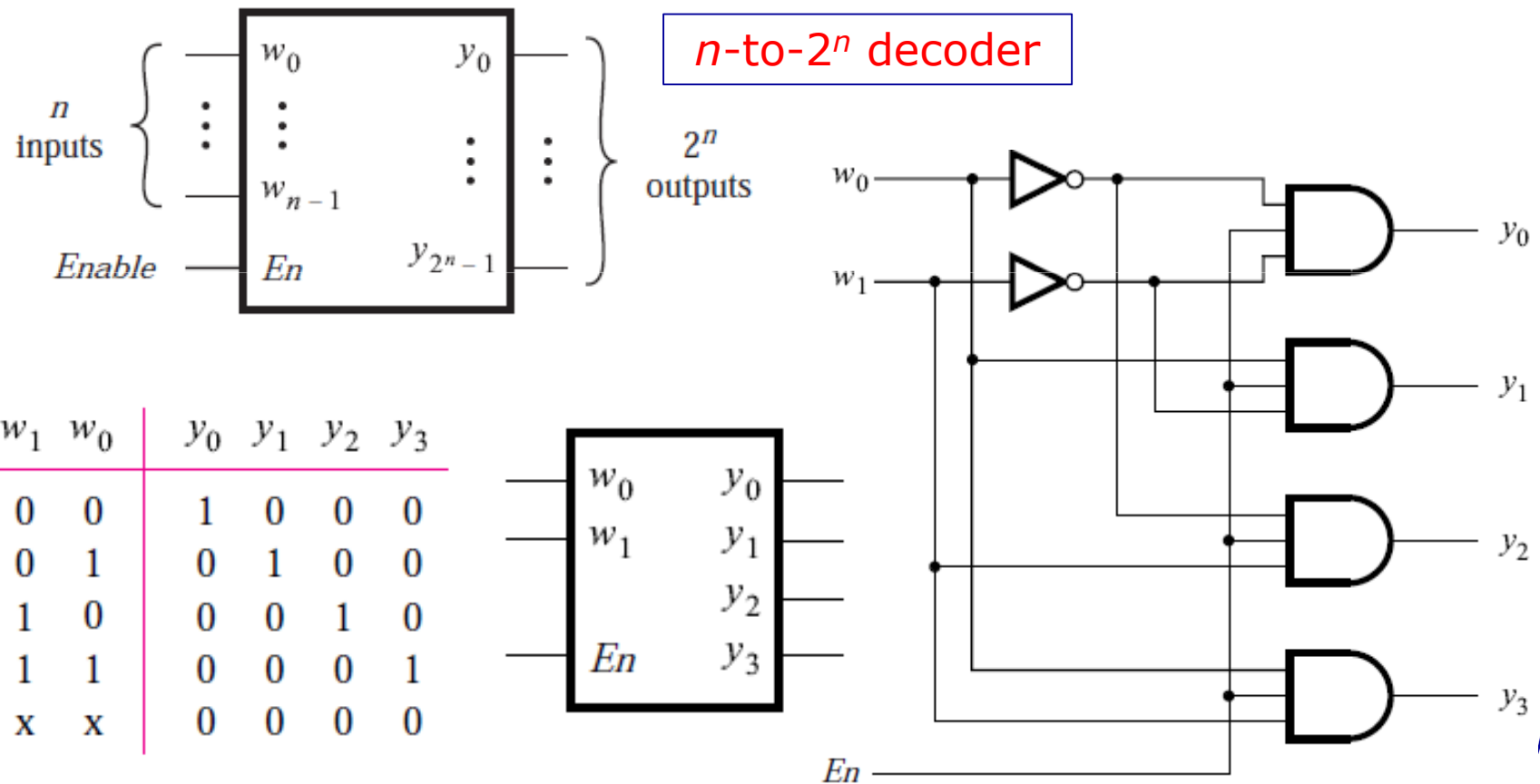


Decoder

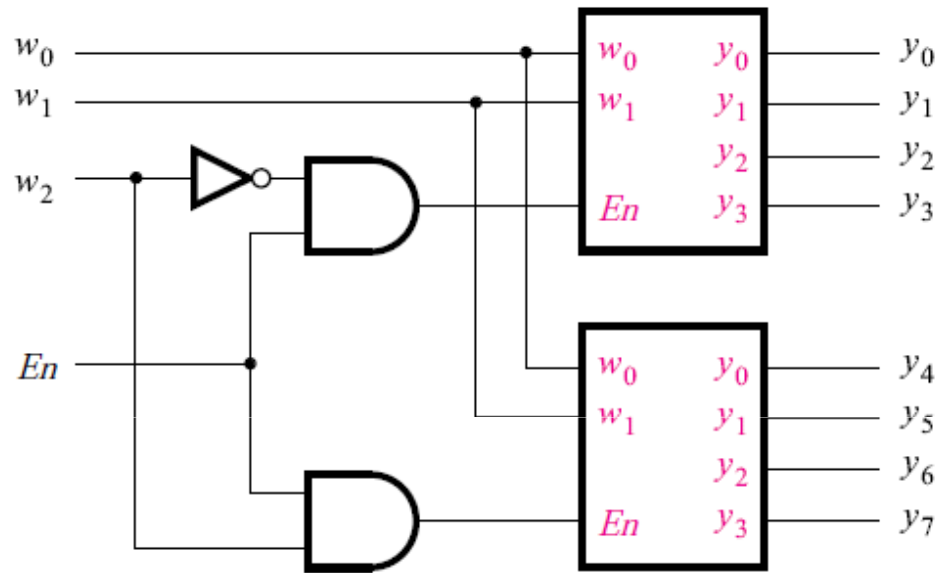


3-to-8 decoder using
2-to-4 decoder


4-to-1 MUX using
2-to-4 decoder

 

4-to-16 Decoder

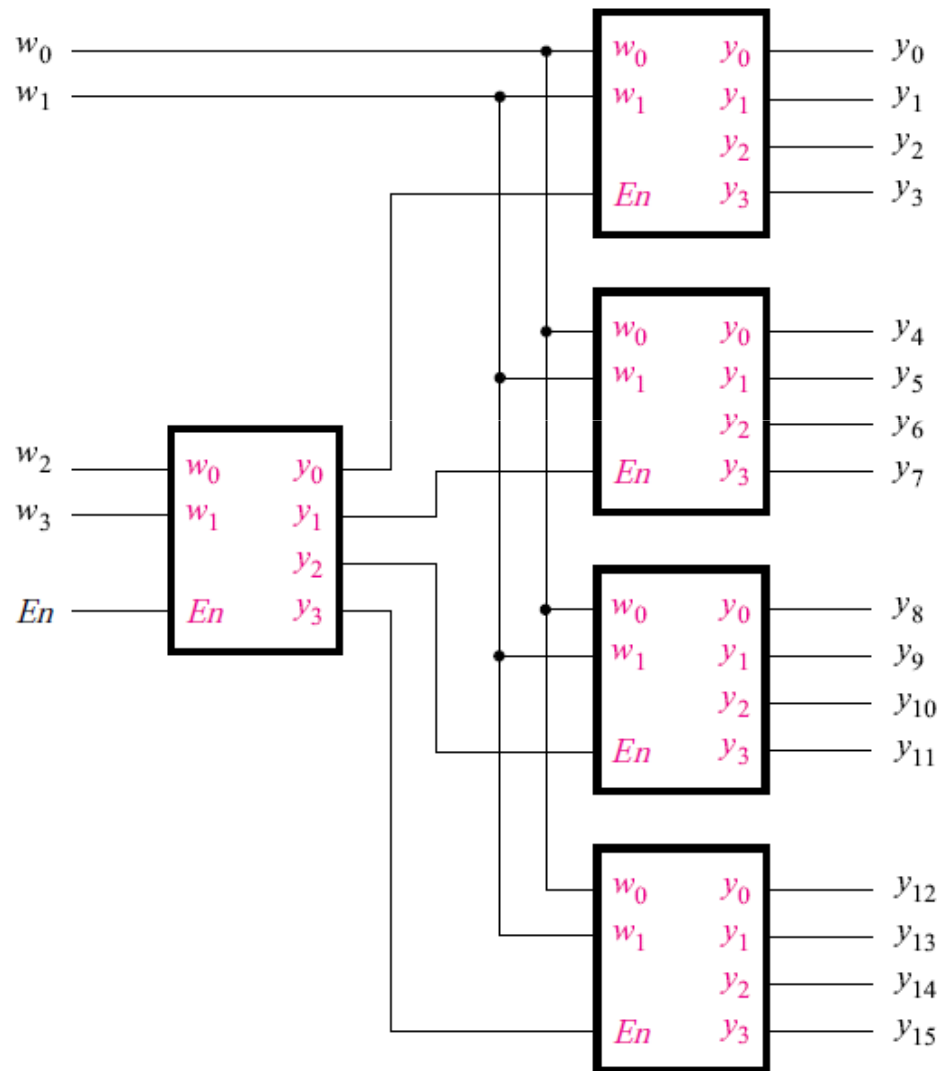


Demultiplexer (DEMUX)

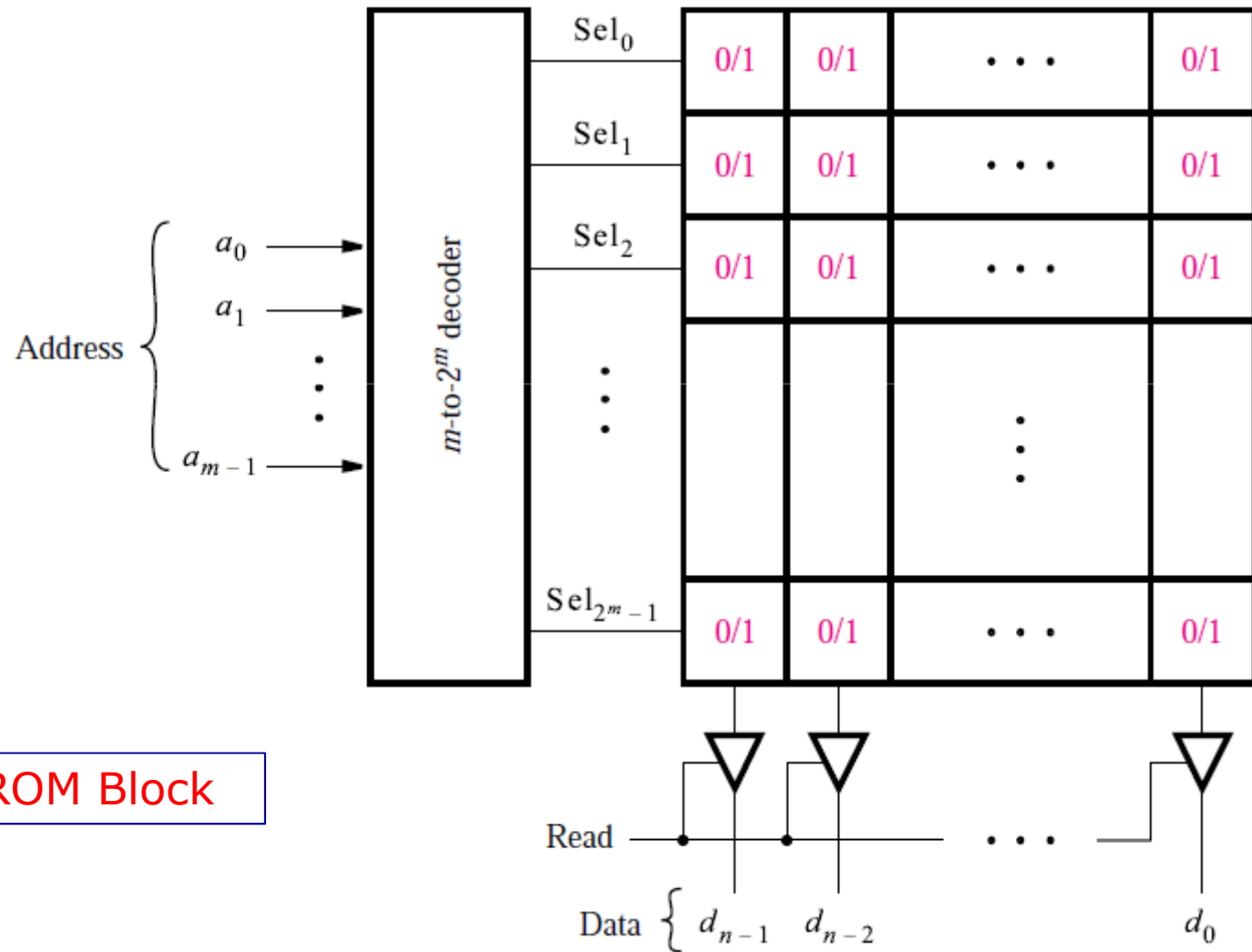


A $2^m \times m$ ROM Block

Encoder

 

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 


4-to-2 binary encoder

Hamming Code

- In “linear block code” family.
- Can correct 1-bit error or detect 2-bit error.
- Add parity bits to message bits.
- Typically use notation (n,k) Hamming code, which means n total bits, k message bits.
- Clearly there are $(n-k)$ parity bits.

(7,4) Hamming Code

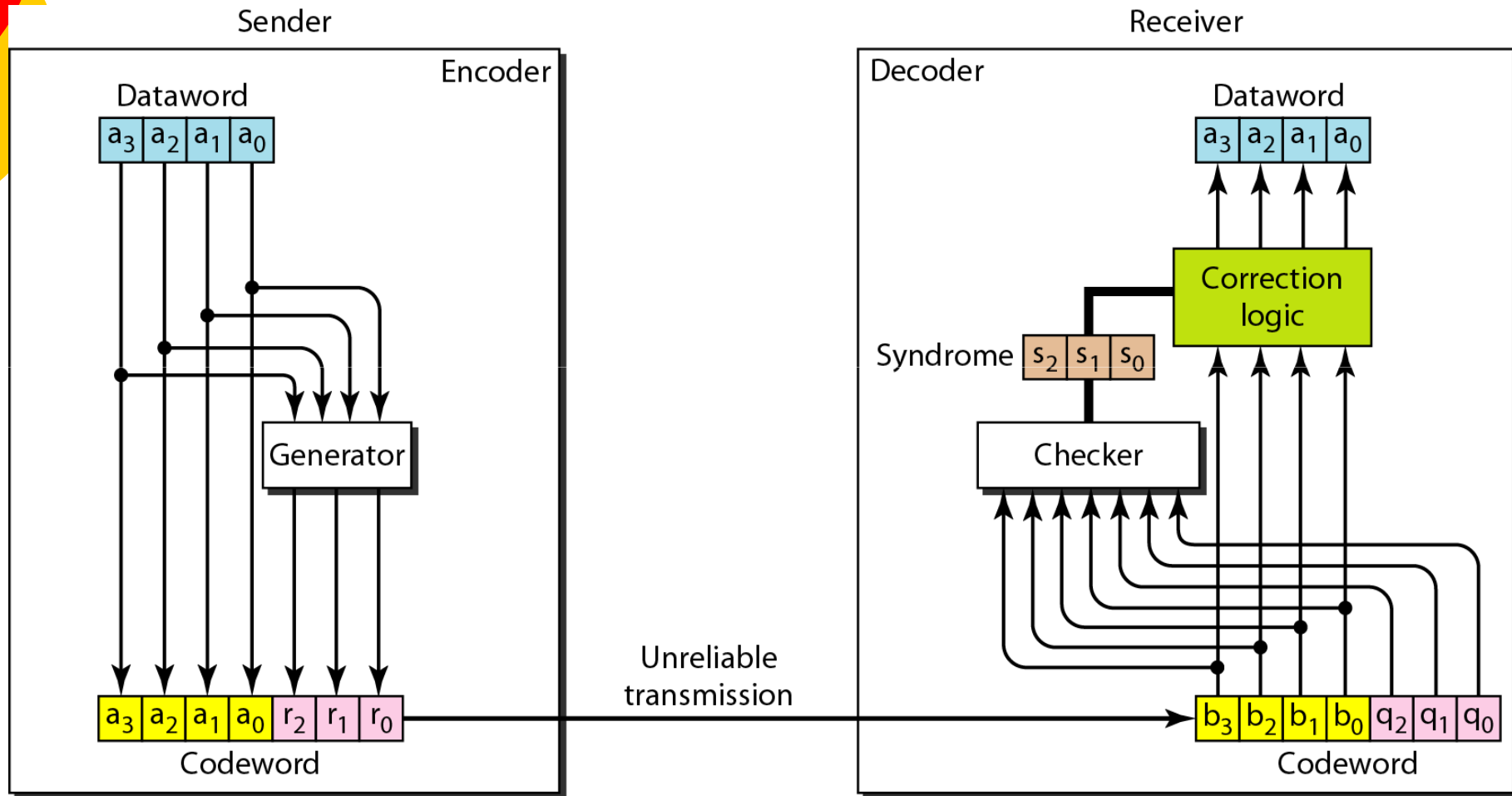

System Structure

Codewords

<i>Datawords</i>	<i>Codewords</i>	<i>Datawords</i>	<i>Codewords</i>
0000	0000 000	1000	1000 110
0001	0001 101	1001	1001 011
0010	0010 111	1010	1010 001
0011	0011 010	1011	1011 100
0100	0100 011	1100	1100 101
0101	0101 110	1101	1101 000
0110	0110 100	1110	1110 010
0111	0111 001	1111	1111 111

Codeword : $a_3a_2a_1a_0r_2r_1r_0$ with

$$r_0 = a_0 \oplus a_1 \oplus a_2; r_1 = a_1 \oplus a_2 \oplus a_3; r_2 = a_0 \oplus a_1 \oplus a_3$$

Syndrome


- Error pattern is given by “syndrome”, i.e., $s_2s_1s_0$ (=s) where

$$s_0 = b_0 \oplus b_1 \oplus b_2 \oplus q_0; s_1 = b_1 \oplus b_2 \oplus b_3 \oplus q_1; s_2 = b_0 \oplus b_1 \oplus b_3 \oplus q_2$$

<i>Syndrome</i>	000	001	010	011	100	101	110	111
<i>Error</i>	None	q_0	q_1	b_2	q_2	b_0	b_3	b_1


- Example : Send 0110100
 - Receive 0110100 -> $s = 000$ -> No error
 - Receive 0111100 -> $s = 101$ -> Error at b_0
 - Receive 0010100 -> $s = 011$ -> Error at b_2

(7,4) Hamming Encoder

 


Exercise : Design the
(7,4) Hamming Decoder

Gate Arrays (Programmable Logic Device)

 

Basic
Structure
(AND-OR GA)

Example

 


$$f = a'b' + abc$$

$$g = a'b'c' + ab + bc$$

$$h = a'b' + c$$

Simplified Diagram

 


Using ROM

$$W(A, B, C, D) = \sum m(3, 7, 8, 9, 11, 15)$$

$$X(A, B, C, D) = \sum m(3, 4, 5, 7, 10, 14, 15)$$
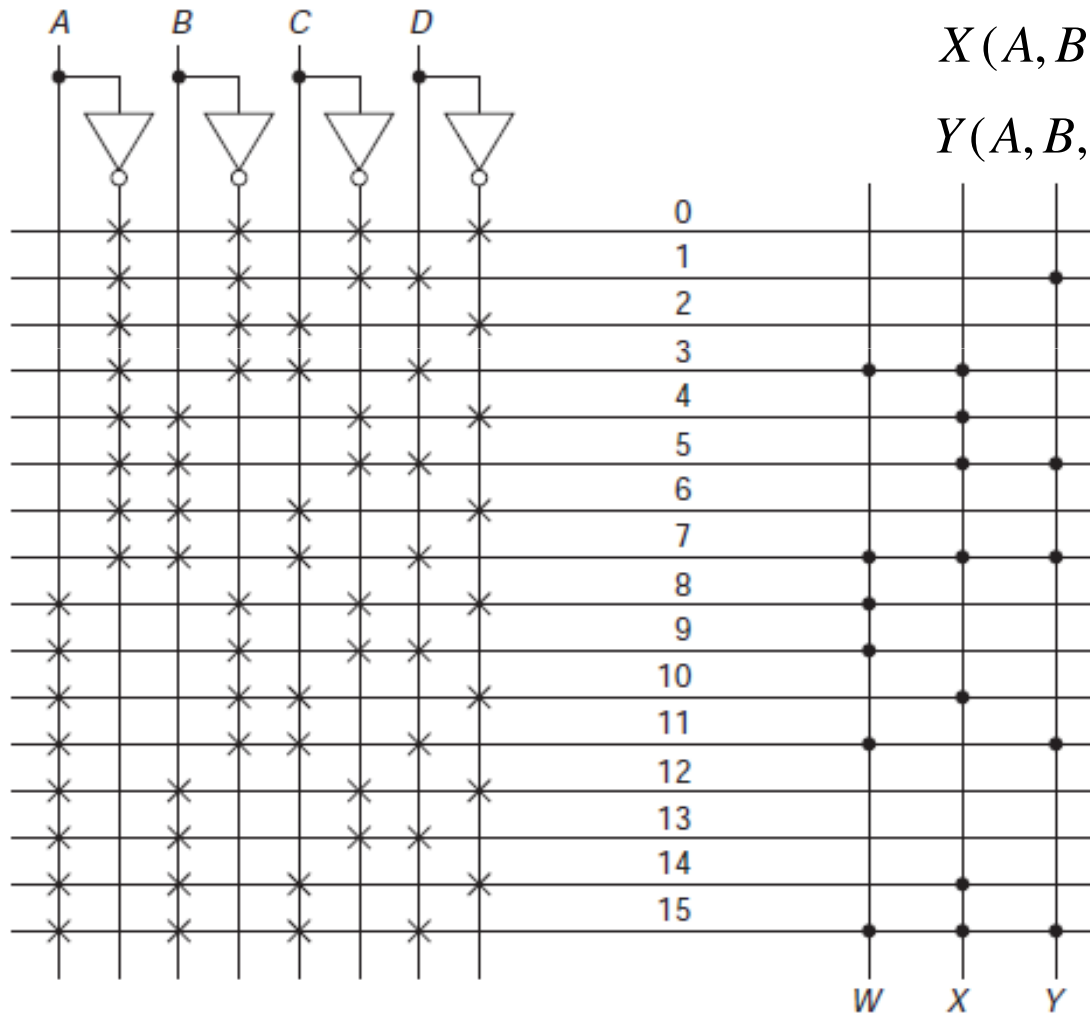
$$Y(A, B, C, D) = \sum m(1, 5, 7, 11, 15)$$



Using PLA

$$W(A, B, C, D) = \sum m(3, 7, 8, 9, 11, 15); X(A, B, C, D) = \sum m(3, 4, 5, 7, 10, 14, 15)$$

$$Y(A, B, C, D) = \sum m(1, 5, 7, 11, 15)$$

		AB			
		00	01	11	10
CD	00				1
	01				1
	11	1	1	1	1
	10				

W

		AB			
		00	01	11	10
CD	00		1		
	01		1		
	11	1	1	1	
	10				1

X

		AB			
		00	01	11	10
CD	00				
	01	1	1		
	11		1	1	1
	10				


Y

$$W = AB'C' + CD = AB'C' + A'CD + ACD$$

$$X = A'BC' + ACD' + A'CD + \{BCD \text{ or } ABC\}$$

$$Y = A'C'D + ACD + \{BCD \text{ or } A'BD\}$$

Using PLA (2)

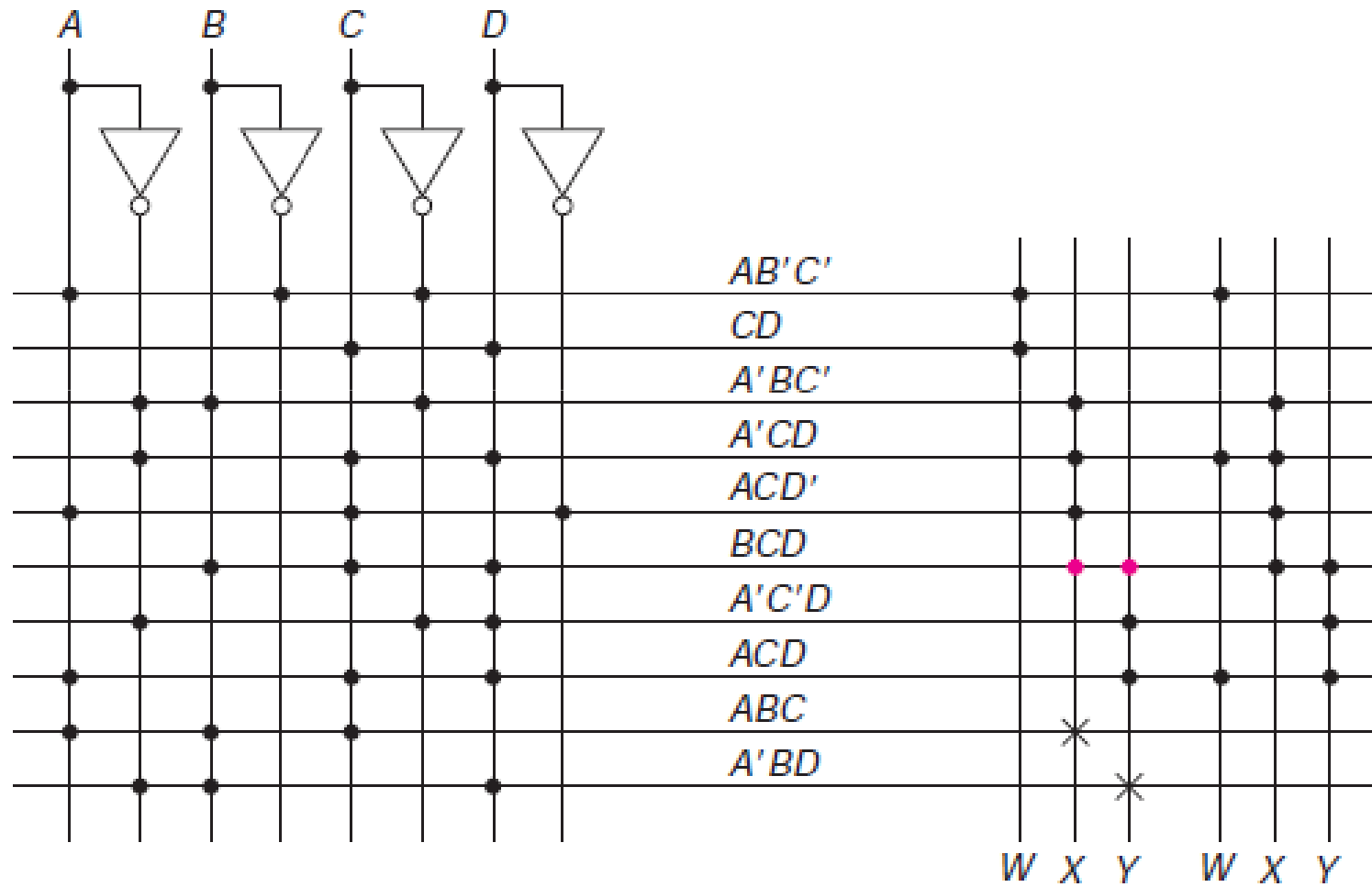

Using Programmable Array Logic

