

SEQUENTIAL CIRCUITS : INTRODUCTION


- ❑ Sequential Circuits
- ❑ Storage Elements (Memory)
 - ❑ Latches
 - ❑ Flip-Flops



SEQUENTIAL CIRCUITS

- ❖ All of the previous circuits were combinational circuits
 - Current flowed in at one end and out the other
 - Combinational circuits cannot *retain* values
 - If we want to build a kind of memory, we need to use a sequential circuit
 - ❖ In a sequential circuit, current flows into the circuit and stays there
 - ❖ This is done by looping the output back into the input
 - Sequential circuits will be used to implement 1-bit storage
 - We can then combine 1-bit storage circuits into groups for n-bit storage (registers, cache)
 - ❖ These circuits will be known as flip-flops because they can flip from one state (storing 1) to another (storing 0) or vice versa

COMBINATIONAL VS SEQUENTIAL

 


❖ A **combinational** circuit:

- At any time, outputs depends only on inputs
- Changing inputs changes outputs
- No regard for previous inputs
- No memory (history)
- Time is ignored !




COMBINATIONAL VS SEQUENTIAL (2)

 

❖ A **sequential** circuit:

- A combinational circuit with **feedback** through **memory**
 - The stored information at any time defines a **state**
- Outputs depends on inputs and previous inputs
 - Previous inputs are stored as binary information into memory
- Next state depends on inputs and present state

EXAMPLES OF SEQUENTIAL SYSTEMS

 

Traffic light




ATM



Vending machine

What is common between these systems?


COMBINATIONAL ADDER

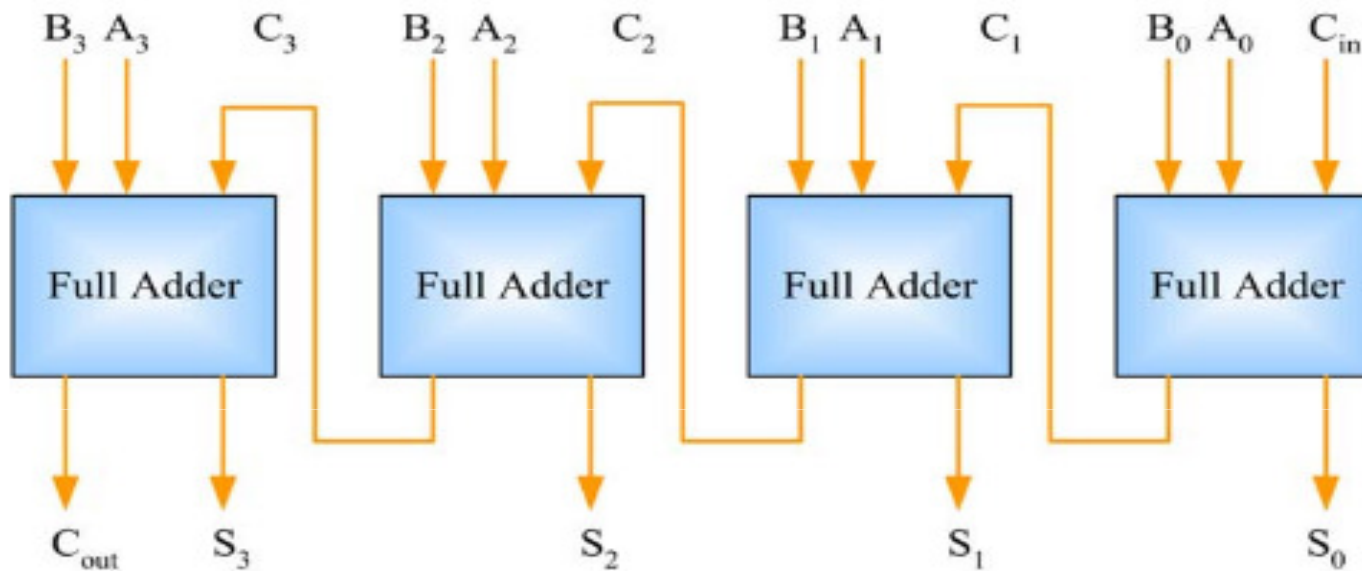

- 4-bit adder (ripple-carry)
 - Notice how carry-out propagates
 - One adder is active at a time
- 4 full adders are needed



SEQUENTIAL ADDER

 


- 1-bit memory and 2 4-bit memory
- Only one full-adder!
- 4 clocks to get the output
- The 1-bit memory defines the circuit state (0 or 1)

TYPES OF SEQUENTIAL CIRCUITS


- Two types of sequential circuits:
 - **Synchronous:** The behavior of the circuit depends on the input signal at discrete instances of time (*also called clocked*)
 - **Asynchronous:** The behavior of the circuit depends on the input signals at any instance of time and the order of the inputs change
 - A combinational circuit with feedback

SYNCHRONOUS SEQUENTIAL CIRCUITS

 

- Synchronous circuits employs a synchronizing signal called **clock** (a periodic train of pulses; 0s and 1s)
- A clock determines **when** computational activities occur
- Other signals determines **what** changes will occur

SYNCHRONOUS SEQUENTIAL CIRCUITS

 

- The storage elements (memory) used in clocked sequential circuits are called **flip-flops**
 - Each flip-flop can store one bit of information 0,1
 - A circuit may use many flip-flops; together they define the circuit state
- Flip-Flops (memory/state) update **only** with the clock

STORAGE ELEMENTS (MEMORY)

- A storage element can maintain a binary state (0,1) indefinitely, until directed by an input signal to switch state
- Main difference between storage elements:
 - Number of inputs they have
 - How the inputs affect the binary state
- Two main types:
 - Latches (level-sensitive)
 - Flip-Flops (edge-sensitive)
- Latches are useful in asynchronous sequential circuits
- Flip-Flops are built with latches

CHARACTERISTIC TABLES

- A characteristic table defines the operation of a latch or flip-flop in a tabular form
- Next state is defined in terms of the current state and the inputs
 - $Q(t)$ (or just Q) refers to current state (**before** the clock arrives)
 - $Q(t+1)$ (or Q_+) refers to next state (**after** the clock arrives)
- Similar to the truth table in combinational circuits

Flip-Flop Characteristic Tables

JK Flip-Flop			
J	K	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

D Flip-Flop		
D	$Q(t + 1)$	
0	0	Reset
1	1	Set


T Flip-Flop		
T	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

LATCHES

- A **latch** is a binary storage element
- Can store a 0 or 1
- The most basic memory
- Easy to build
 - Built with gates (NORs, NANDs, NOT)




SR LATCH

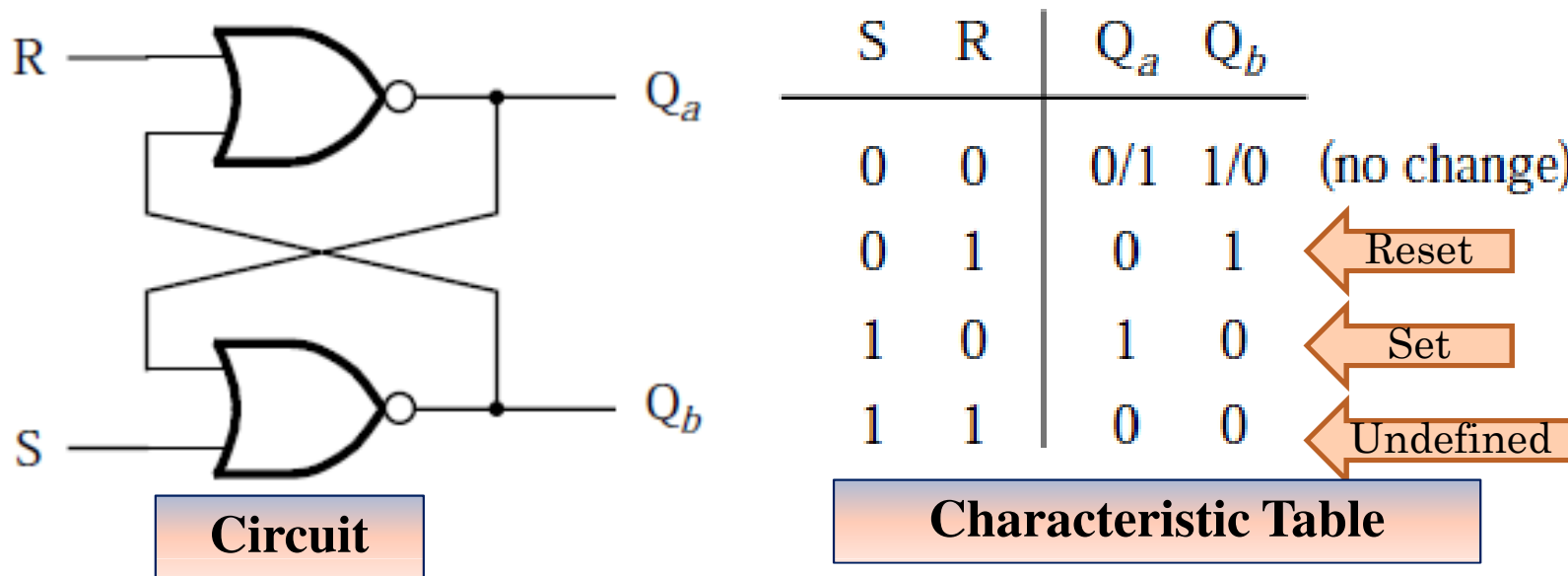

- Two states: Set ($Q_a = 1$) and Reset ($Q_a = 0$)
- When $S=R=0$, Q_a remains the same, $S=R=1$ is not allowed!
- Normally, $S=R=0$ unless the state needs to be changed (memory?)
- State of the circuit depends not only on the current inputs, but also on the recent history of the inputs


SR LATCH TIMING DIAGRAM

 


UNSTABLE STATE (OSCILLATION)

- ❖ After t_{10} : If S and R remains 0,
 - $Q_a : 0 \rightarrow 1 \rightarrow 0 \rightarrow 1$
 - $Q_b : 0 \rightarrow 1 \rightarrow 0 \rightarrow 1$
 - If the delays through two NOR gates are exactly the same, oscillation continues indefinitely \rightarrow Unstable!
 - If the delays slightly different \rightarrow one “uncertain” state
 - $S=R=1$ not allowed!

GATED SR LATCH

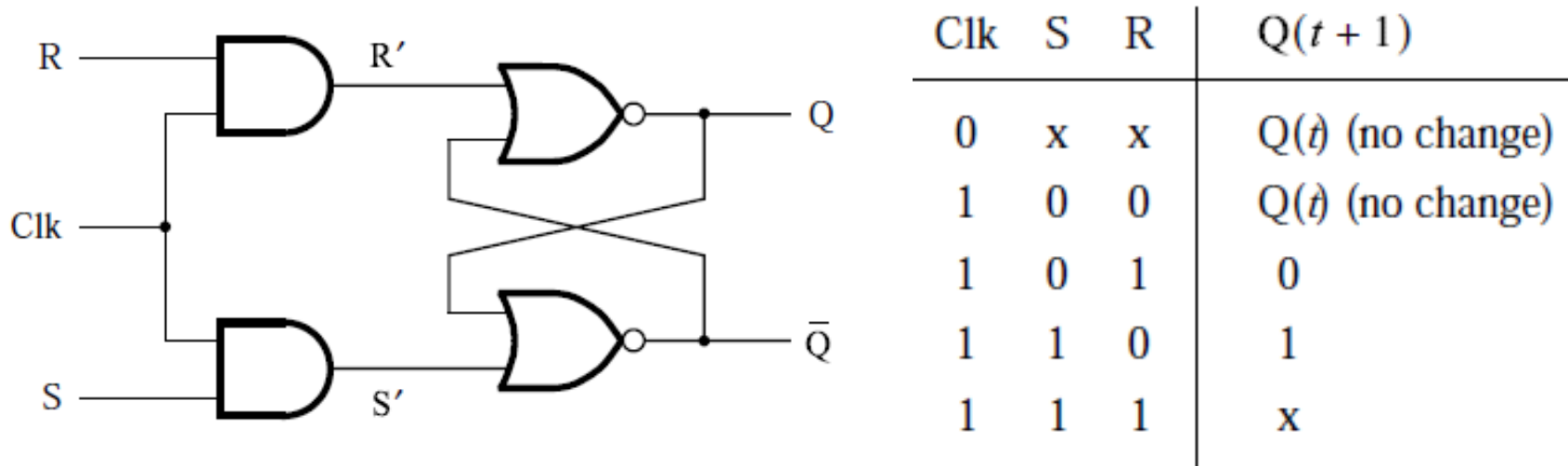


 - An SR Latch can be modified to control when it changes
- An additional input signal Clock (Clk)
- When $C=0$, the S and R inputs have no effect on the latch
- When $C=1$, the inputs affect the state of the latch and possibly the output




**Graphical
Symbol**

GATED SR LATCH TIMING DIAGRAM

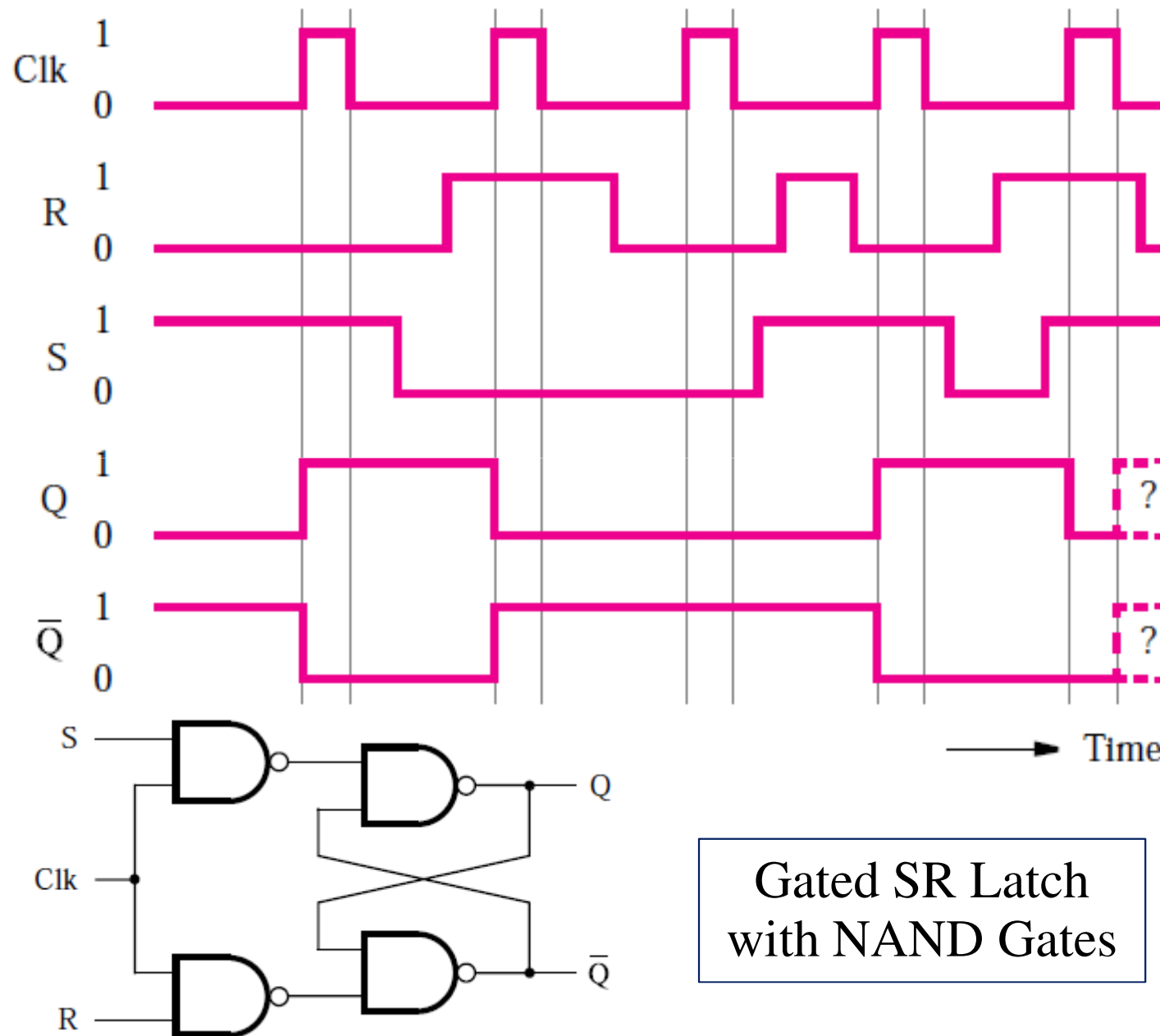



GATED D LATCH

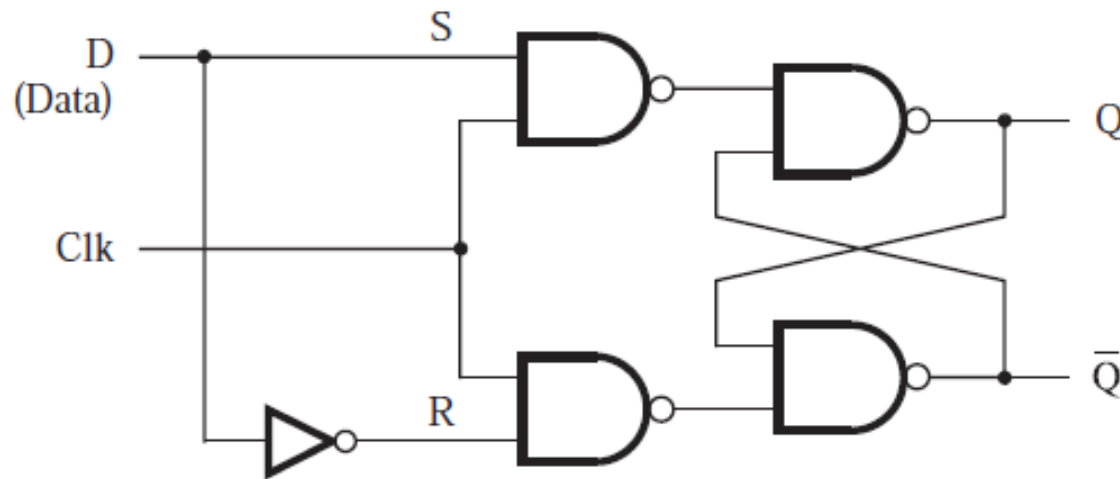

- To forbid $S=R=1$ input, only one input (**D**)
 - **D** connects to **S**
 - **D'** connects to **R**
- **D** stands for data
- Output follows the input when $\text{Clk} = 1$
- When $\text{Clk} = 0$, **Q** remains the same


GATED D LATCH

Clk	D	$Q(t + 1)$
0	x	$Q(t)$
1	0	0
1	1	1

  



EFFECT OF PROPAGATION DELAY

- ❖ Condition : D signal is stable (not changing) at the time Clk changes (from 0 to 1, or from 1 to 0)
- ❖ Key quantities:
 - Setup time (t_{su}) : The minimum time D signal must be stable **prior** to the negative/positive edge of the Clk signal. (typical 0.3 ns)
 - Hold time (t_h) : The minimum time D signal must remain stable **after** the negative/positive edge of the Clk signal. (typical 0.2 ns)

 

MASTER-SLAVE D FLIP-FLOP

❖ Q changes at the negative edge.

 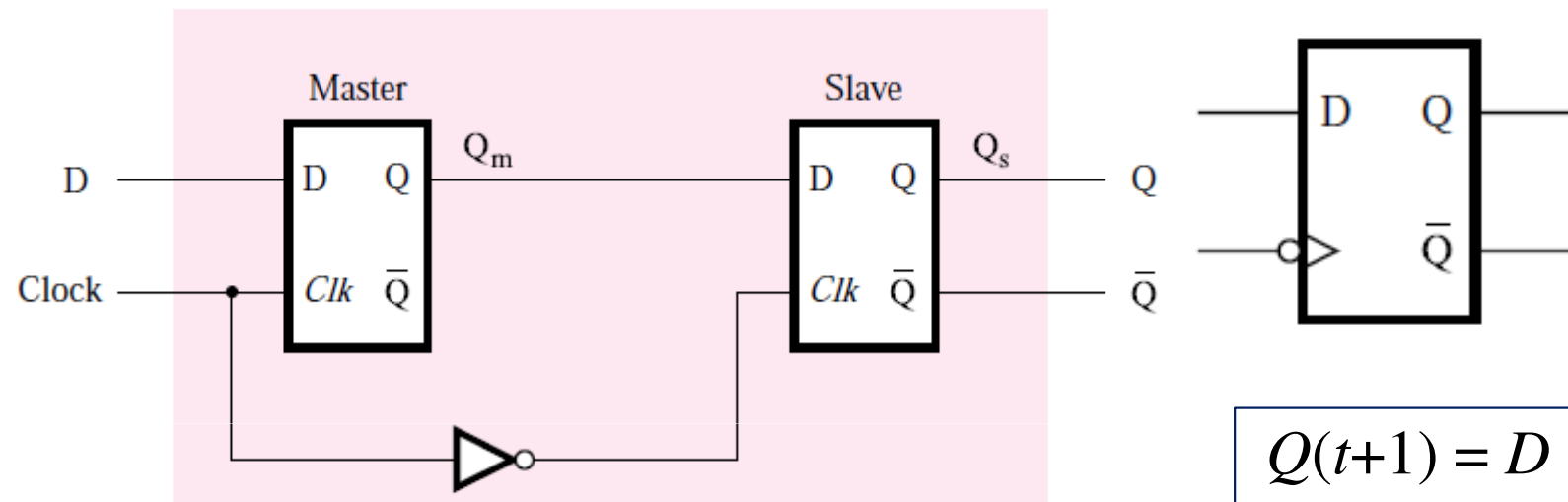



EDGE-TRIGGERED D FLIP-FLOP

❖ Q changes at the positive edge.

❖ Use fewer transistors.



❖ Operation:

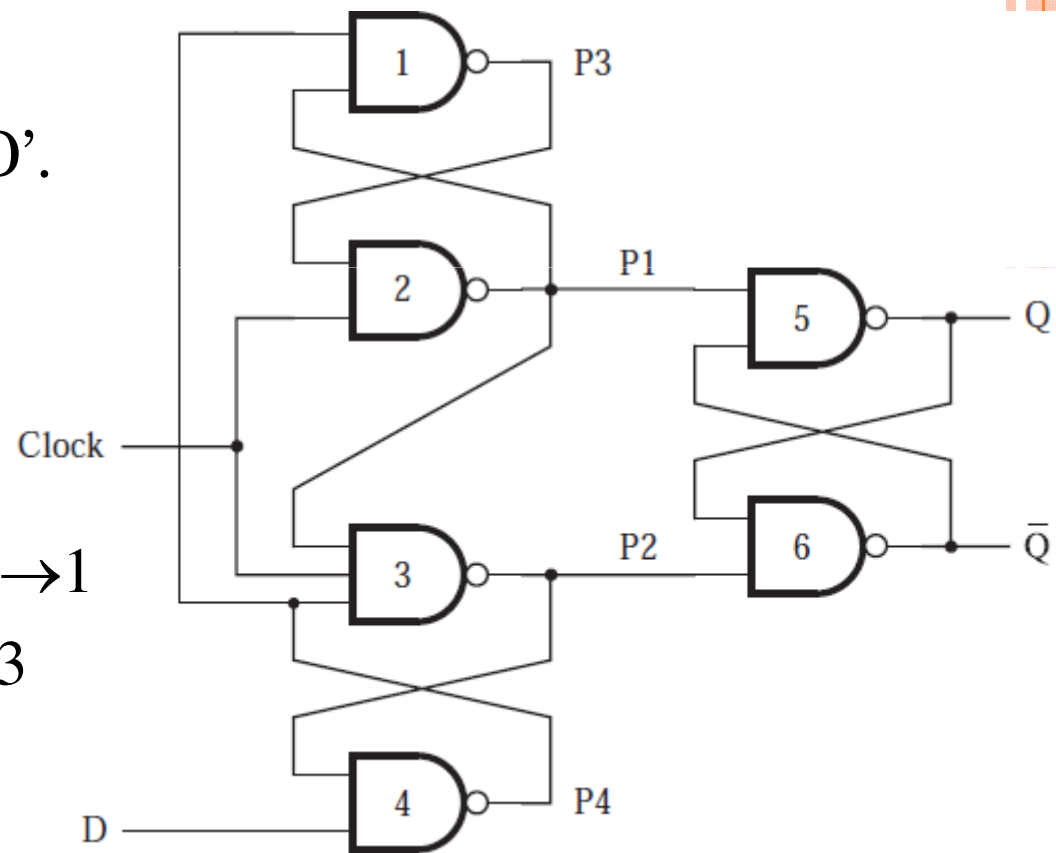 - Clock=0: $P1=P2=1$, Q unchanged, $P3=D$, $P4=D'$.
- Clock: $0 \rightarrow 1$: $P3, P4$ transmitted through $G2, G3 \rightarrow P1=D', P2=D \rightarrow Q=D$
- $P3, P4$ stable when Clock $0 \rightarrow 1$
- t_{su} : Gate delay from D to $P3$ through $G4, G1$
- t_h : Gate delay through $G3$



D LATCH VS D FLIP-FLOP

  - ❖ D Latch : Level-sensitive
- ❖ D Flip-Flop : Edge-sensitive
 - ❖ Positive-edge Triggered (Q_b)
 - ❖ Negative-edge Triggered (Q_c)





MASTER-SLAVE D FF WITH CLEAR, PRESET


❖ Clear=1 \rightarrow Q=0, Preset=0 \rightarrow Q=1

❖ Clear=Preset=0 \rightarrow Unstable

  ❖ “Asynchronous” clear
(unrelated to clock signal)




MASTER-SLAVE D FF WITH CLEAR, PRESET

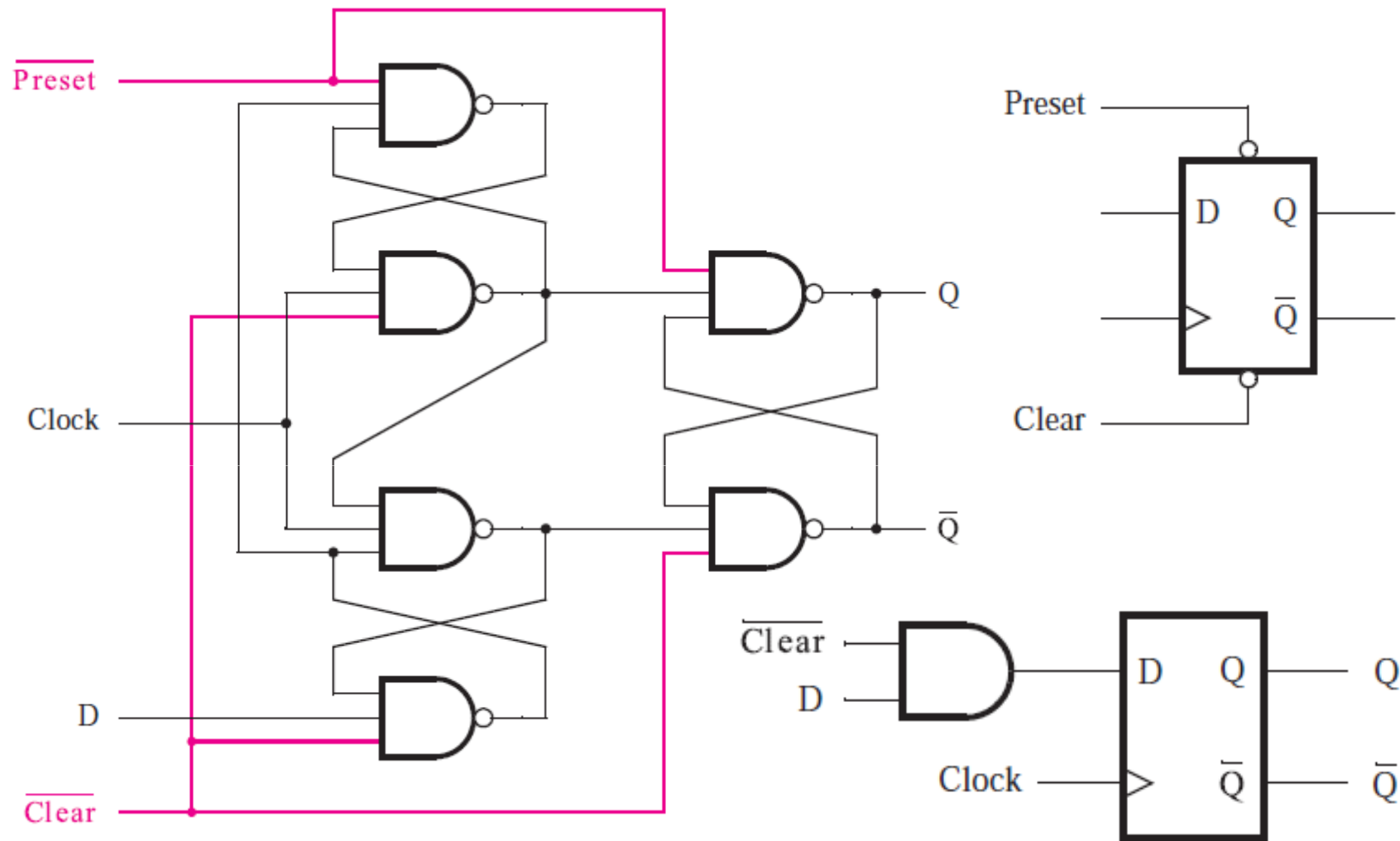

Adding a
synchronous clear


CLOCK-TO-Q PROPAGATION DELAY

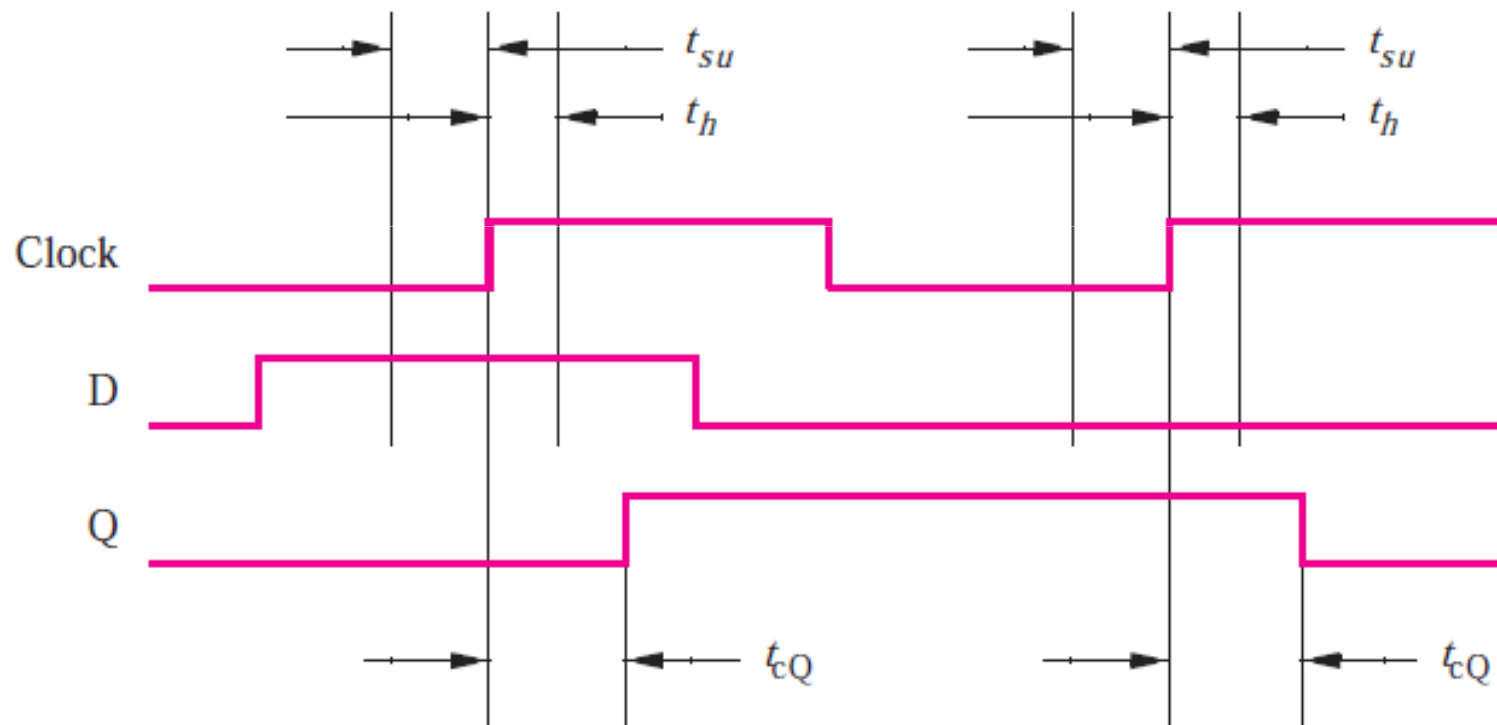❖ t_{cQ} : Time before Q changes after a positive clock edge.





T FLIP-FLOP

 ❖ T="Toggle" → toggle when T=1, clock 0 → 1



T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

  


JK FLIP-FLOP

- ❖ Similar to SR FF with $J=S$, $K=R$
- ❖ $J=K=1 \rightarrow$ toggle
- ❖ $J=K \rightarrow$ T-FF


J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

$$Q(t+1) = JQ' + K'Q$$

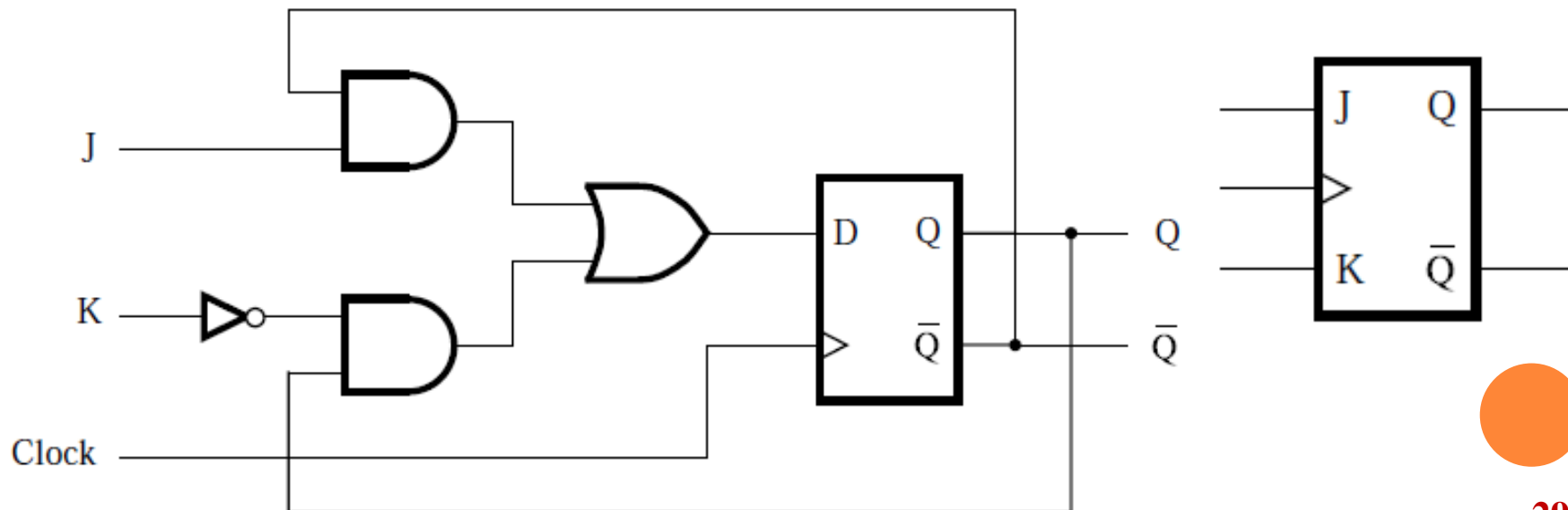

SHIFT REGISTER

❖ Register = a set of n flip-flops

 


	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

Output shifts to the right at positive-edge

PARALLEL-ACCESS SHIFT REGISTER

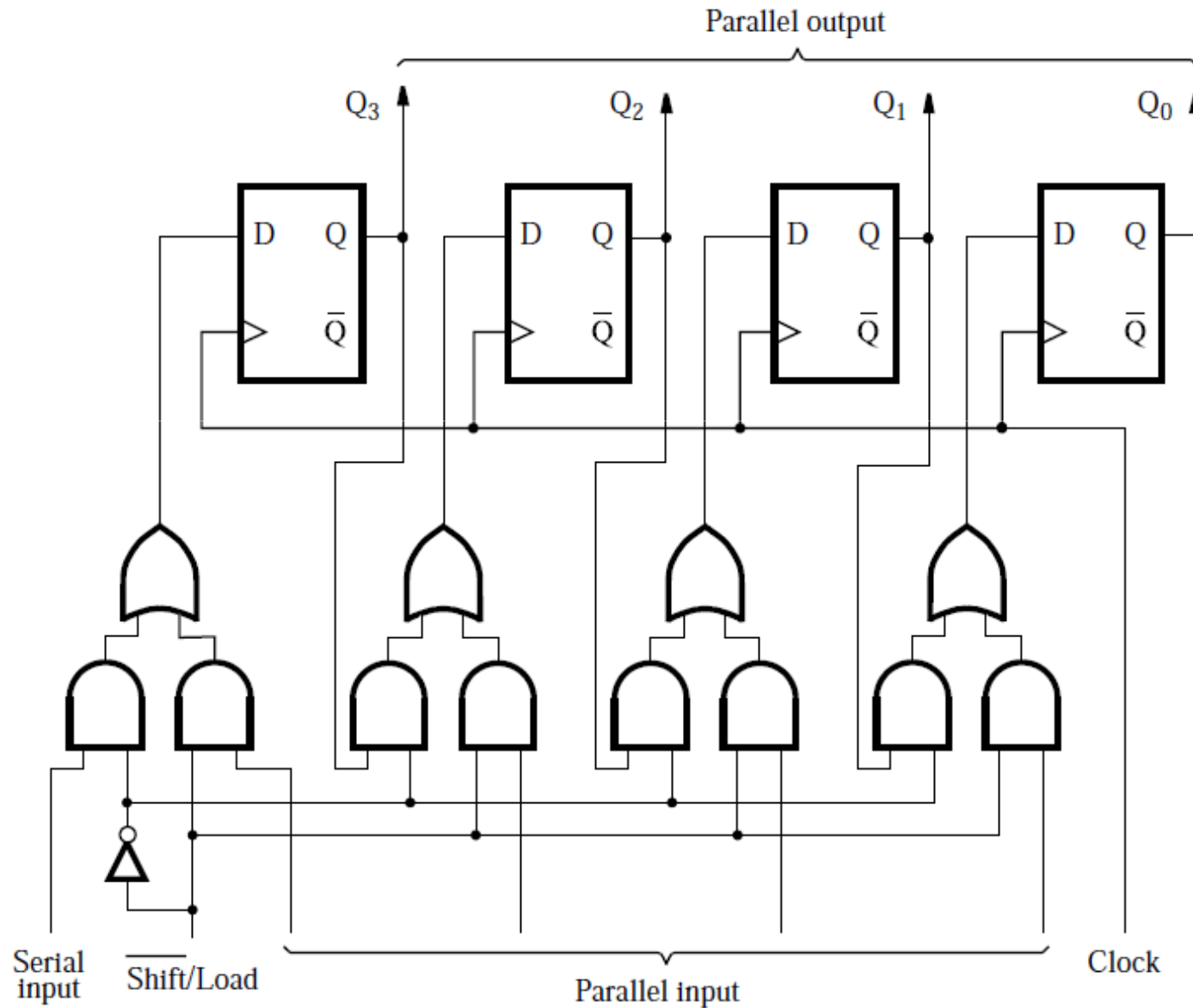❖ $\overline{\text{shift/load}}=0 \rightarrow \text{shift register}$, $\overline{\text{shift/load}}=1 \rightarrow \text{parallel access}$





ASYNCHRONOUS COUNTER (UP-COUNTER)



❖ Q1 changes after Q0, Q2 changes after Q1
→ similar to ripple-carry adder

❖ “Ripple” Counter

❖ Modulo-8, i.e.,
0,1,...,7,0,...

 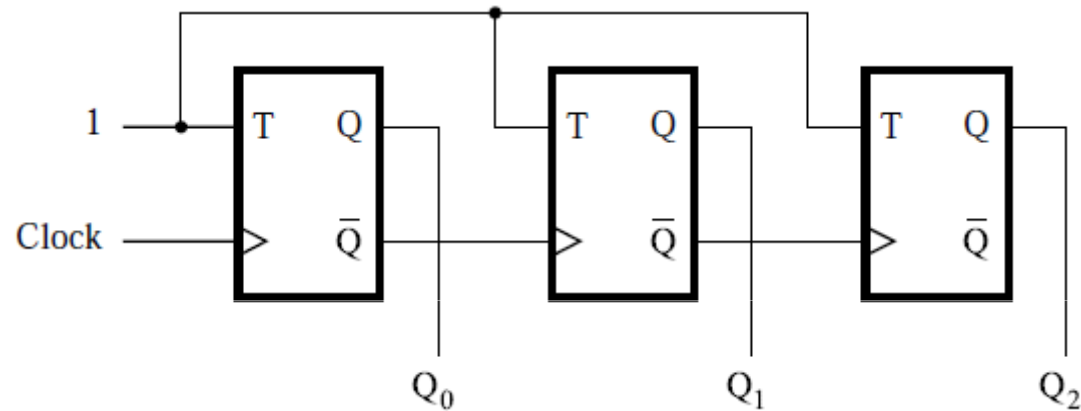

ASYNCHRONOUS COUNTER (DOWN-COUNTER)

 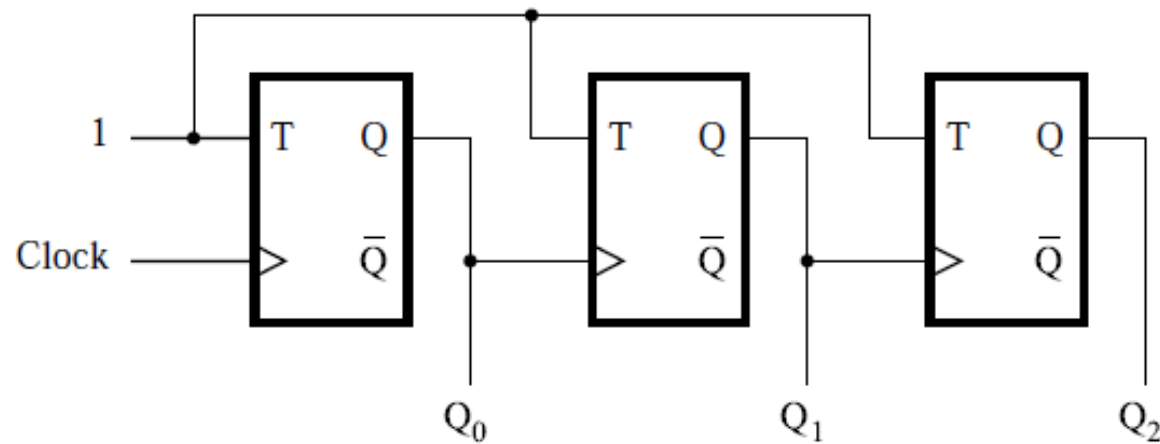

SYNCHRONOUS COUNTER

❖ Asynchronous counter : delay -> Not fast

❖ Synchronous counter can work faster.

❖ 3-bit up-counter :
table 7.1:

❖ For n-bit counter:

$$T_0 = 1$$

$$T_1 = Q_0$$

$$T_2 = Q_0 Q_1$$

$$T_3 = Q_0 Q_1 Q_2$$


⋮

$$T_n = Q_0 Q_1 Q_2 \dots Q_{n-1}$$



Table 7.1

Derivation of the synchronous up-counter.

Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

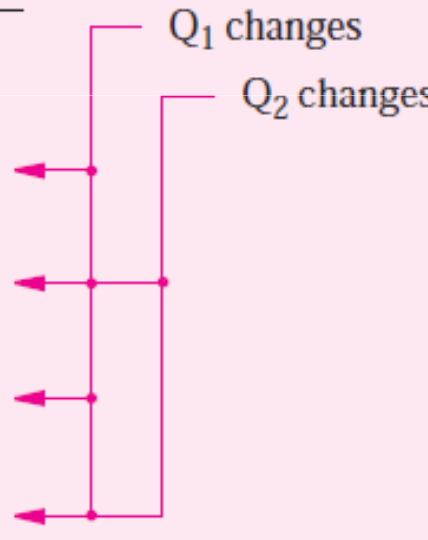


SYNCHRONOUS COUNTER (UP-COUNTER)

 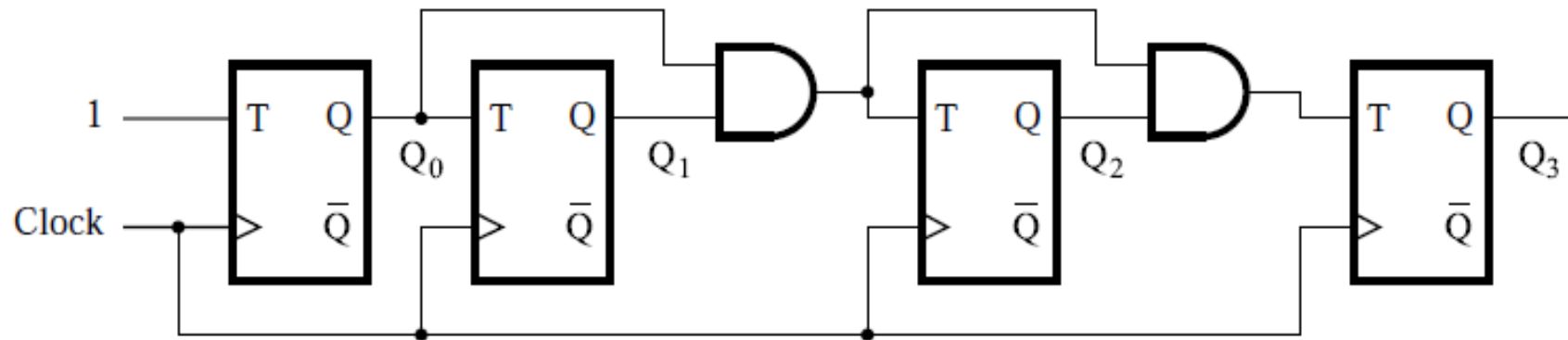


COUNTER WITH ENABLE & CLEAR

 - ❖ Enable=0 \rightarrow T=0, Enable=1 \rightarrow Counter
- ❖ Clear=0 \rightarrow Reset ($Q_0=Q_1=Q_2=0$)



RING COUNTER

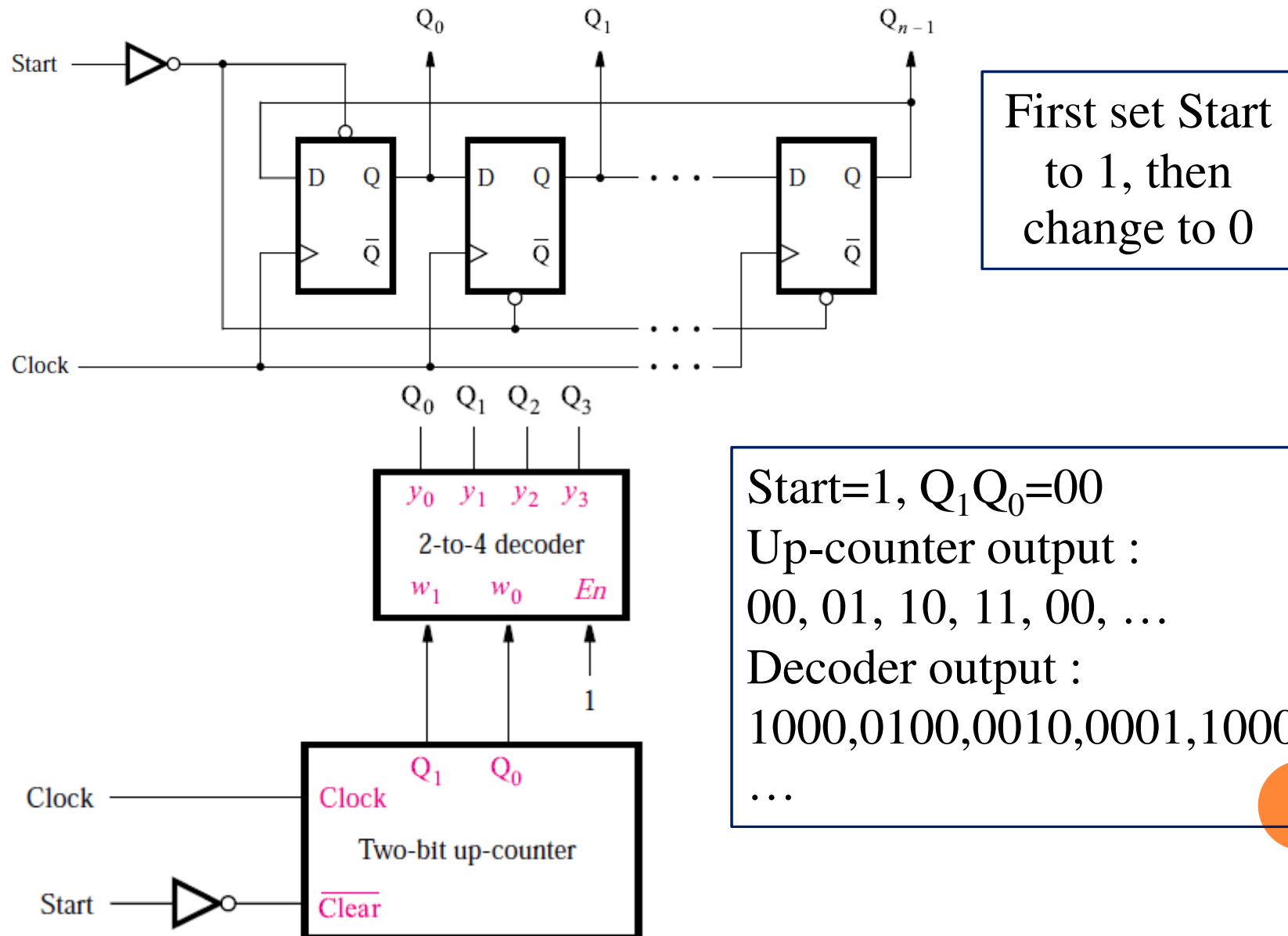1000→0100→0010→0001→1000→... “One-Hot” Code




A REGISTER FILE


The decoder accepts a 3-bit register number from the control unit

This along with the system clock selects the register

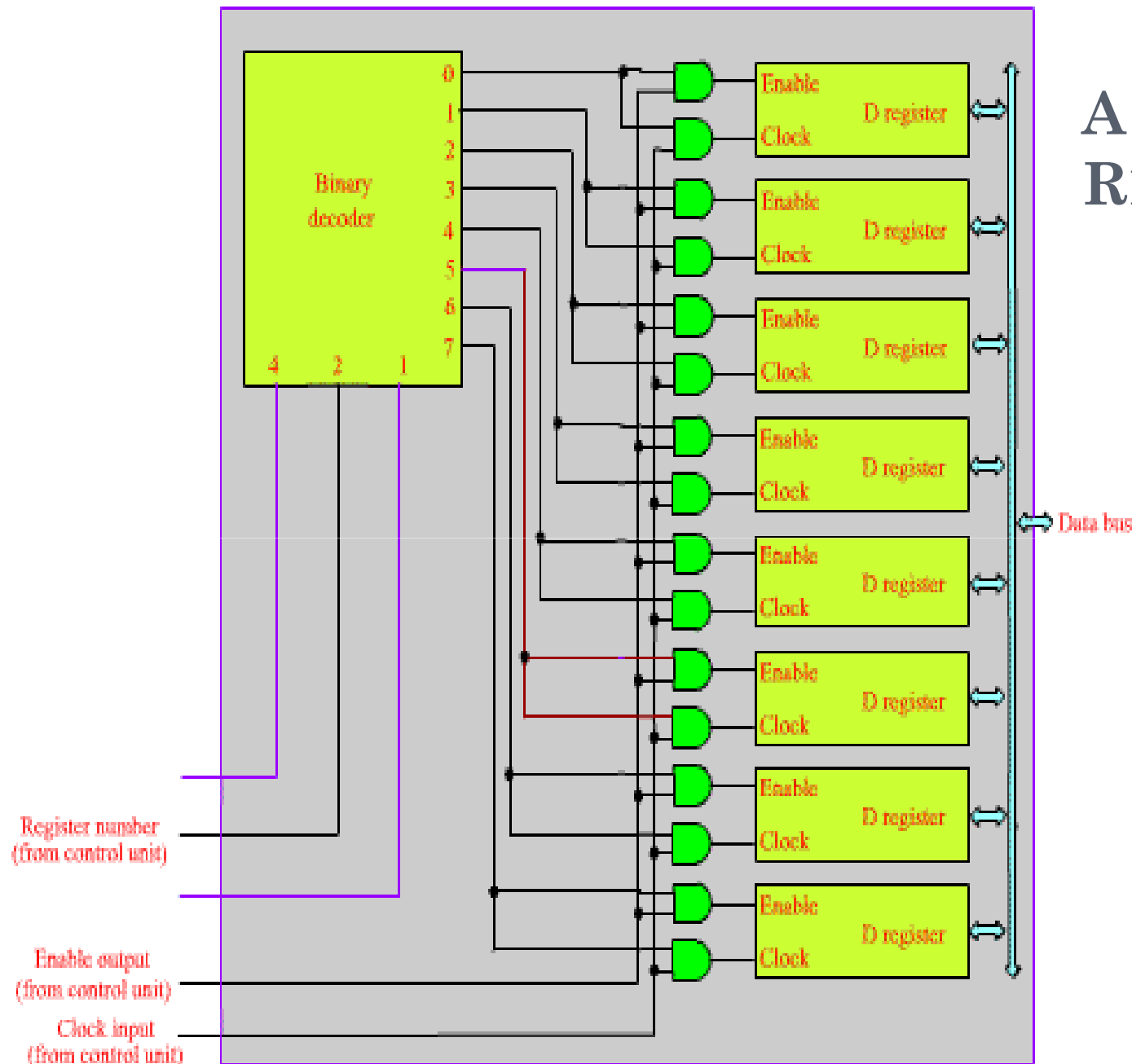The data bus is used for both input and output to the selected register



A 4x3 MEMORY

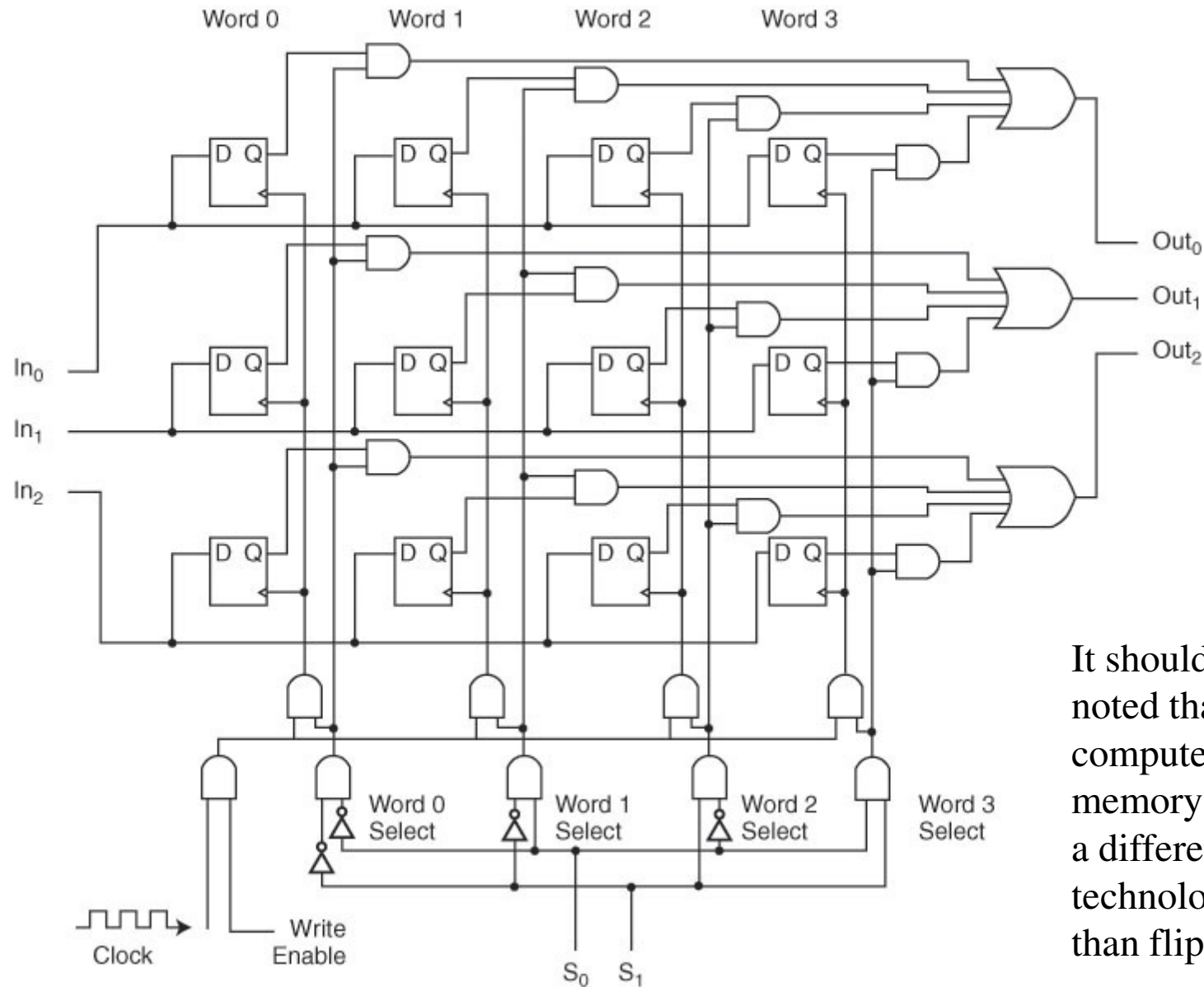

This is a collection of flip-flops that can store 4 items (each consisting of 3 bits)

The two bit selector $S_0 S_1$ chooses which of the 4 items is desired

It should be noted that computer memory uses a different technology than flip-flops



TIMING ANALYSIS OF FLIP-FLOP

❖ Want to find the **maximum clock**

frequency $f_{max} = 1/T_{min}$ (T_{min} :
minimum clock period)

❖ Consider the circuit on the right

❖ Operation :


1. D is loaded with positive clock edge.
2. D propagates to Q
3. Q propagates through NOT.

❖ T_{min} is given by $T_{min} = t_{cQ} + t_{NOT} + t_{su}$

❖ Example : t_{su} 0.6 ns, t_h 0.4 ns, $0.8 \text{ ns} \leq t_{cQ} \leq 1 \text{ ns}$,
and assume $t_{NOT} = 1 + 0.1k$ (k : Number of input to the gate)

Thus, $T_{min} = 1 + 1.1 + 0.6 = 2.7 \text{ ns}$.

 And, $f_{max} = 1/2.7(\text{ns}) = 370.37 \text{ MHz}$



TIMING ANALYSIS OF A 4-BIT COUNTER

❖ First find the longest path (critical path).

❖ In this example, $Q_0 \rightarrow Q_3$

❖ The delay of this critical path includes


- ❖ clock-to-Q of Q_0
- ❖ delay through 3 AND's
- ❖ delay through 1 XOR

❖ Also need to take into account setup time of Q_3 .

❖ Thus,

$$\begin{aligned} T_{min} &= t_{cQ} + 3t_{AND} + t_{XOR} + t_{su} \\ &= 1 + 3(1.2) + 1.2 + 0.6 \\ &= 6.4 \text{ ns} \end{aligned}$$
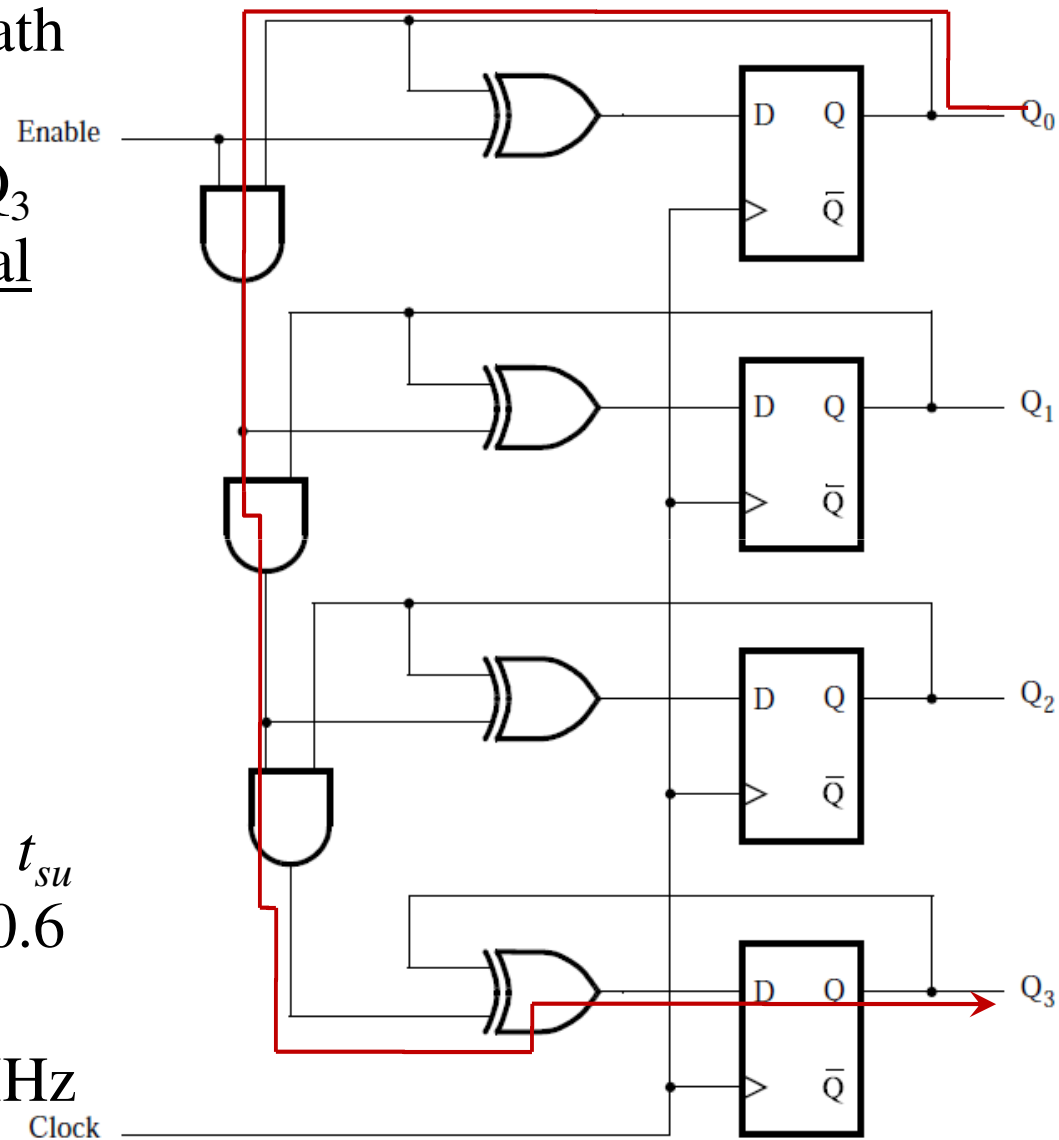
$$\therefore f_{max} = 1/6.4\text{ns} = 156.25 \text{ MHz}$$



SUMMARY

- In a sequential circuit, outputs depends on inputs and previous inputs
 - Previous inputs are stored as binary information into memory
 - The stored information at any time defines a state
 - Similarly, next state depends on inputs and present state
- Two types of sequential circuits: Synchronous and Asynchronous
- Two types of Memory elements: Latches and Flip-Flops.
- Flip-flops are built with latches
- A flip-flop is described using characteristic table/equation
- Flips-flops can have direct asynchronous inputs