 


Logic Gates

- Inverter
- AND Gate
- OR Gate
- Exclusive-OR Gate
- NAND Gate
- NOR Gate
- Exclusive-NOR Gate
- Transmission Gate
- IC

The Inverter




A	X
0	1
1	0

Truth table

0 = LOW
1 = HIGH

$$X = \overline{A}$$


Boolean expression

 


Pulsed waveforms

The output of an inverter is always the complement (opposite) of the input.

The AND Gate

 

Distinctive shape symbol

 

Rectangular outline symbol


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

0 = LOW
1 = HIGH

$$X = AB$$


Boolean expression

 


Pulsed waveforms

The output of an AND gate is HIGH only when all inputs are HIGH.

The AND Gate

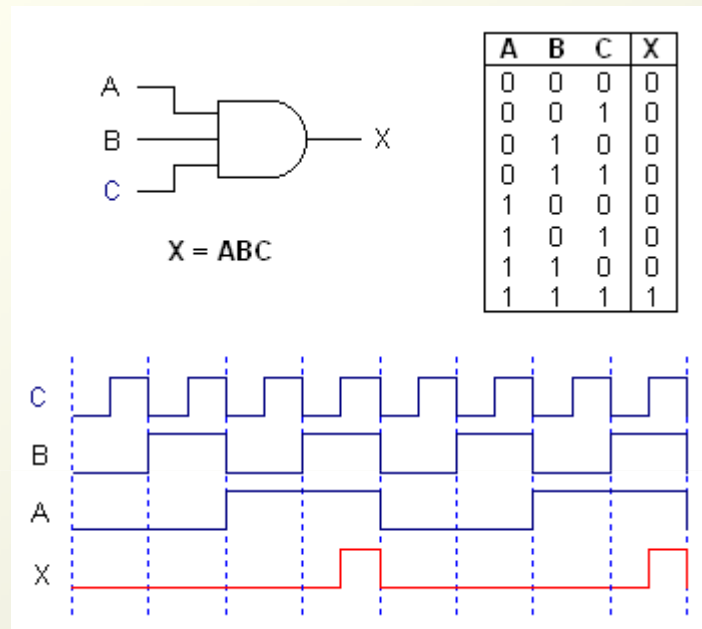


3-Input AND Gate

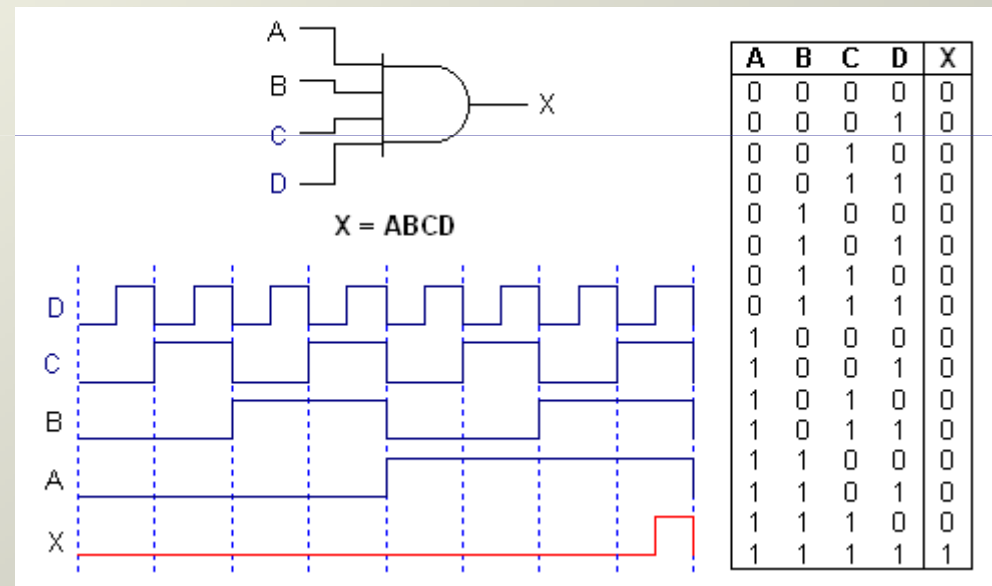


4-Input AND Gate

AND Gate Applications

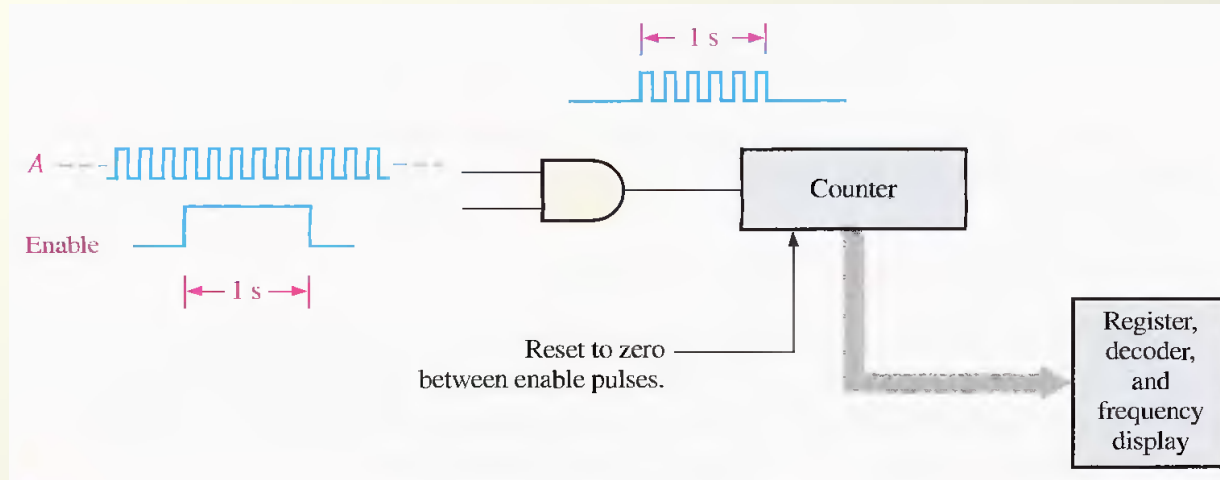


Frequency Counter


Seat Belt Alarm

 

The OR Gate

 

Distinctive shape symbol

 

Rectangular outline symbol

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


Truth table

0 = LOW

1 = HIGH

$$X = A + B$$


Boolean expression

 


Pulsed waveforms

**The output of an OR gate is HIGH
whenever one or more inputs are HIGH**

The OR Gate

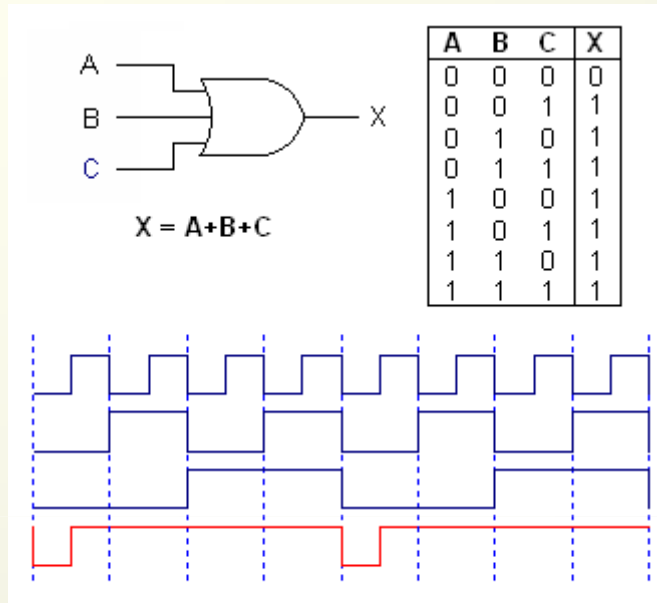


3-Input OR Gate

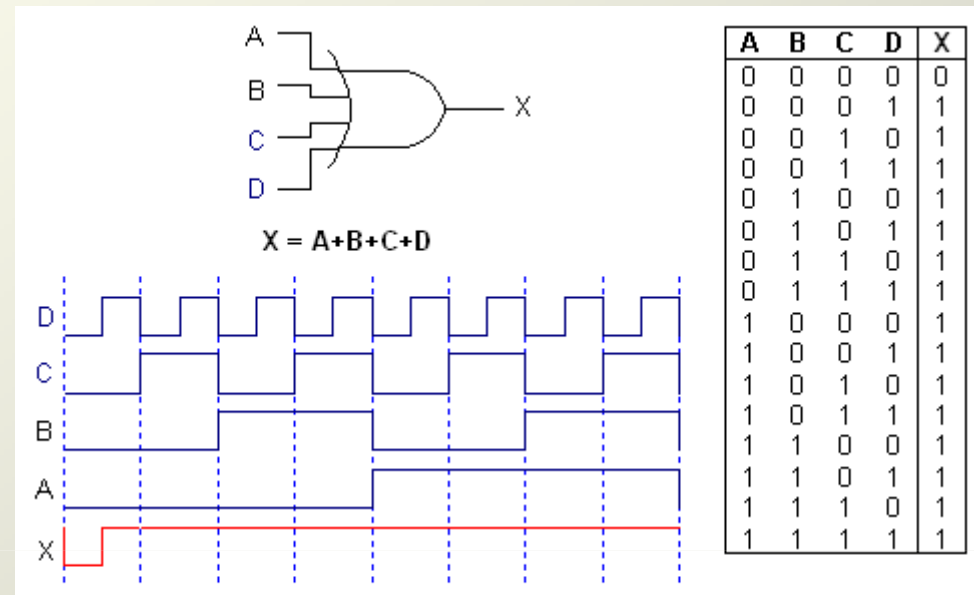


4-Input OR Gate


Intrusion Detection

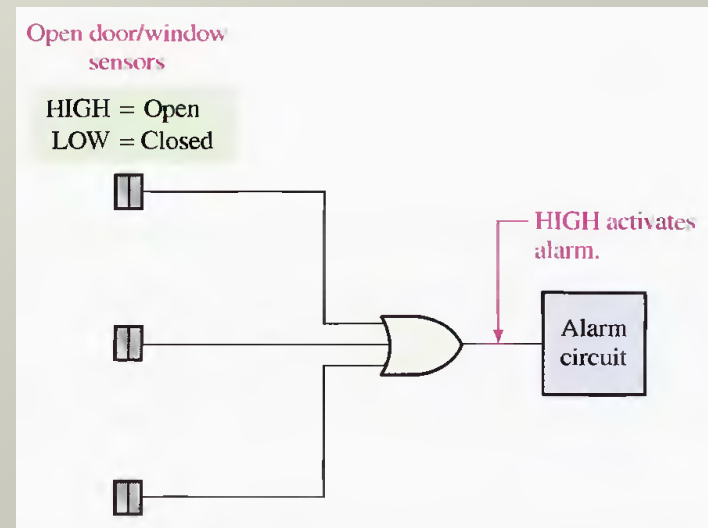


The NAND Gate

 

Distinctive shape symbol

 

Rectangular outline symbol

 


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Truth table

0 = LOW
1 = HIGH

$$X = \overline{AB}$$


Boolean expression

 


Pulsed waveforms

The output of a NAND gate is HIGH whenever one or more inputs are LOW.

The NAND Gate

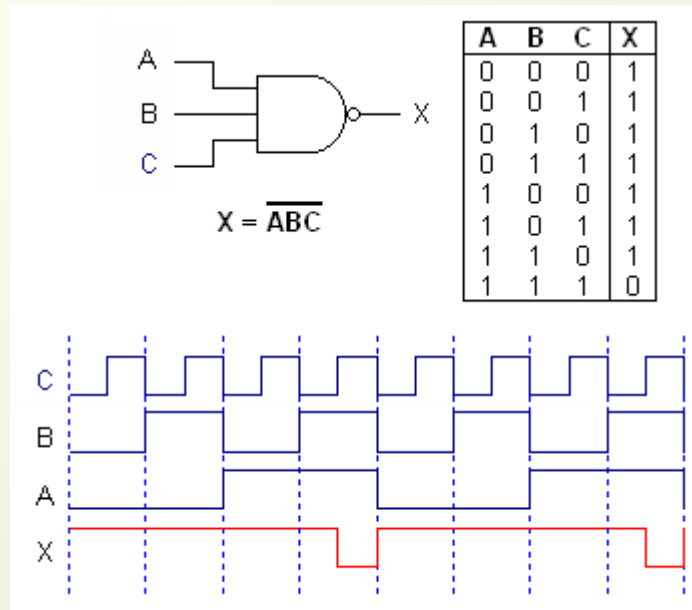

3-Input NAND Gate

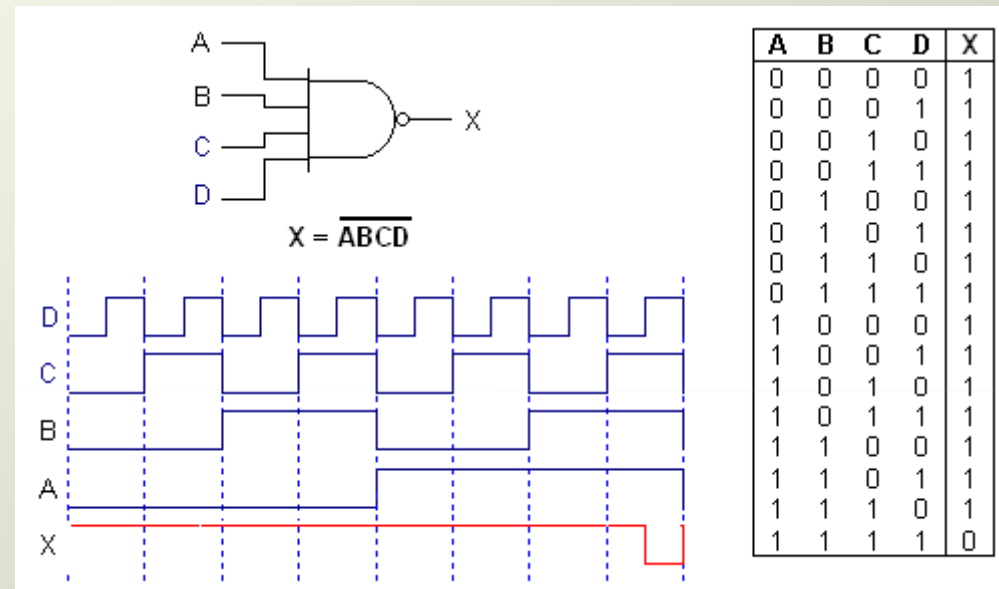


4-Input NAND Gate


The NOR Gate



Distinctive shape symbol

 

Rectangular outline symbol

 

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0


Truth table

0 = LOW

1 = HIGH

$$X = \overline{A + B}$$


Boolean expression

 


Pulsed waveforms

The output of a NOR gate is LOW whenever one or more inputs are HIGH.

The NOR Gate



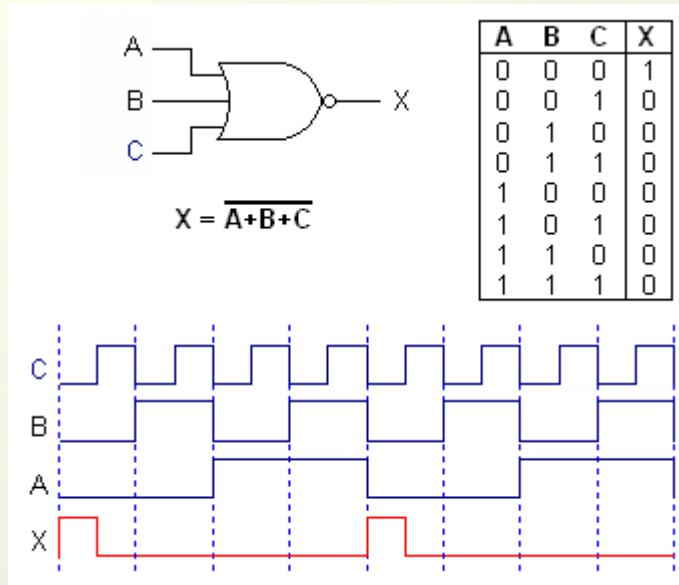


3-Input NOR Gate

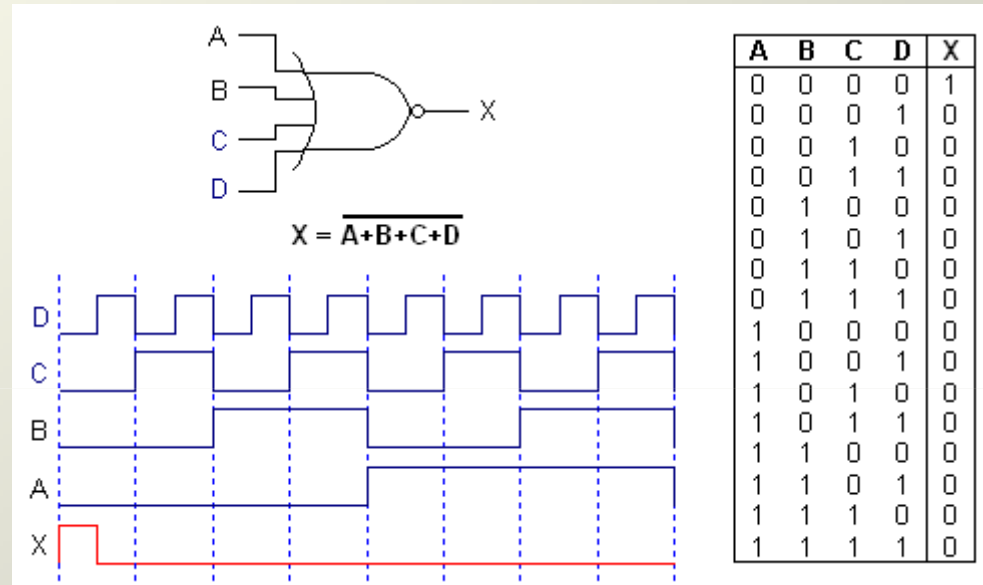


4-Input NOR Gate


NAND & NOR Gates Applications

   

Exclusive-OR Gate

 

Distinctive shape symbol

 

Rectangular outline symbol


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

0 = LOW
1 = HIGH

$$X = A \oplus B$$


Boolean expression

 


Pulsed waveforms

The output of an XOR gate is HIGH whenever the two inputs are different.

Exclusive-NOR Gate

 

Distinctive shape symbol

 

Rectangular outline symbol


A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

Truth table

0 = LOW
1 = HIGH

$$X = \overline{A \oplus B}$$

Boolean expression

 


Pulsed waveforms


The output of an XNOR gate is HIGH whenever the two inputs are identical.

Transmission Gates

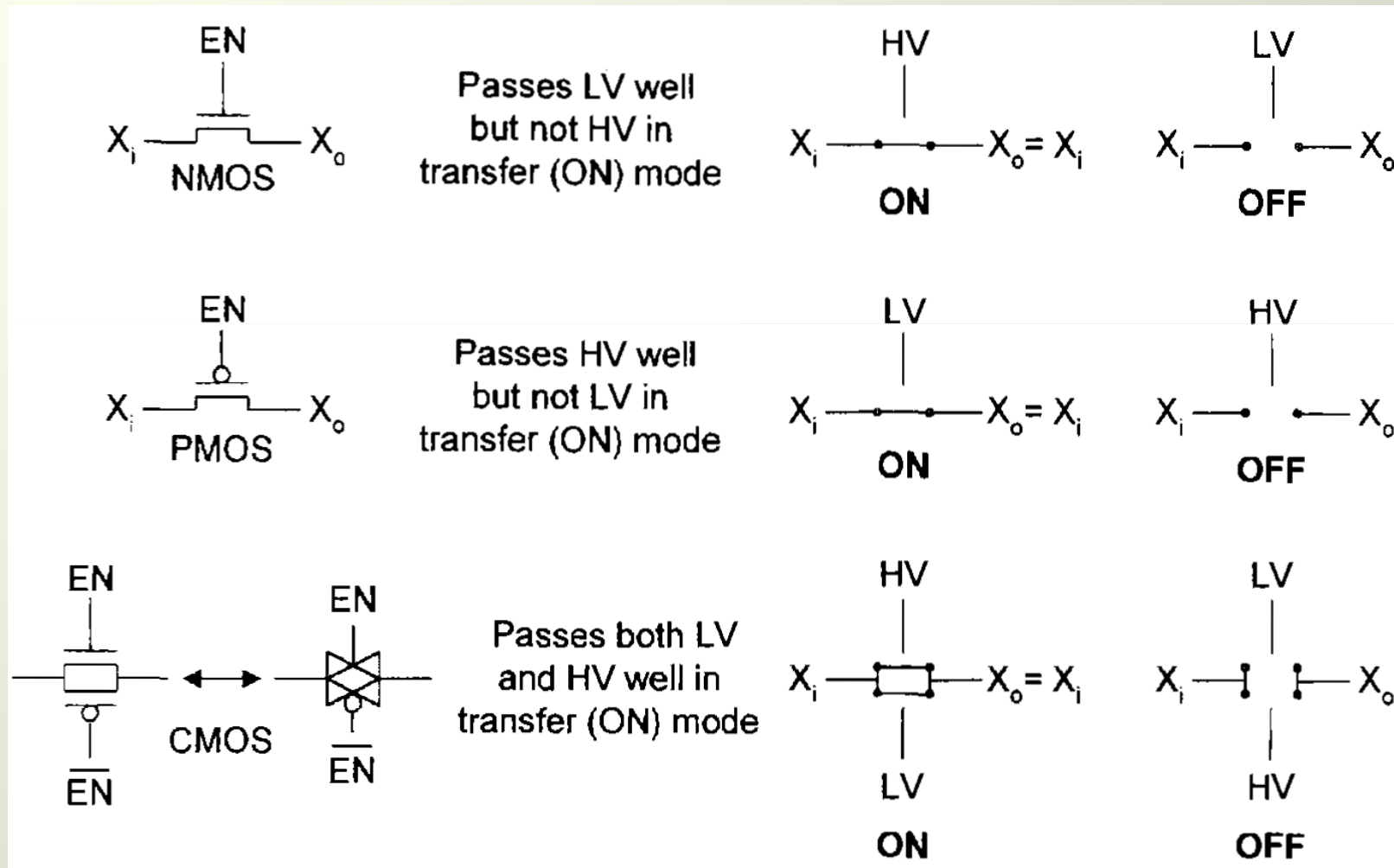- NMOS passes 0 well, but not 1; PMOS does the opposite.
- *Transmission gates* pass both 0 and 1 well




Transmission Gates

 


(a) Circuit

s	f
0	Z
1	x

(b) Truth table

 


(c) Equivalent circuit

 

 
(d) Graphical symbol

Noninverting Buffer


The buffer is a single-input device which has a gain of 1, mirroring the input at the output. It has value for impedance matching (high-to-low) and for isolation of the input and output. Typically, it is used to deliver higher power to drive a large capacitive load.



*Brown's fundamentals of digital logic

 


(a) Implementation of a buffer

 


(b) Graphical symbol

Tri-state Buffer

 


Symbol

 


Equivalent Circuit

e	x	f
0	0	Z
0	1	Z
1	0	0
1	1	1

Truth Table

 

Implementation

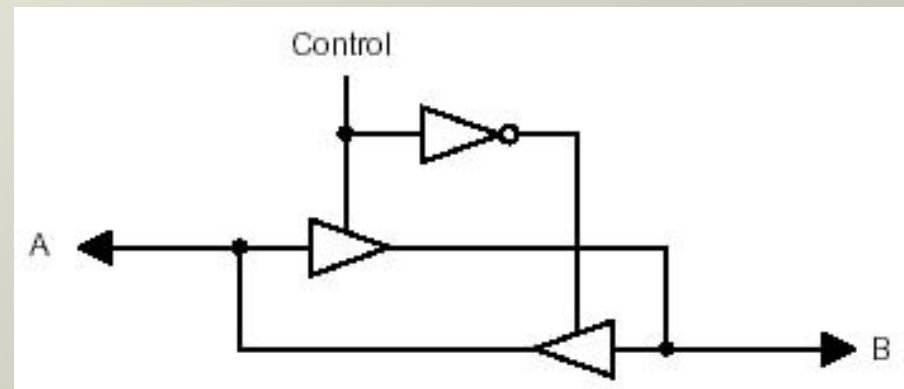

Application Example


Types of ICs

Design Style




- ASSP
- ASIC

Use

 


Cell based

 


Gate Array

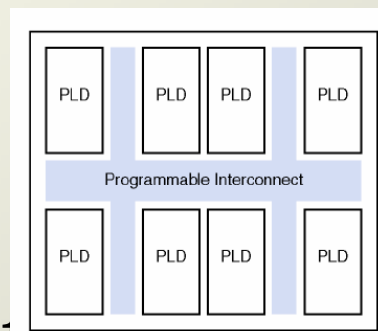- Full-custom
- Semi-custom
 - Cell Based
 - Gate Arrays
- Programmable
 - CPLD and FPGA




CPLD

 

FPGA





Programmable Logic Device (PLD)

- Programmable AND array

 



Programmable link technology

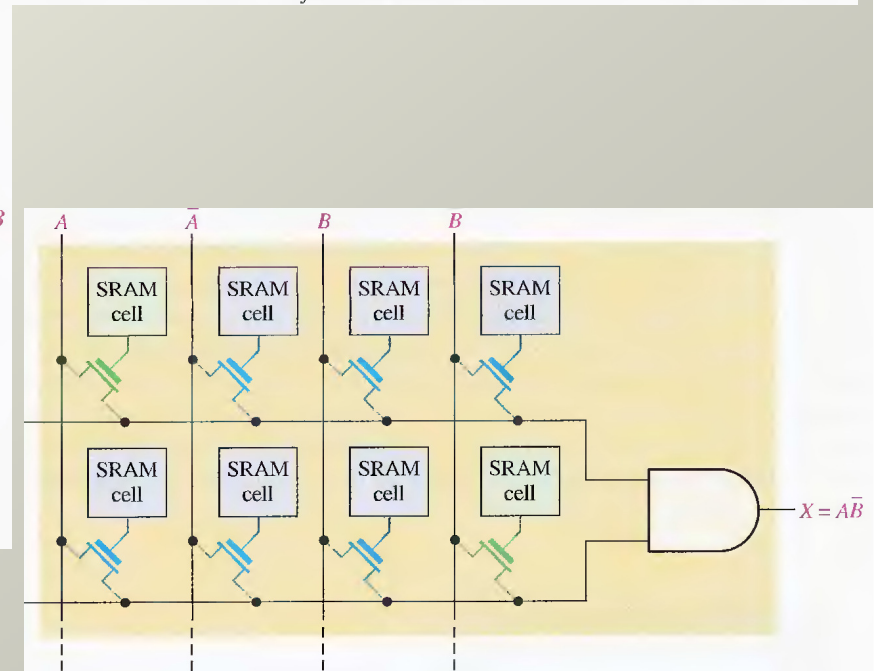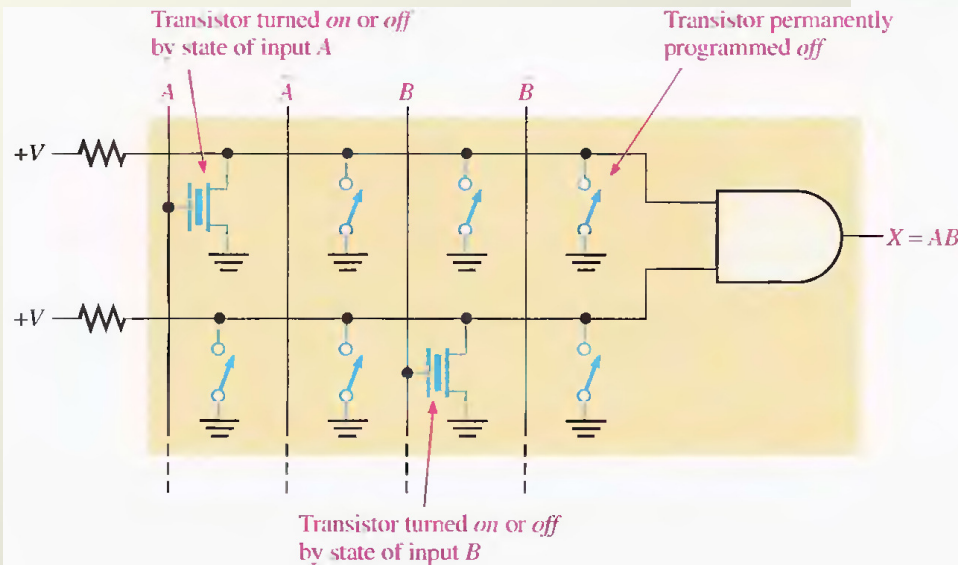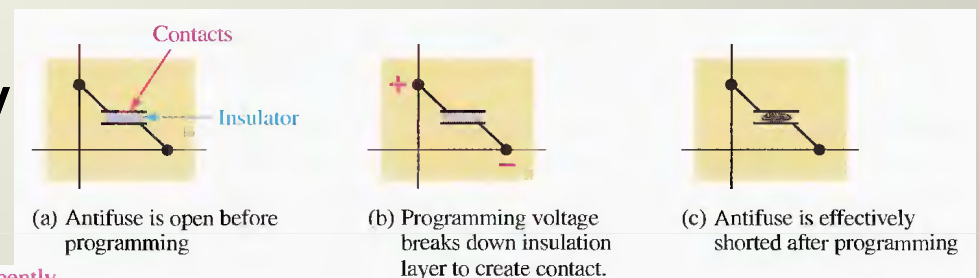 - Fuse technology
- Anti-fuse technology
- EPROM technology
- EEPROM technology
- SRAM technology





Device programming

  - Design entry
 - Text entry
 - Graphic (schematic) entry



Programmable Logic

 
 
- In-system programming (ISP)
 - Joint Test Action Group (JTAG)
 - Embedded processor




Fixed-Function Logic

- CMOS
- TTL (Transistor-Transistor Logic)

DIP (Dual In Line)




 
 


SOIC (Small Outline IC)

 


Copyright ©2006 by Pearson Education, Inc.
Upper Saddle River, New Jersey 07458
All rights reserved.

IC Gates

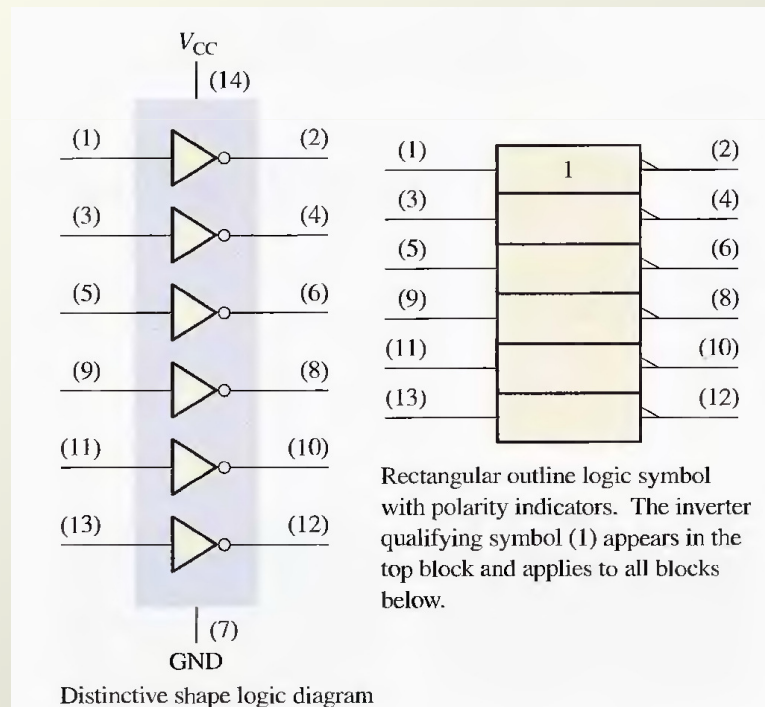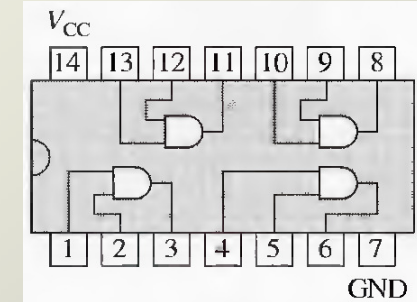   

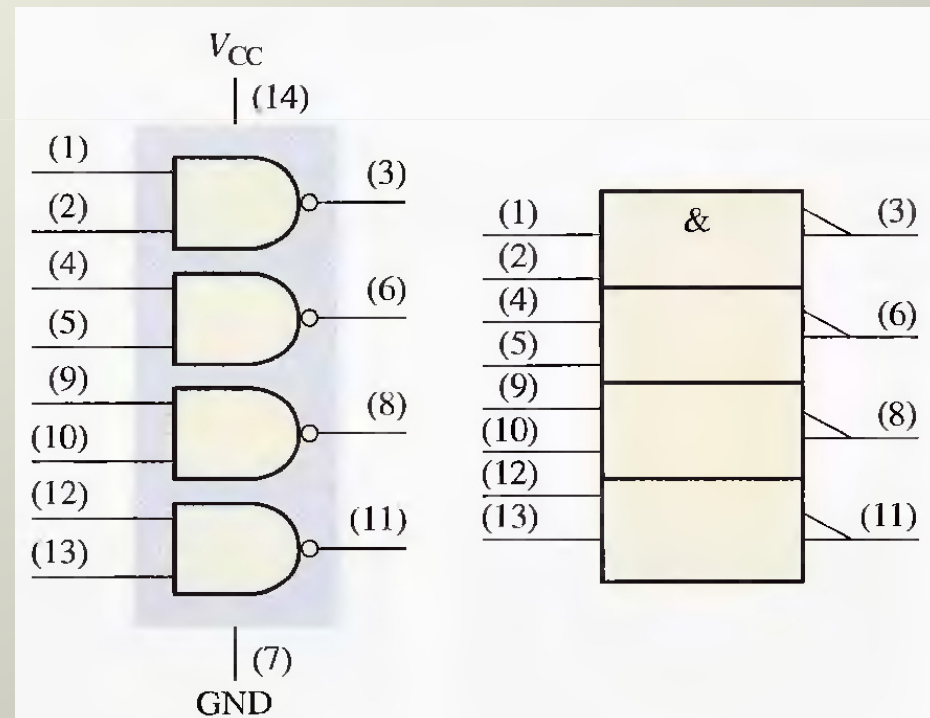
Rectangular outline logic symbol with polarity indicators. The inverter qualifying symbol (1) appears in the top block and applies to all blocks below.




Chip Integration Level

- **SSI** = small-scale integration
(up to 10 gates)
- **MSI** = medium-scale integration
(up to 1000 gates)
- **LSI** = large-scale integration
(up to 10000 gates)
- **VLSI** = very large-scale integration
(over 10000 gates)


Design Abstraction Levels

 


Design Abstraction Levels

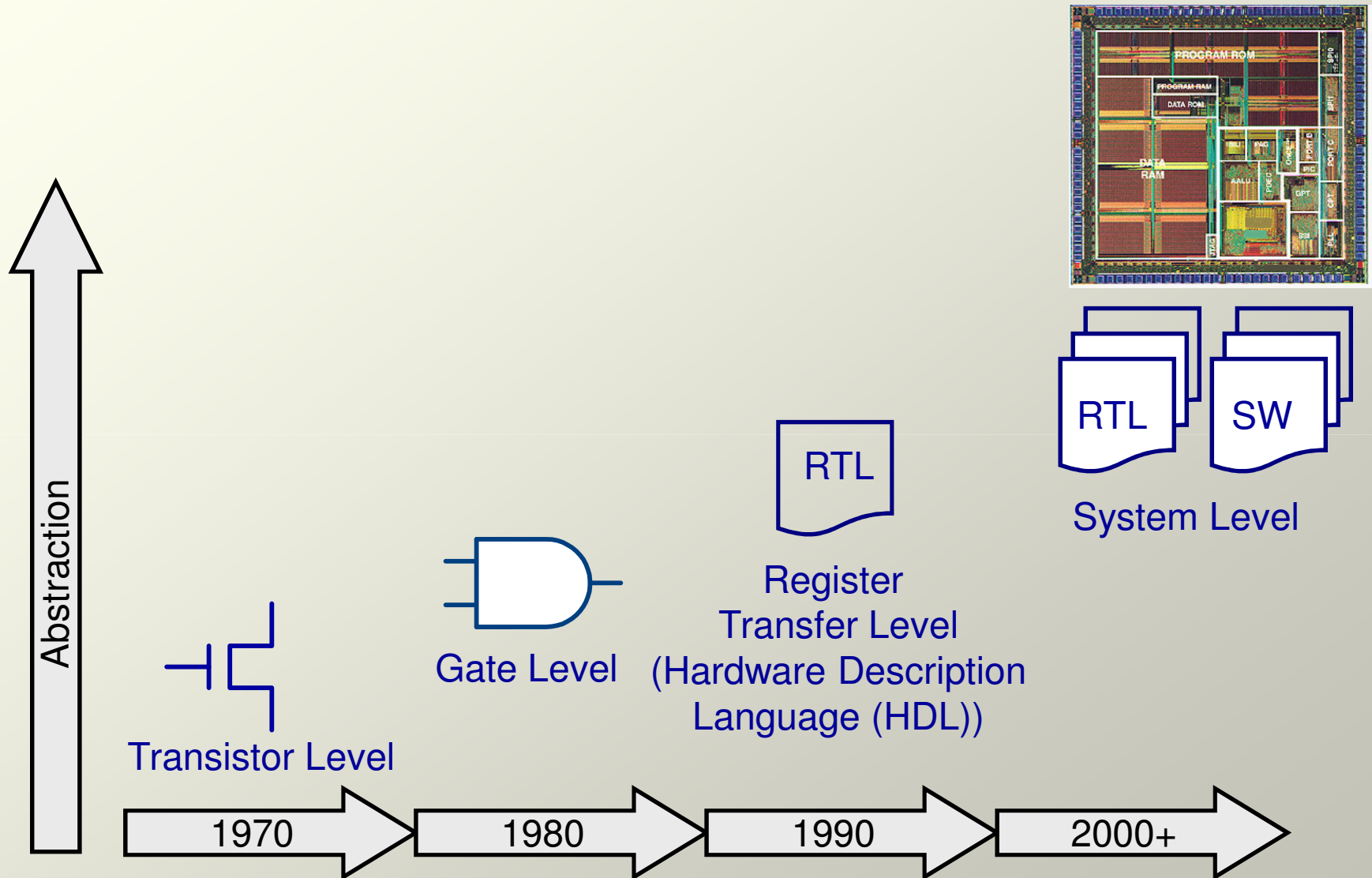

A mux at different levels of abstraction

 

symbol for multiplexer function

 

switch model for multiplexer


multiplexer function logic equation

$$Z = A \cdot S' + B \cdot S$$

multiplexer truth table


S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

gate-level logic diagram for mux

 

A mux at different levels of abstraction

multiplexer using an MSI building block

 

*multiplexer desing using
MOS transistors*

