

SYNCHRONOUS SEQUENTIAL CIRCUITS

☐ Part I: Analysis


- ☐ State Table
- ☐ State Diagram
- ☐ Finite State Machine (FSM)
- ☐ Mealy & Moore State Model

☐ Part 2: Synthesis (Design)

- ☐ General Procedure
- ☐ Write a State Diagram, State Assignment
- ☐ State Table
- ☐ State Equations
- ☐ Choice of Flip-Flop

GENERAL FORM

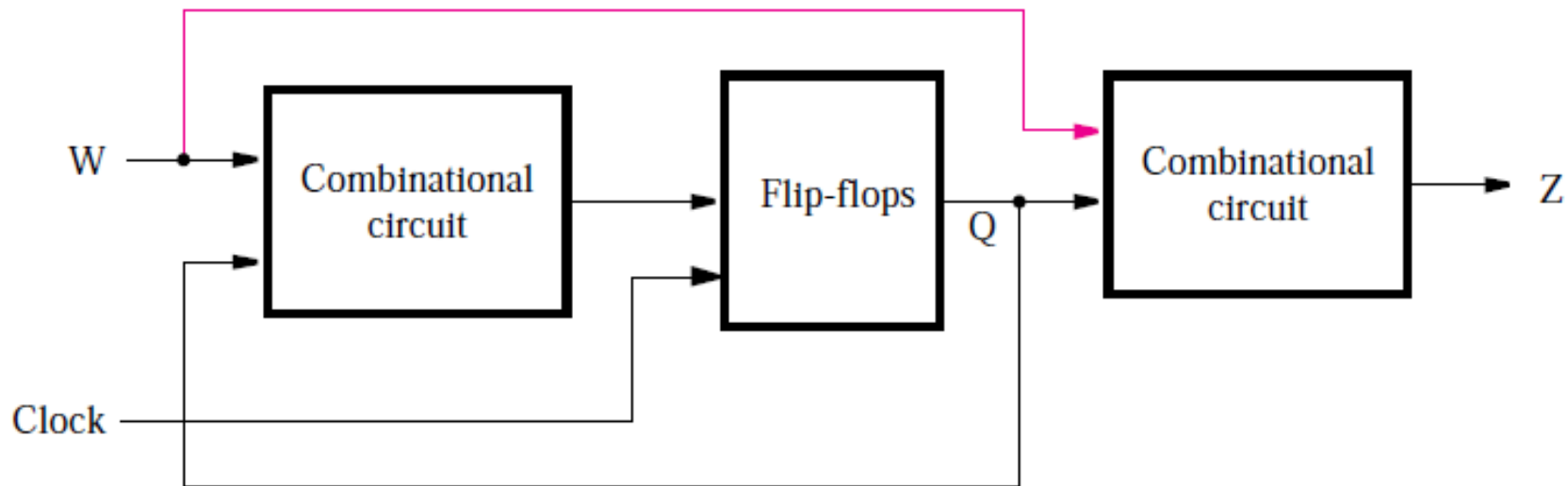- ❖ Combinational circuit for both input and output.
- ❖ Flip-flops for “memory” function
- ❖ Clock signal for “synchronization”



ANALYSIS OF SEQUENTIAL CIRCUITS

- Analysis is describing what a given circuit will do.
- The behavior of a clocked (synchronous) sequential circuit is determined from the inputs, the output, and the states of FF

❖ Steps:

- Obtain state equations
 - FF input equations
 - Output equations
- Fill the state table
 - Put all combinations of inputs and current states
 - Fill the next state and output
- Draw the state diagram

ANALYSIS OF COMBINATIONAL VS SEQUENTIAL CIRCUITS

◦ Combinational :

- Boolean Equations
- Truth Table

- Output as a function of inputs

◦ Sequential :

- ✓ State Equations
- ✓ State Table
- ✓ State Diagram

- ✓ Output as a function of input and current state
- ✓ Next state as a function of inputs and current state.

STATE EQUATIONS

○ A **state equation** is a Boolean expression which specifies the next state and output as a function of the present state and inputs.

○ **Example:**


- The shown circuit has two D-FFs (A,B), an input x and output y.
- The D input of a FF determines the next state

$$A(t+1) = A(t)x + B(t)x = Ax + Bx$$

$$B(t+1) = A'(t)x = A'x$$

- Output:

$$y = (A+B)x'$$

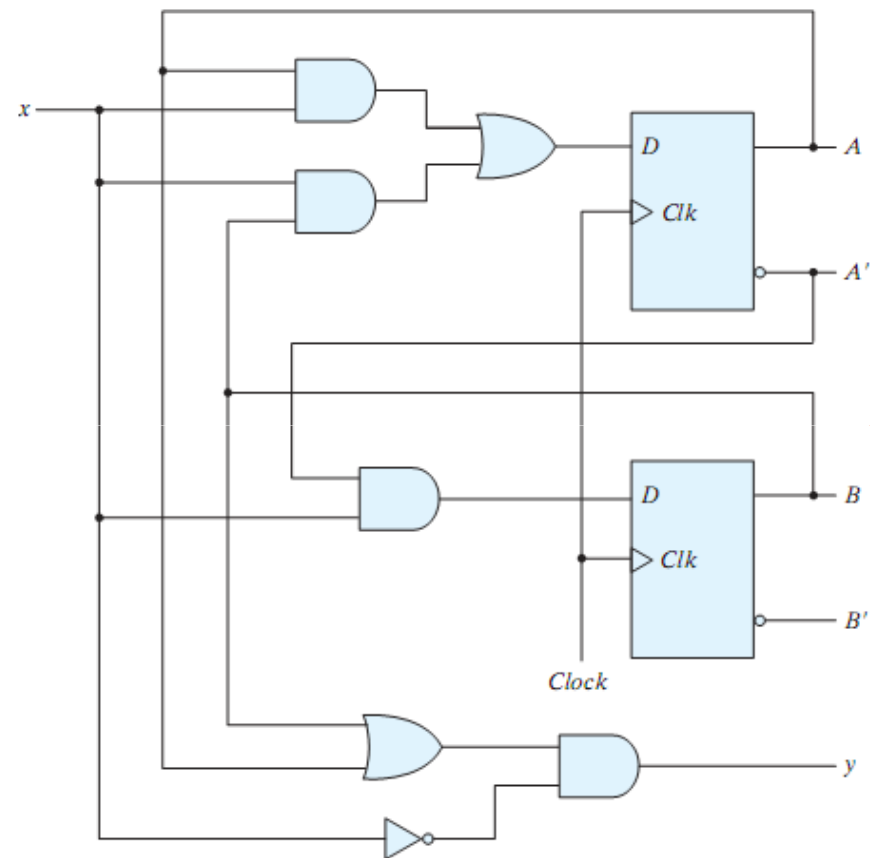


STATE TABLE

- A **state table** is a table enumerating all present states, inputs, next states and outputs.
- Present state, inputs: list all combinations
- Next states, outputs: derived from state equations

4 sections

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

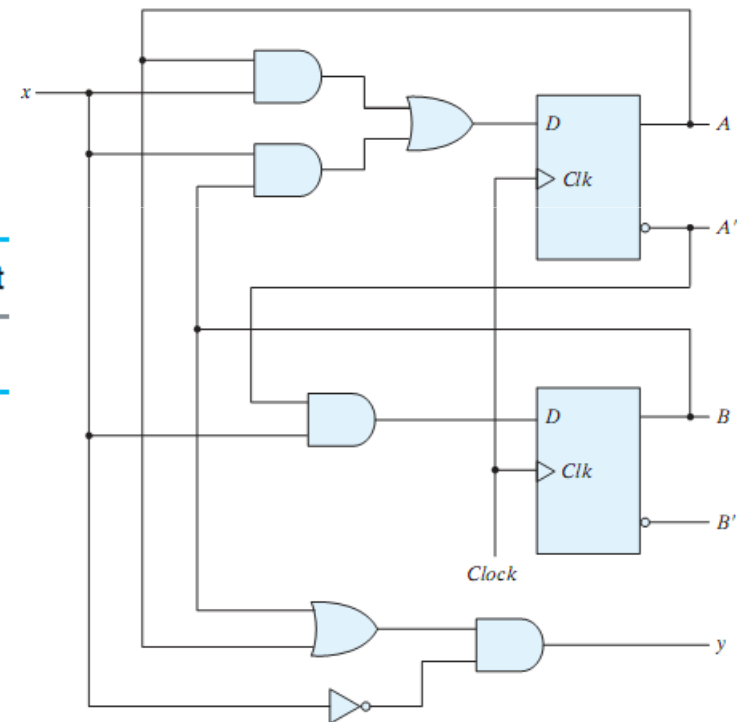


STATE TABLE

○ A **state table** is a table enumerating all present states, inputs, next states and outputs.

- Present state, inputs: list all combinations
- Next states, outputs: derived from state equations


2-D Form

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

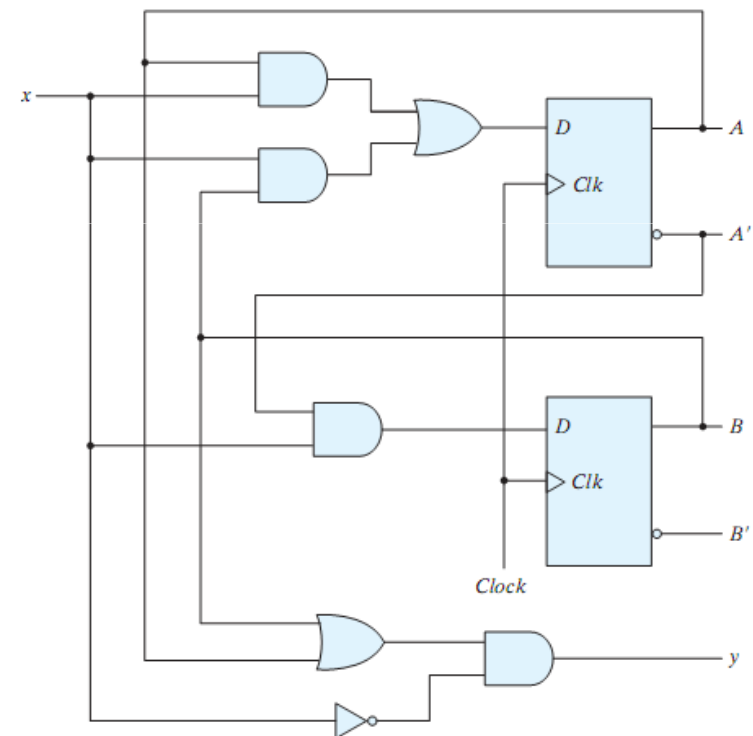

STATE DIAGRAM

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 


- The **state diagram** is a graphical representation of a state table (provides same information)
- Circles are states (FFs), Arrows are transitions between states
- Labels of arrows represent inputs and outputs
- State diagrams are used to represent “**finite state machine (FSM)**”, which is a mathematical model of computation used to design both sequential circuits and computer programs.
- As the name implies, FSM consists of **finite** number of states.

MEALY VS MOORE FINITE STATE MACHINE (FSM)


Mealy FSM:

 - Output depends on current state and input
- Output is not synchronized with the clock




Moore FSM:

- Output depends on current state only

 

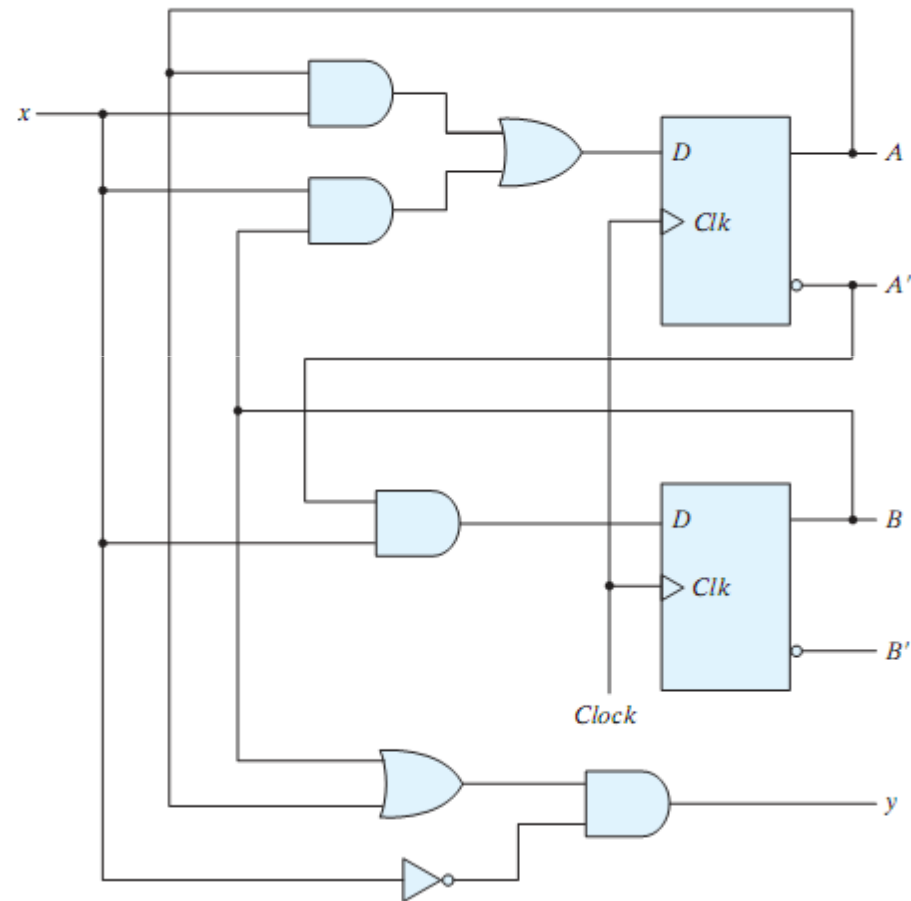
EXAMPLE 1

- ❖ Analyze this circuit?
- Is this a sequential circuit? Why?
- How many inputs?
- How many outputs?
- How many states?
- What type of memory?




EXAMPLE 1 (CONT.)

D Flip Flop (review)

 

(a) Positive-edge

 

(a) Negative-edge

Characteristic Tables and Equations

$Q(t)$	D	$Q(t+1)$
0	0	0
0	1	1
1	0	0
1	1	1

D	$Q(t+1)$
0	0
1	1

$$Q(t+1) = D$$

EXAMPLE 1 (CONT.)

❖ State equations:


$$D_A = AX + BX$$

$$D_B = A'X$$

$$Y = (A + B)X'$$

❖ State table:

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

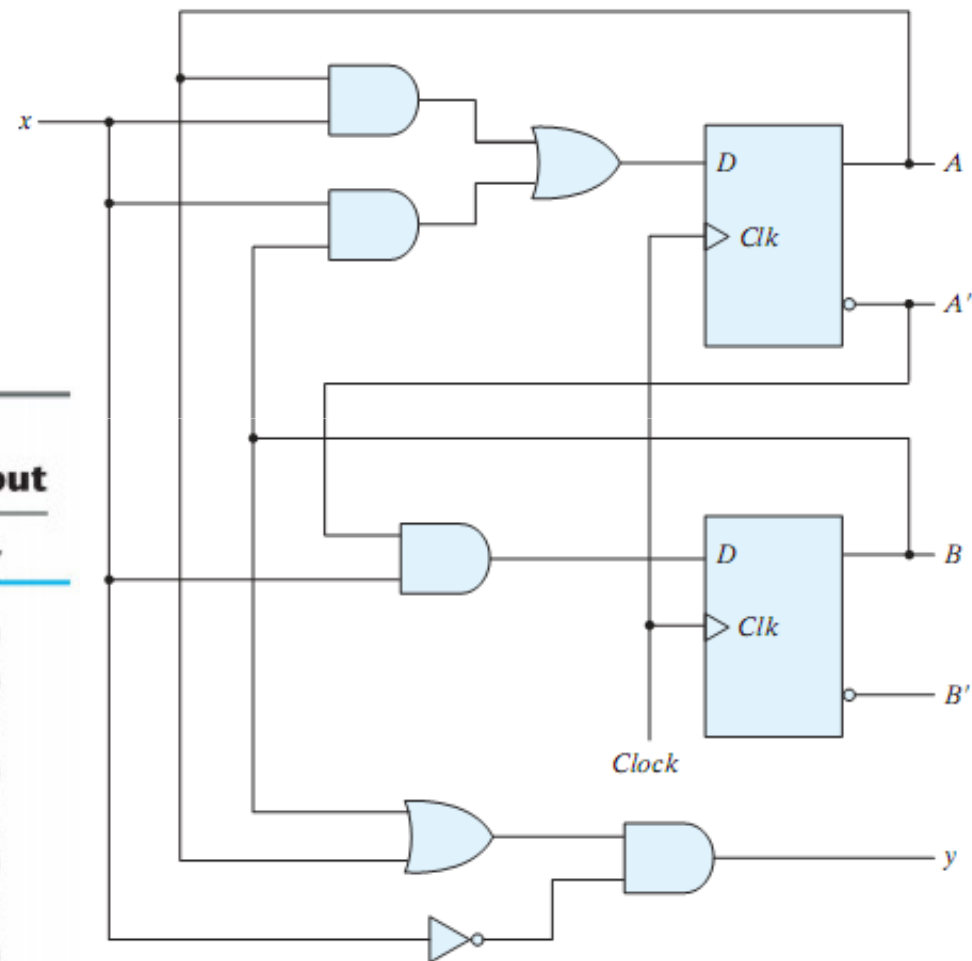

EXAMPLE 1 (CONT.)

❖ State equations:


$$D_A = AX + BX$$

$$D_B = A'X$$

$$Y = (A + B)X'$$

❖ State table (2D):

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

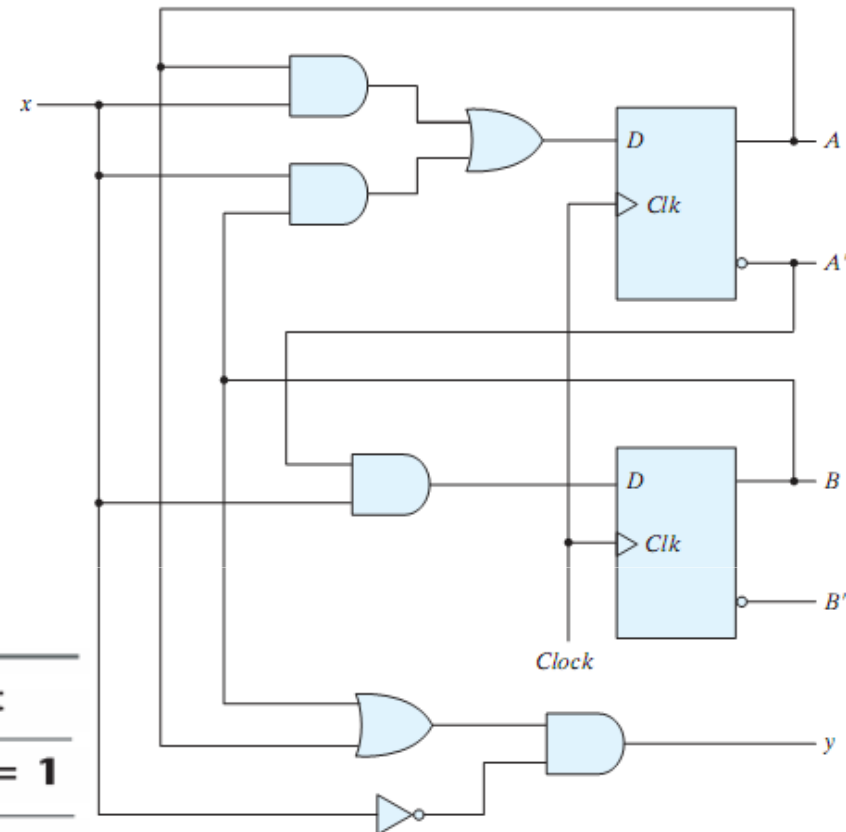

EXAMPLE 1 (CONT.)

❖ State equations:

$$D_A = AX + BX$$


$$D_B = A' X$$

$$Y = (A + B) X'$$

❖ State table:


Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State diagram:

 


Mealy-type FSM

EXAMPLE 2

 

- Analyze this circuit.
- What about the output?
- This circuit is an example of a **Moore machine** (output depends only on current state)
- **Mealy machines** is the other type (output depends on both inputs and current states)


EXAMPLE 2 (CONT.)

 

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Equation:


$$D_A = A \oplus X \oplus Y$$

 

 EXAMPLE 3


❖ Analyze this circuit?

- Is this a sequential circuit? Why?
- How many inputs?
- How many outputs?
- How many states?
- What type of memory?



EXAMPLE 3 (CONT.)

JK Flip Flop (review)

 


Characteristic Tables and Equations

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

$$Q(t+1)=Q^+ = JQ' + K'Q$$

EXAMPLE 3 (CONT.)

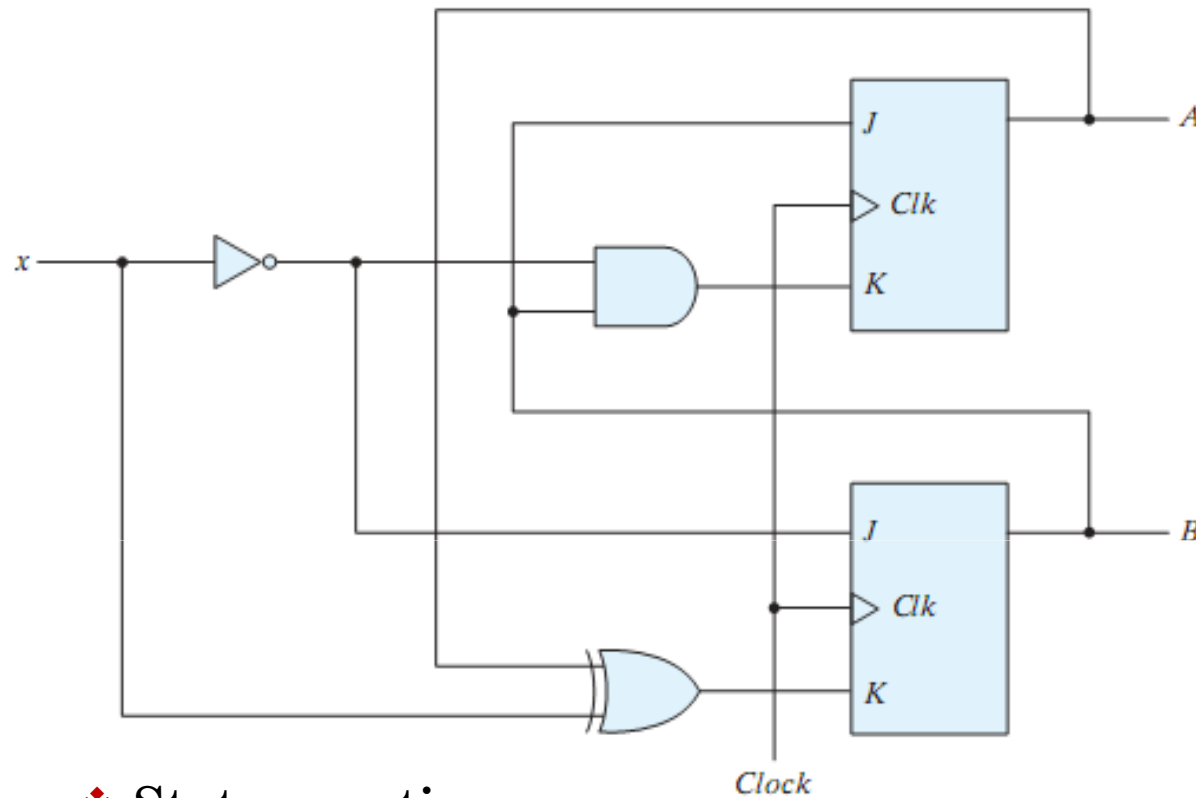

❖ **State equations:**

$$J_A = B, K_A = B X'$$

$$\mathbf{J}_B = \mathbf{X}', \mathbf{K}_B = \mathbf{A} \oplus \mathbf{X}$$


❖ **by substitution:**

$$A(t+1) = J_A A' + K_A' A = A' B + A B' + A X$$

$$\mathbf{B}(t+1) = \mathbf{J}_B^{\mathbf{X}} \mathbf{B}' + \mathbf{K}_B^{\mathbf{X}} \mathbf{B} = \mathbf{B}' \mathbf{X}' + \mathbf{A} \mathbf{B} \mathbf{X} + \mathbf{A}' \mathbf{B} \mathbf{X}'$$


EXAMPLE 3 (CONT.)

Present State		Input x	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

 

 EXAMPLE 4

- ❖ Analyze this circuit?
- Is this a sequential circuit? Why?
- How many inputs?
- How many outputs?
- How many states?
- What type of memory?



EXAMPLE 4 (CONT.)

State equations:

$$J_A = BX'$$

$$K_A = BX' + B'X$$


$$D_B = X$$

$$Y = X'AB$$

by substitution:

$$\begin{aligned} A(t+1) &= J_A A' + K_A A \\ &= A' BX' + A(B' + X)(B + X') \\ &= A' BX' + A(BX + B'X') \end{aligned}$$

$$B(t+1) = X$$

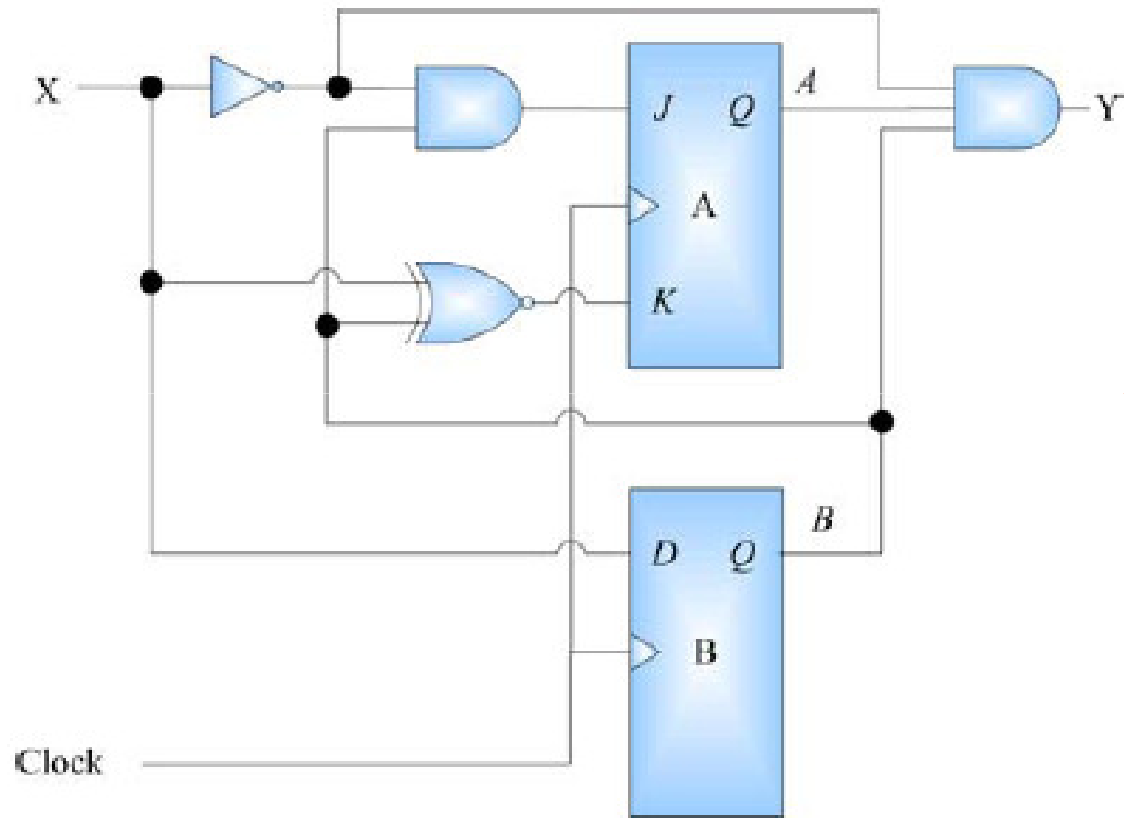

EXAMPLE 4 (CONT.)

State equations:

$$J_A = BX'$$

$$K_A = BX' + B'X$$

$$D_B = X$$

$$Y = X'AB$$

by substitution:


$$\begin{aligned} A(t+1) &= J_A A' + K_A' A \\ &= A' BX' + A(BX + B'X') \end{aligned}$$

$$B(t+1) = X$$

<i>Current State</i>		<i>Input</i>	<i>Next State</i>		<i>Output</i>
<i>A(t)</i>	<i>B(t)</i>	<i>X</i>	<i>A(t+1)</i>	<i>B(t+1)</i>	<i>Y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	0	0	1
1	1	1	1	1	0

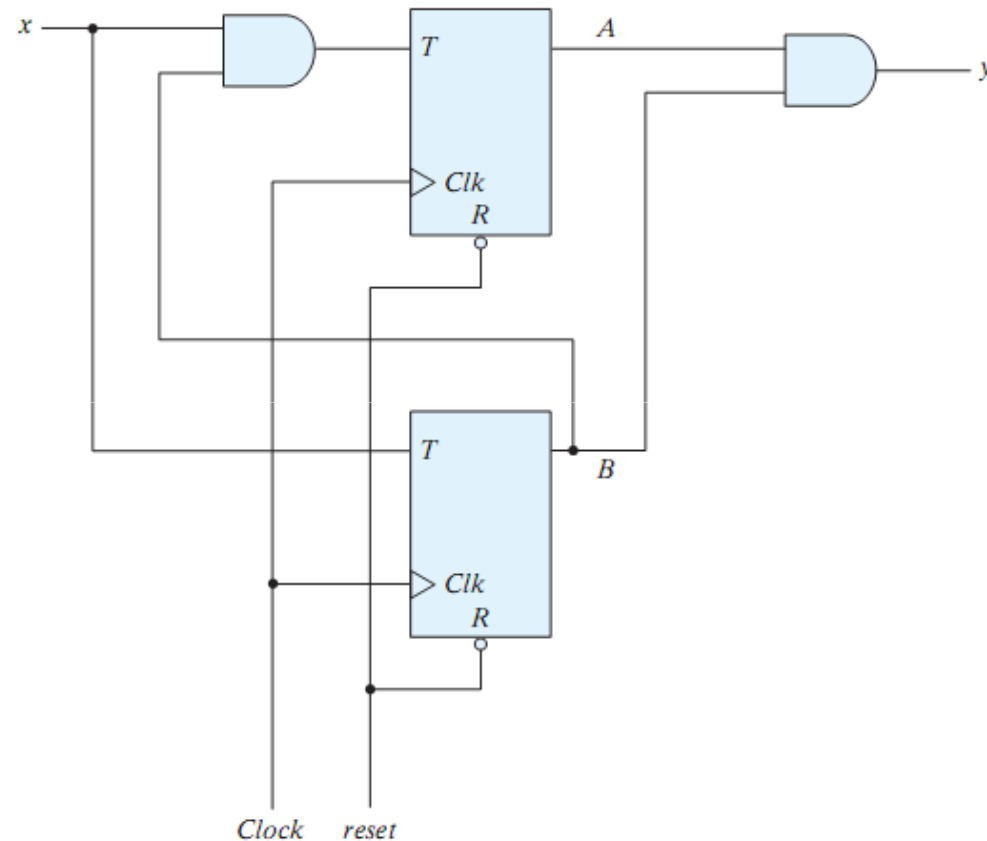
EXAMPLE 5

- ❖ Analyze this circuit?
- Is this a sequential circuit? Why?
- How many inputs?
- How many outputs?
- How many states?
- What type of memory?



EXAMPLE 5 (CONT.)

T Flip Flop (review)

 

Characteristic Tables and Equations

T	Q(t+1)
0	Q(t)
1	Q'(t)

$$Q(t+1) = TQ' + T'Q$$

EXAMPLE 5 (CONT.)

State equations:

$$T_A = BX$$

$$T_B = X$$


$$Y = AB$$

by substitution:

$$\begin{aligned} A(t+1) &= T_A A' + T_A' A \\ &= A' BX + A(B' + X') \end{aligned}$$

$$B(t+1) = B'X + BX'$$

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

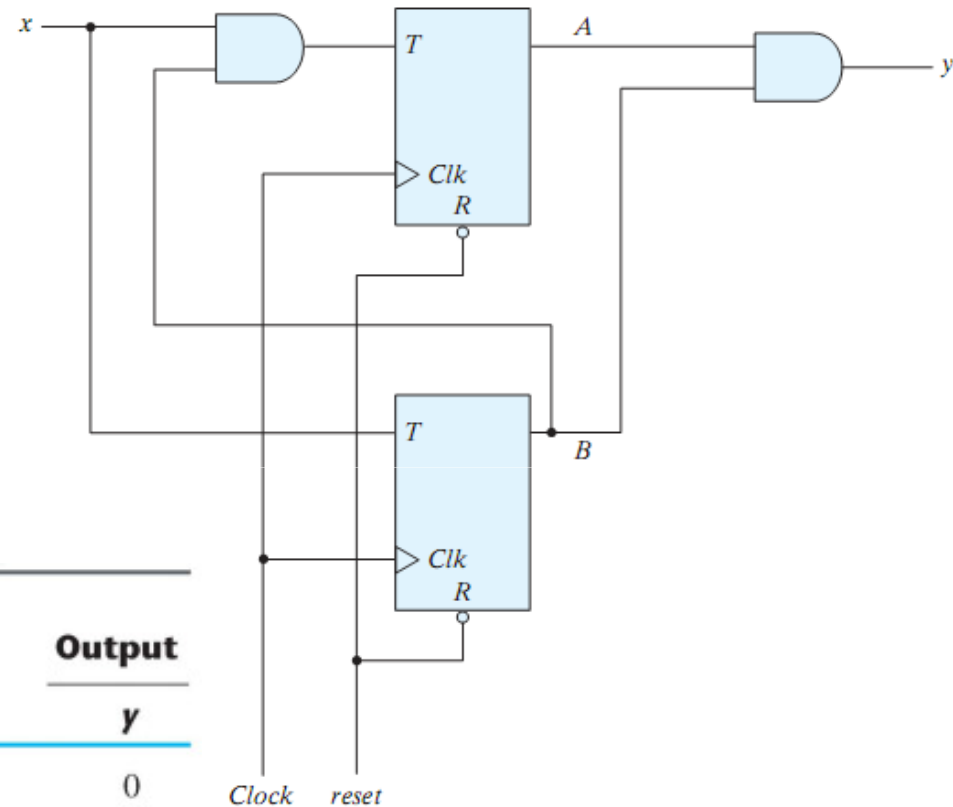

EXAMPLE 5 (CONT.)

State equations:



$$T_A = BX$$

$$T_B = X$$

$$Y = AB$$

by substitution:

$$A(t+1) = T_A A' + T_A' A$$

 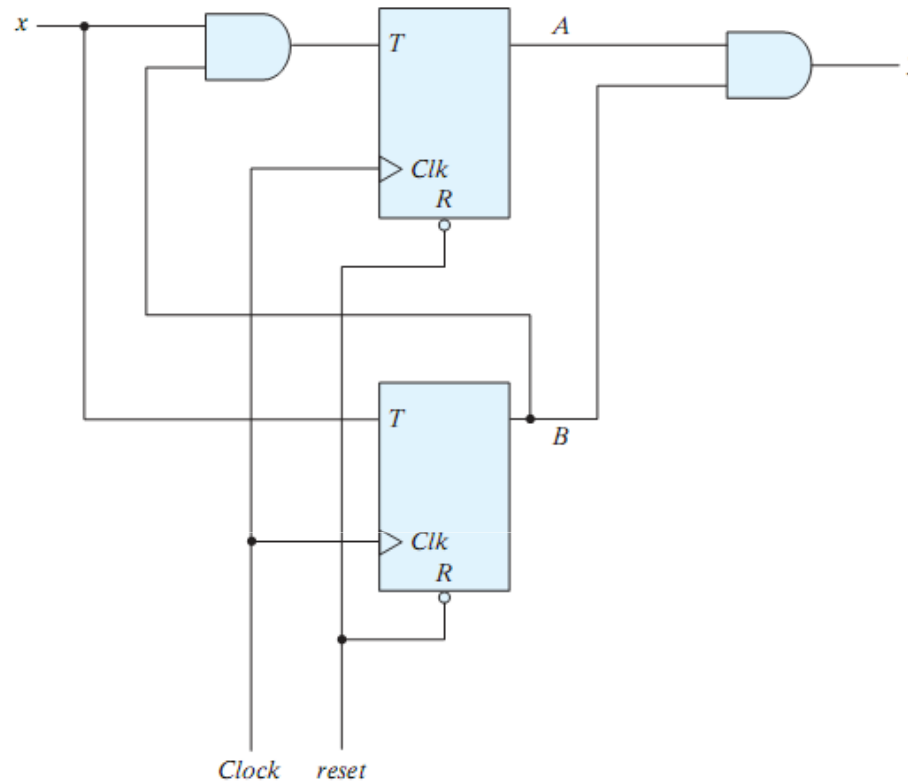

The output depends only on current state.
This is a **Moore** machine

What does this circuit do?

ANALYSIS SUMMARY

- To analyze a sequential circuit:
 - Obtain state equations
 - FF input equations
 - Output equations
 - Fill the state table
 - Put all combinations of inputs and current states
 - Fill the next state and output
 - For the next state use characteristic table/equation
 - Draw the state diagram
- Two types of synchronous sequential circuits (Mealy and Moore)

DESIGN (SYNTHESIS) OF SYNCHRONOUS SEQUENTIAL CIRCUITS

- The **design** of a clocked sequential circuit starts from a set of specifications and ends with a logic diagram (Analysis reversed!)
- Building blocks: flip-flops, combinational logic
- Need to choose type and number of flip-flops
- Need to design combinational logic together with flip-flops to produce the required behavior
- The combinational part is
 - flip-flop input equations
 - output equations

DESIGN OF SYNCHRONOUS SEQUENTIAL CIRCUITS


❖ Design Procedure:

- Obtain a state diagram from the specification
 - State reduction if necessary
- Obtain State Table
 - State Assignment
 - Choose type of flip-flops
 - Use FF's excitation table to complete the table
- Derive state equations
 - Obtain the FF input equations and the output equations
 - Use K-Maps to function simplification
- Draw the circuit diagram

STEP1: OBTAINING THE STATE DIAGRAM


- A very important step in the design procedure.
- Requires experience!

 ○ **Example:** Design a circuit that detects a sequence of three consecutive 1's in a string of bits coming through an input line (serial bit stream)



STEP2: OBTAINING THE STATE TABLE

 - Assign binary codes for the states
00, 01, 10, 11 for S_0 , S_1 , S_2 , S_3
 - We choose 2 D-FF (simplest!)
 - Next state specifies what should be the input to each FF
- **Example:** Design a circuit that detects a sequence of three consecutive 1's in a string of bits coming through an input line (serial bit stream)



State Table for Sequence Detector


Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

STEP3: OBTAINING THE STATE EQUATIONS


- Input Equations : $A(t + 1) = D_A = \sum(3,5,7) = A x + B x$,
 $B(t + 1) = D_B = \sum(1,5,7) = A x + B' x$, $y = \sum(6,7) = A B$

State Table for Sequence Detector


Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

 

$$D_A = A x + B x$$

 


$$D_B = A x + B' x$$

 

$$y = A B$$

STEP4: DRAW CIRCUITS

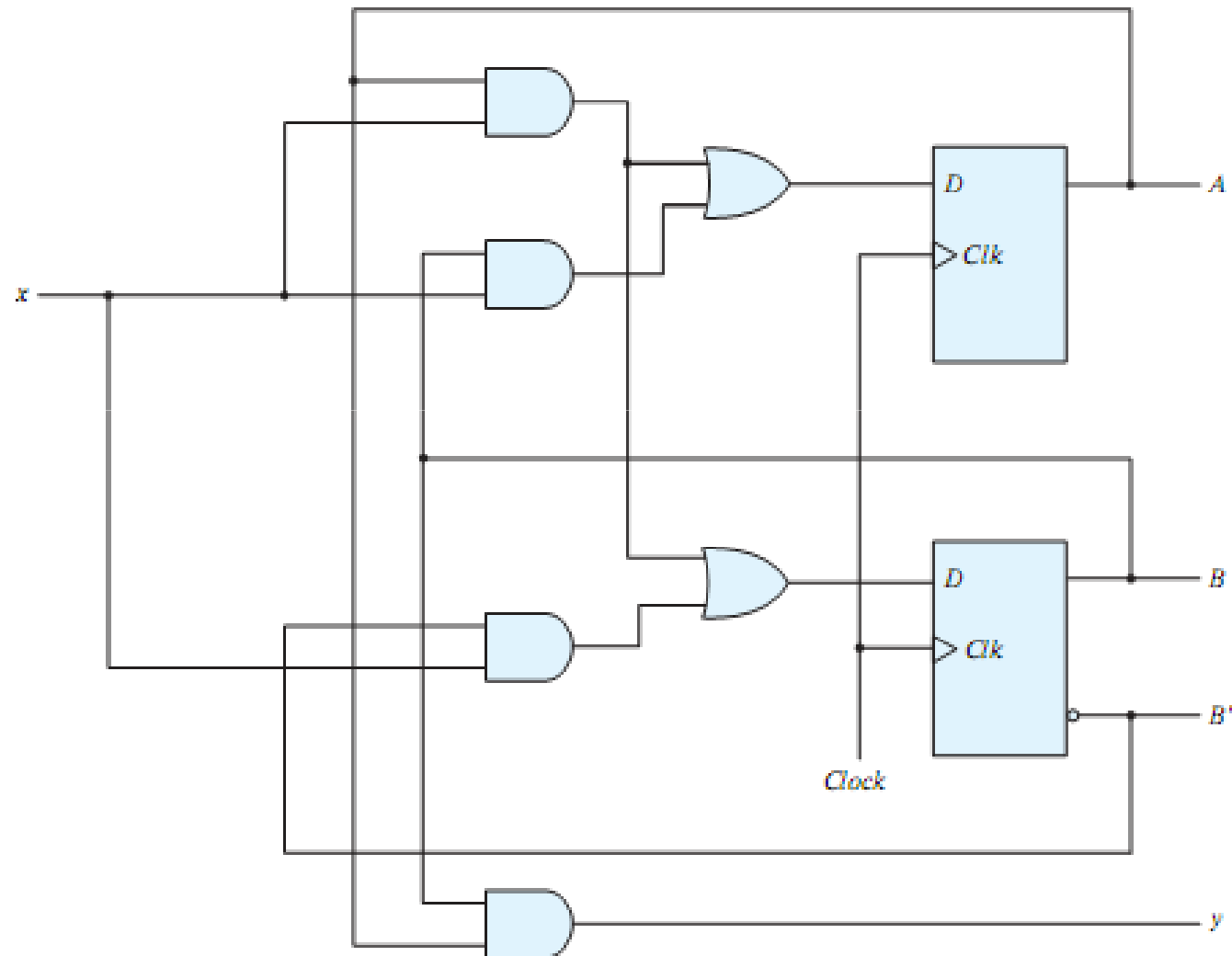

DESIGN WITH OTHER TYPES OF FF

- In designing with D-FFs, the input equations are obtained from the next state (simple!)
- It is not the case when using JK-FF and T-FF !
- **Excitation Table:** Lists the required inputs that will cause certain transitions.
 - Characteristic tables used for analysis, while excitation tables used for design

Flip-Flop Excitation Tables

$Q(t)$	$Q(t = 1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(a) JK

$$Q(t+1) = JQ' + K'Q$$

$Q(t)$	$Q(t = 1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

(b) T

$$Q(t+1) = TQ' + T'Q$$

STATE TABLE FOR JK FLIP-FLOP CASE


❖ Use the previous state assignment.

Present State		Input	Next State		Flip-Flop Input				Output
A	B	x	A	B	J _A	K _A	J _B	K _B	y
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	0	0	0	X	X	1	0
0	1	1	1	0	1	X	X	1	0
1	0	0	0	0	X	1	0	X	0
1	0	1	1	1	X	0	1	X	0
1	1	0	0	0	X	1	X	1	1
1	1	1	1	1	X	0	X	0	1

STATE EQUATIONS AND CIRCUIT

$$A(t+1) = J_A A' + K_A' A;$$

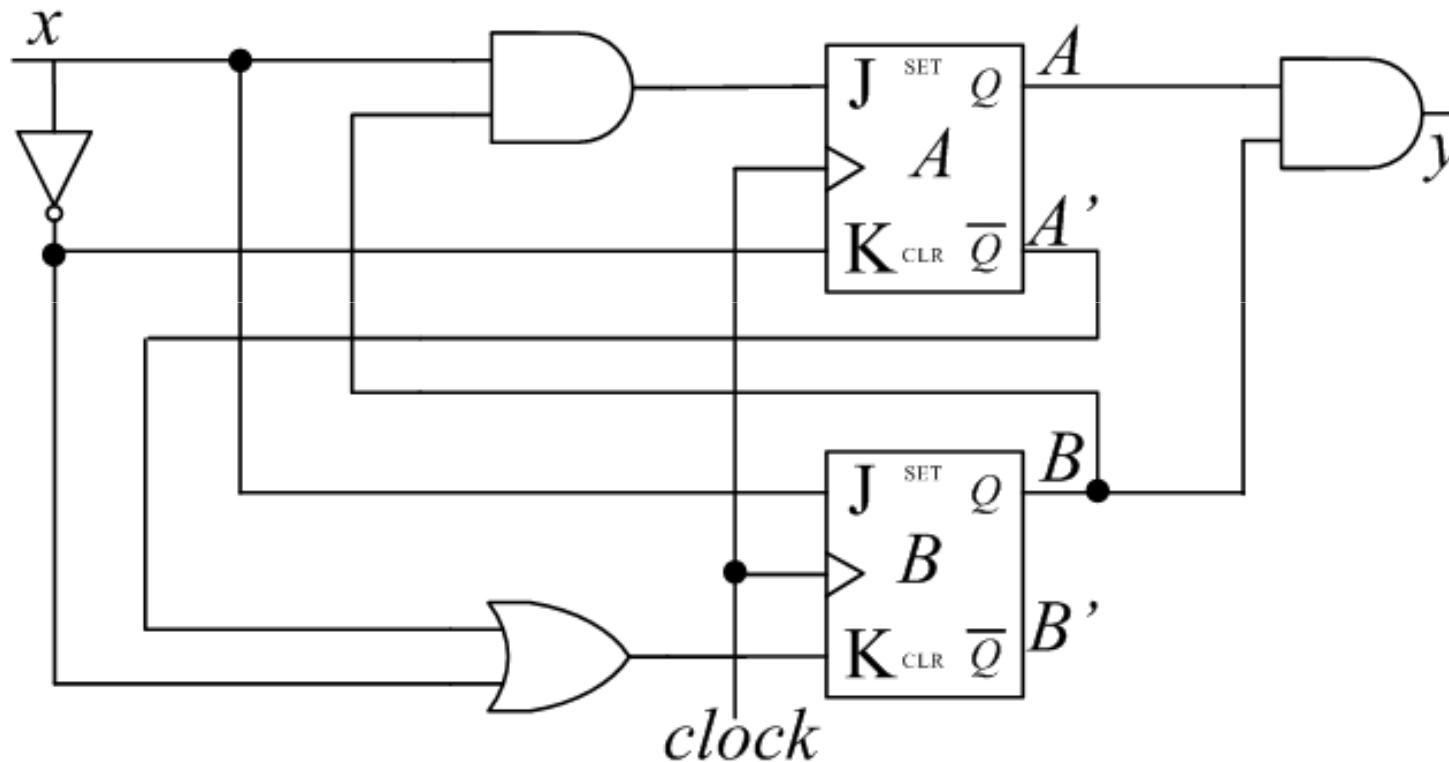
$$J_A = Bx, K_A = x', J_B = x, K_B = A' + x'; y = AB$$



Note: Fewer logic gates required.

 EXAMPLE 1

- ❖ **Problem: Design of A Sequence Recognizer**
- ❖ Design a circuit that reads as inputs continuous bits, and generates an output of '1' if the sequence (1011) is detected




Input	1	1	1	0	0	1	0	0	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	1	1
Output	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0	0	0


EXAMPLE 1 (CONT.)

❖ Step1: State Diagram


Sequence to be detected: 1011

 


(a)

 


(b)

 

(c)

 


(d)

 

(e)

EXAMPLE 1 (CONT.)

❖ Step 2: State Table

 

OR

Inputs of Combinational Circuit		Next State	Output
Present State	Input		
<i>S0</i>	0	<i>S0</i>	0
<i>S0</i>	1	<i>S1</i>	0
<i>S1</i>	0	<i>S2</i>	0
<i>S1</i>	1	<i>S1</i>	0
<i>S2</i>	0	<i>S0</i>	0
<i>S2</i>	1	<i>S3</i>	0
<i>S3</i>	0	<i>S2</i>	0
<i>S3</i>	1	<i>S1</i>	1

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
<i>S0</i>	<i>S0</i>	<i>S1</i>	0	0
<i>S1</i>	<i>S2</i>	<i>S1</i>	0	0
<i>S2</i>	<i>S0</i>	<i>S3</i>	0	0
<i>S3</i>	<i>S2</i>	<i>S1</i>	0	1

EXAMPLE 1 (CONT.)

❖ Step 2: State Table

❖ *state assignment* \Rightarrow

State	Assignment
<i>S0</i>	00
<i>S1</i>	01
<i>S2</i>	10
<i>S3</i>	11

Q: How many FF?

$\lceil \log_2(\text{no. of states}) \rceil$

Inputs of Combinational Circuit		Next State	Output
Present State	Input		
<i>S0</i>	0	<i>S0</i>	0
<i>S0</i>	1	<i>S1</i>	0
<i>S1</i>	0	<i>S2</i>	0
<i>S1</i>	1	<i>S1</i>	0
<i>S2</i>	0	<i>S0</i>	0
<i>S2</i>	1	<i>S3</i>	0
<i>S3</i>	0	<i>S2</i>	0
<i>S3</i>	1	<i>S1</i>	1



Inputs of Combinational Circuit		Next State	Output
Present State	Input		
<i>A B</i>	<i>X</i>	<i>A B</i>	<i>Y</i>
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	1 0	0
0 1	1	0 1	0
1 0	0	0 0	0
1 0	1	1 1	0
1 1	0	1 0	0
1 1	1	0 1	1

EXAMPLE 1 (CONT.)

❖ Step 2: State Table

❖ *choose FF*

❖ In this example, let's use
JK-FF for A and D-FF for B

Inputs of Combinational Circuit		Next State	Output
Present State	Input		
<i>A</i> <i>B</i>	<i>X</i>	<i>A</i> <i>B</i>	<i>Y</i>
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	1 0	0
0 1	1	0 1	0
1 0	0	0 0	0
1 0	1	1 1	0
1 1	0	1 0	0
1 1	1	0 1	1

EXAMPLE 1 (CONT.)

<i>Present State</i>	<i>Input</i>	<i>Next State</i>	<i>output</i>	<i>Flip-flops Inputs</i>		
<i>A B</i>	<i>X</i>	<i>A B</i>	<i>Y</i>	<i>J_A</i>	<i>K_A</i>	<i>D_B</i>
0 0	0	0 0	0	0	X	0
0 0	1	0 1	0	0	X	1
0 1	0	1 0	0	1	X	0
0 1	1	0 1	0	0	X	1
1 0	0	0 0	0	X	1	0
1 0	1	1 1	0	X	0	1
1 1	0	1 0	0	X	0	0
1 1	1	0 1	1	X	1	1

D–FF excitation table

<i>Q(t+1)</i>	<i>D</i>	<i>Operation</i>
0	0	Reset
1	1	Set

JK–FF excitation table

<i>Q(t)</i>	<i>Q(t+1)</i>	<i>J</i>	<i>K</i>	<i>Operation</i>
0	0	0	X	No change
0	1	1	X	Set
1	0	X	1	Reset
1	1	X	0	No Change

EXAMPLE 1 (CONT.)

❖ Step 3: State Equations

❖ *use k-map*

$$J_A = BX'$$

$$K_A = BX + B'X'$$

$$D_B = X$$

$$Y = ABX'$$

	BX			
A	00	01	11	10
0				1
1	X	X	X	X

$$J_A = BX'$$

	BX			
A	00	01	11	10
0	X	X	X	X
1	1		1	

$$K_A = BX + B'X'$$

	BX			
A	00	01	11	10
0		1	1	
1		1	1	

$$D_B = X$$

	BX			
A	00	01	11	10
0				
1				1

$$Y = ABX'$$

EXAMPLE 1 (CONT.)


❖ Step 4: Draw Circuit

$$J_A = BX'$$

$$K_A = BX + B'X'$$

$$D_B = X$$

$$Y = ABX'$$

 

EXAMPLE 2

Problem: Design of A 3-bit Counter


Design a circuit that counts in binary form as follows
000, 001, 010, ... 111, 000, 001, ...



 EXAMPLE 2 (CONT.)

❖ Step1: State Diagram

- The outputs = the states
- Where is the input?
- What is the type of this sequential circuit?



EXAMPLE 2 (CONT.)

❖ Step2: State Table

❖ *We choose T-FF*

T-FF excitation table

$Q(t+1)$	T	Operation
$Q(t)$	0	No change
$\bar{Q}(t)$	1	Complement

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	1	1
1	1	1	0	0	0	1	1	1

EXAMPLE 2 (CONT.)

❖ Step3: State Equations

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5	m_7 1	m_6

$T_{A2} = A_1 A_0$

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0	m_1 1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6

$T_{A1} = A_0$

$A_2 \backslash A_1 A_0$		A_1			
		00	01	11	10
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1	m_4 1	m_5 1	m_7 1	m_6 1

$T_{A0} = 1$


EXAMPLE 2 (CONT.)

❖ Step4: Draw Circuit

$$T_{A0} = 1$$

$$T_{A1} = A_0$$

$$T_{A2} = A_1A_0$$

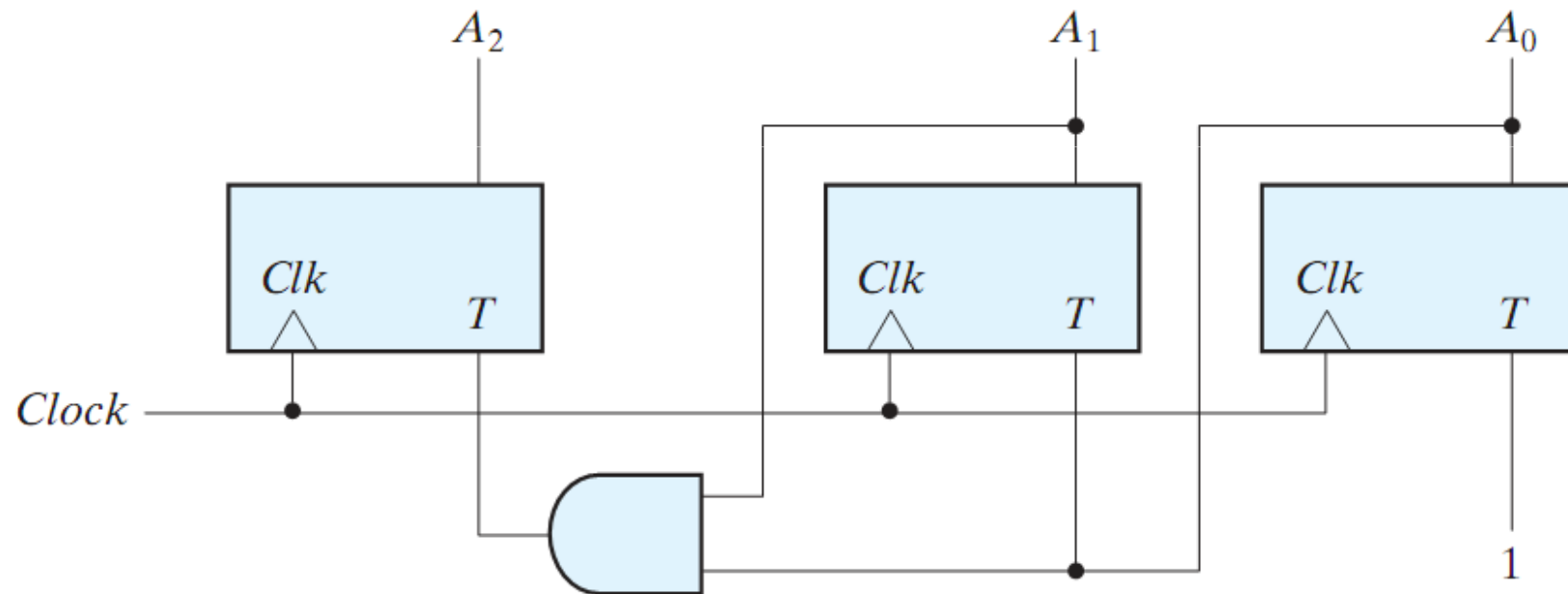


EXAMPLE 3

Problem: Design of A Sequence Recognizer

Design a **Moore** machine to detect the sequence (111). The circuit has one input (X) and one output (Z).

❖ Step1: State Diagram

Sequence to be detected: 111

 


EXAMPLE 3 (CONT.)

❖ Step2: State Table

❖ *Use binary encoding*

❖ *Use JK-FF and D-FF*

 

Inputs of Comb.Circuits			Next State	Outputs of Comb.Circuit			Output	
Present State	Input			Flip-flop Inputs				
A	B	X	A	B	J _A	K _A	D _B	Z
0	0	0	0	0	0	X	0	0
0	0	1	0	1	0	X	1	0
0	1	0	0	0	0	X	0	0
0	1	1	1	0	1	X	0	0
1	0	0	0	0	X	1	0	0
1	0	1	1	1	X	0	1	0
1	1	0	0	0	X	1	0	1
1	1	1	1	1	X	0	1	1

EXAMPLE 3 (CONT.)

❖ Step4: Draw Circuit


❖ *For step3, use k-maps as usual*

$$J_A = XB$$

$$K_A = X'$$

$$D_B = X(A+B)$$



$$Z = A.B$$

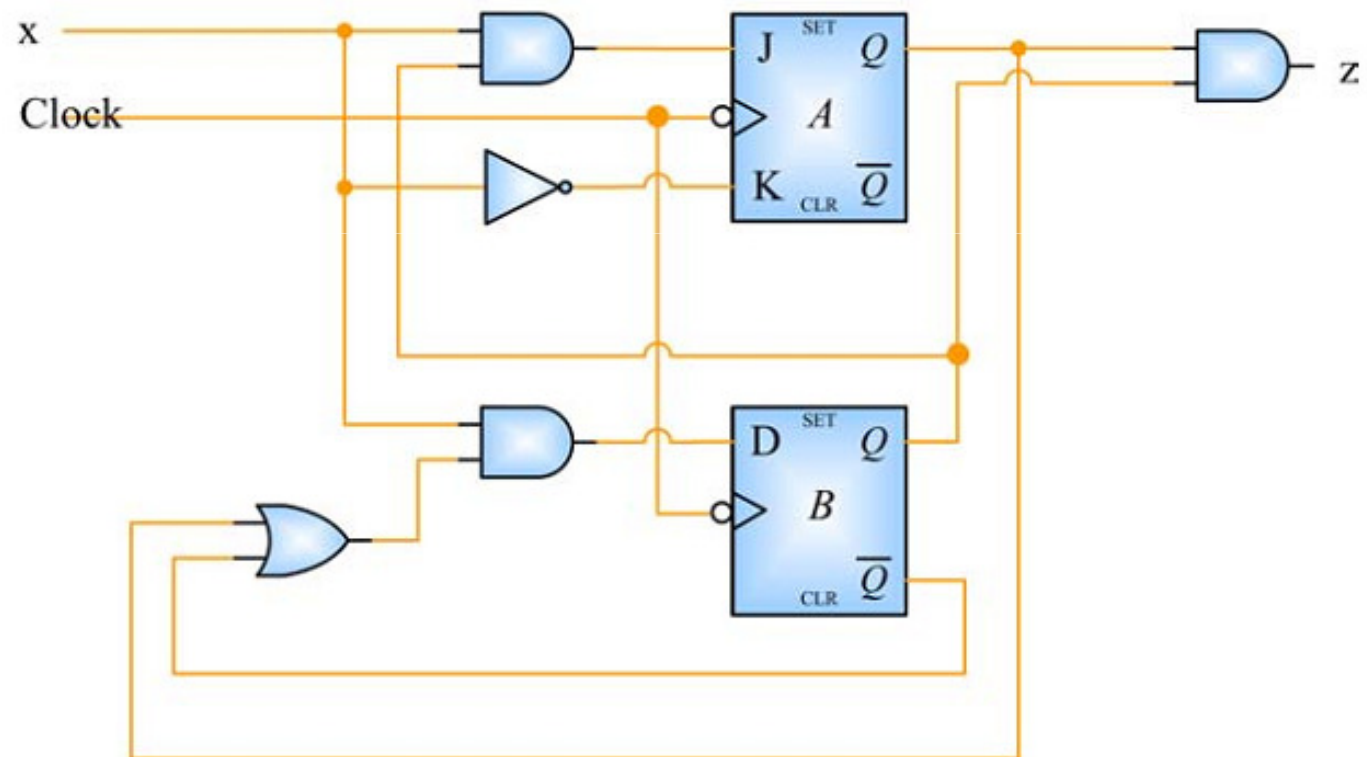

EXAMPLE 3 (CONT.)

❖ Timing Diagram (verification)

❖ *Question: Does it detect 111 ?*

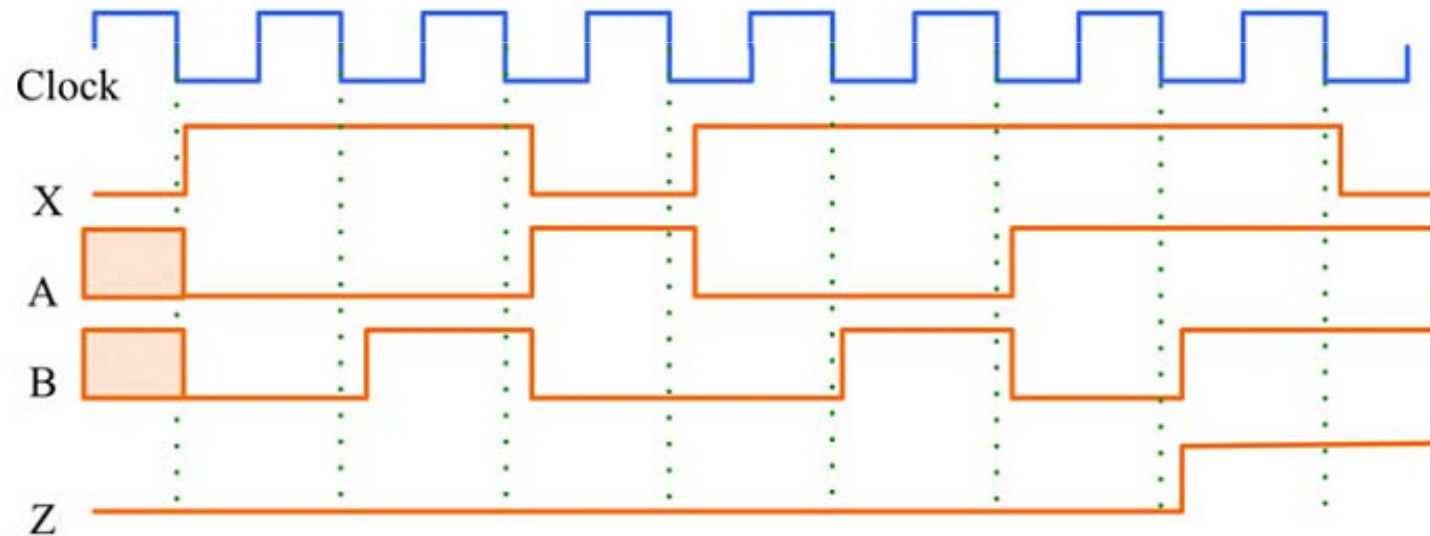 


EXAMPLE 4

- ❖ **Problem: Design Up/Down counter with Enable**
- ❖ Design a sequential circuit with two JK flip-flops A and B and two inputs X and E. If $E = 0$, the circuit remains in the same state, regardless of the input X. When $E = 1$ and $X = 1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11, back to 00, and then repeats. When $E = 1$ and $X = 0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01, back to 00 and then repeats.



EXAMPLE 4 (CONT.)

 

Present State		Inputs		Next State		FF Inputs			
A	B	E	X	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

EXAMPLE 4 (CONT.)

EX \ AB	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

$$J_A = BEX + B'EX'$$

EX \ AB	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	0	0	1	0
10	0	0	0	1


$$K_A = BEX + B'EX'$$

EX \ AB	00	01	11	10
00	0	0	1	1
01	x	x	x	x
11	x	x	x	x
10	0	0	1	1

$$J_B = E$$


EX \ AB	00	01	11	10
00	x	x	x	x
01	0	0	1	1
11	0	0	1	1
10	x	x	x	x

$$K_B = E$$

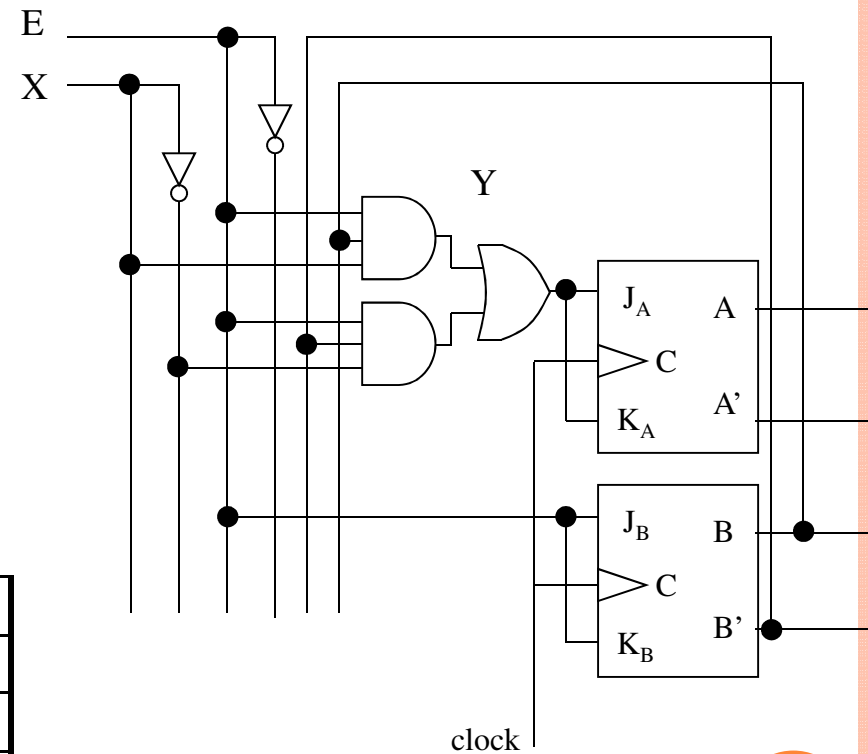

 EXAMPLE 5


❖ **Problem:** Design a traffic light controller for a 2-way intersection. In each way, there is a sensor and a light



Traffic	Action
EW only	EW Signal green NS Signal red
NS only	NS Signal green EW Signal red
EW & NS	Alternate
No traffic	Previous state

EXAMPLE 5 (CONT.)

❖ Step1: State Diagram

 

STATES

- NS: NS is green
- EW: EW is green

INPUTS

- Sensors X_1, X_0
- X_0 : car coming on NS
- X_1 : car coming on EW

OUTPUTS

- Light S_1, S_0
- S_0 : NS is green
- S_1 : EW is green

EXAMPLE 5 (CONT.)


❖ **Exercise:** Complete the design using:

- D-FF
- JK-FF
- T-FF




CHOICE OF FSM (MOORE VS MEALY)

 - ❖ In general, Moore-type is easier to design, but may require more states → more FFs.
- ❖ Mealy-type is more flexible and may to state reduction → simpler implementation.
- ❖ 3 consecutive 1 detector example



Mealy-type

 

STATE TABLE & CIRCUIT


State Assignment:

$S_0 \rightarrow 00$

$S_1 \rightarrow 01$

$S_2 \rightarrow 11$

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	1	0
1	1	0	0	0	0
1	1	1	1	1	1

 


State Equations:

$$D_A = Bx, D_B = (A' + B)x,$$


$$y = ABx$$

MEALY-TYPE FSM FOR SERIAL ADDER

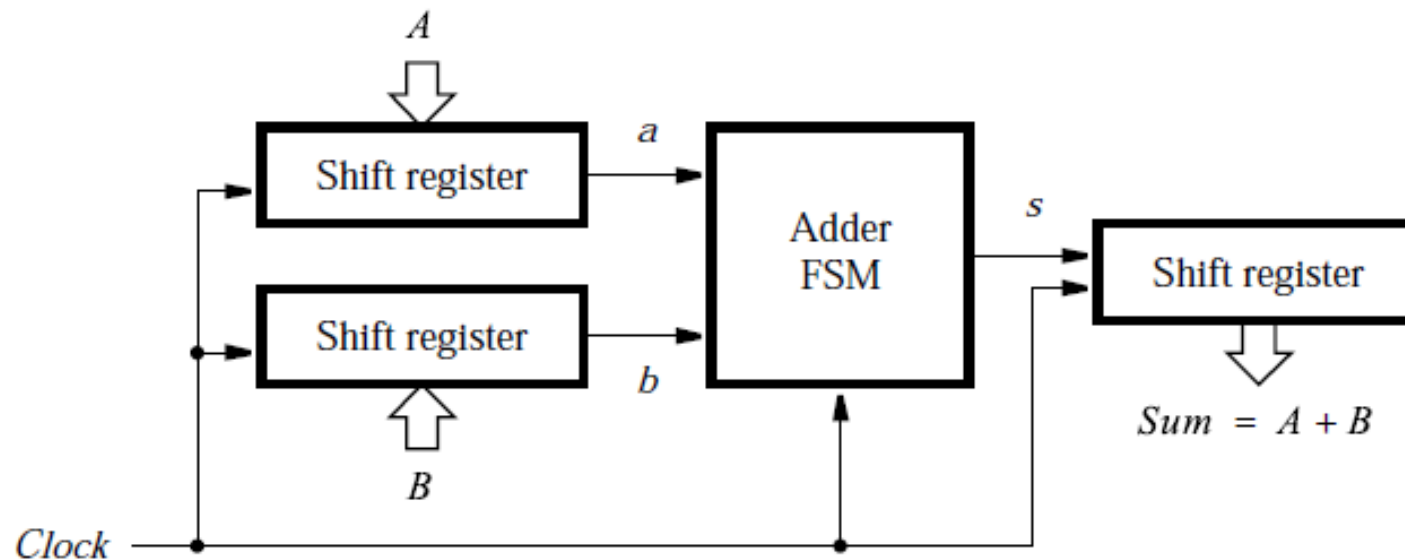- ❖ Input: $A = a_{n-1}a_{n-2}\dots a_0$, $B = b_{n-1}b_{n-2}\dots b_0$
- ❖ Output: $Sum = s_{n-1}s_{n-2}\dots s_0$.
- ❖ 3 Shift register for storing A , B and Sum .
- ❖ Addition performed “sequentially”.



STATE DIAGRAM & TABLE

 

G: carry-in = 0

H: carry-in = 1

Mealy-type FSM for
serial adder

Present state	Next state				Output s			
	$ab = 00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

State Table

Present state	Next state				Output			
	$ab = 00$	01	10	11	00	01	10	11
y	Y				s			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1


State-assigned Table

CIRCUIT


State Equations:

$$D = Y = ab + by + ay,$$

$$s = a \oplus b \oplus y$$

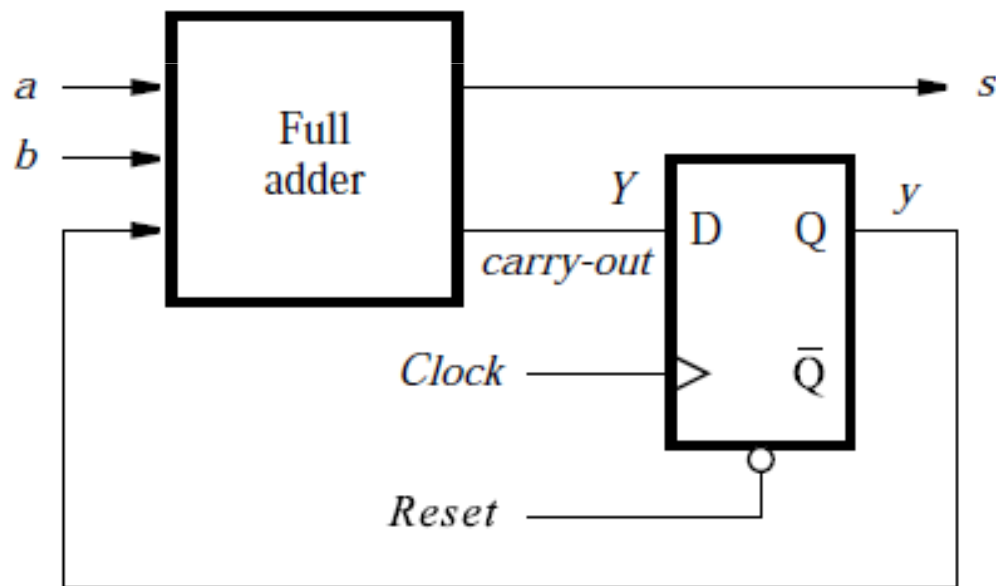

MOORE-TYPE STATE DIAGRAM & TABLE

 

Moore-type FSM for serial adder

Present state	Next state				Output s
	$ab = 00$	01	10	11	
G_0	G_0	G_1	G_1	H_0	0
G_1	G_0	G_1	G_1	H_0	1
H_0	G_1	H_0	H_0	H_1	0
H_1	G_1	H_0	H_0	H_1	1

State Table

Present state y_2y_1	Next state				Output s
	$ab = 00$	01	10	11	
	Y_2Y_1				
00	00	01	01	10	0
01	00	01	01	10	1
10	01	10	10	11	0
11	01	10	10	11	1


State-assigned Table

CIRCUIT

State Equations:

$$D_1 = Y_1 = a \oplus b \oplus y_2, D_2 = Y_2 = ab + by_2 + ay_2,$$

$$s = y_1$$

 

STATE REDUCTION

- Two sequential circuits may exhibit the same input-output behavior, but have a different number of states
- **State Reduction:** The process of reducing the number of states, while keeping the input-output behavior unchanged.
- It results in fewer Flip flops
- It may increase the combinational logic!




STATE REDUCTION (EXAMPLE)

❖ Is it possible to reduce this FSM?

- How many states?
- How many input/outputs?

❖ Notes:

 
- we use letters to denote states rather than binary codes
- we only consider input/output sequence and transitions



STATE REDUCTION (EXAMPLE)

❖ Step 1: get the state table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

 


STATE REDUCTION (EXAMPLE)

- ❖ Step 1: get the state table
- ❖ Step 2: find similar states

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

 - e and g are equivalent states
- remove g and replace it with e




STATE REDUCTION (EXAMPLE)

- ❖ Step 1: get the state table
- ❖ Step 2: find similar states

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

 - e and g are equivalent states
- remove g and replace it with e




STATE REDUCTION (EXAMPLE)

- ❖ Step 1: get the state table
- ❖ Step 2: find similar states

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

 - d and f are equivalent states
- remove f and replace it with d




STATE REDUCTION (EXAMPLE)

- ❖ Step 1: get the state table
- ❖ Step 2: find similar states


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 - d and f are equivalent states
- remove f and replace it with d





STATE REDUCTION (EXAMPLE)

❖ Reduced FSM

 

Verify sequence:

State	a	a	b	c	d	e	f	f	g	f
input	0	1	0	1	0	1	1	0	1	
output	0	0	0	0	0	1	1	0	1	

  

PARTITIONING MINIMIZATION PROCEDURE

Definition 1 *Two states S_i and S_j are said to be equivalent if and only if for every possible input sequence, the same output sequence will be produced regardless of whether S_i or S_j is the initial state.*

❖ *k -successor of S_i :* The next state with input= k .

❖ If S_i and S_j are equivalent, then their corresponding *k -successors* for all k are also equivalent.

Definition 2 *A partition consists of one or more blocks, where each block comprises a subset of states that may be equivalent, but the states in a given block are definitely not equivalent to the states in other blocks.*

EXAMPLE

❖ State table of this Moore-type FSM shown below

Step 1: $P_1 = (ABCDEFGG)$

Step 2: A, B, D \rightarrow output 1, else \rightarrow output 0

$P_2 = (ABD)(CEFG)$

Step 3: 0-successors of
(ABD) = (BDB),

1-successors = (CFG)

0-successors of (CEFG) =
(FFEF), 1-suc = (EC**D**G)

$P_3 = (ABD)(CEG)(F)$

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

EXAMPLE (CONT)

Step 4: F is not in the same block as CEG

$$P_4 = (AD)(B)(CEG)(F)$$

Step 5: Check k-successors of AD and CEG

AD: 0-suc=BB, 1-suc=CG

CEG: 0-suc=FFF, 1-suc=ECG

Thus, $P_5 = (AD)(B)(CEG)(F)$

(AD) \rightarrow A, (CEG) \rightarrow C

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

PREVIOUS EXAMPLE

$$P_1 = (abcdefg)$$

$$P_2 = (abc)(defg)$$

$$P_3 = (a)(bc)(df)(eg)$$

$$P_4 = (a)(b)(c)(df)(eg)$$

$$P_5 = (a)(b)(c)(df)(eg)$$


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

A VENDING MACHINE

Specification A candy vending machine with

 - accepts only nickels and dimes
- 15 cents for 1 candy
- If 20 cents are deposited, no change, but 5 cents are credited for next purchase.



A VENDING MACHINE (2)


Input D, N : indicate whether a dime or a nickel is deposited.

D, N cannot be 1 at the same time.


($sense_N, sense_D$: Sensor output)

Output z : indicate whether a candy is released or not.

Clock period : 100 ns

 

A VENDING MACHINE (3)

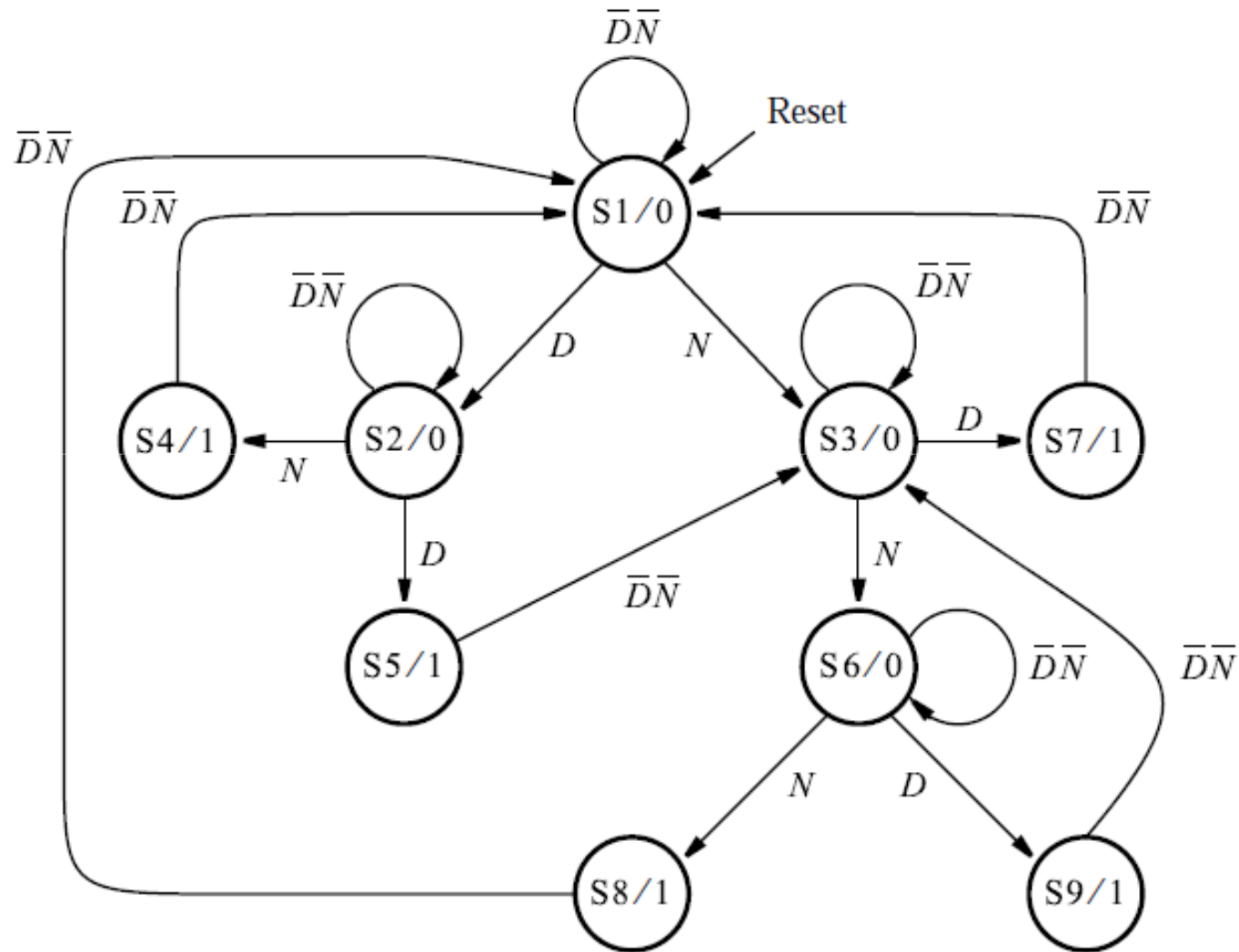

STATE TABLE & MINIMIZATION

1: $P_1 = (123456789)$

2: $P_2 = (1236)(45789)$

3: $P_3 = (1)(3)(26)(45789)$

4: $P_4 = (1)(3)(26)(478)(59)$

5: $P_5 = (1)(3)(26)(478)(59)$

New States:

(1) \rightarrow S1

(26) \rightarrow S2

(3) \rightarrow S3

(478) \rightarrow S4


(59) \rightarrow S5

Present state	Next state				Output z
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S6	S7	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1
S6	S6	S8	S9	—	0
S7	S1	—	—	—	1
S8	S1	—	—	—	1
S9	S3	—	—	—	1


Present state	Next state				Output z
	$DN = 00$	01	10	11	
S1	S1	S3	S2	—	0
S2	S2	S4	S5	—	0
S3	S3	S2	S4	—	0
S4	S1	—	—	—	1
S5	S3	—	—	—	1

Note that this is an example of *Incompletely specified state table*. 83

FSM

 

Moore-type

 

Mealy-type

EQUIVALENT STATES

❖ Theorem: *Two states p and q are equivalent iff for every single input X , the outputs are the same and the next states are equivalent, that is,*

$$\lambda(p, X) = \lambda(q, X) \text{ and } \delta(p, X) \equiv \delta(q, X)$$

where

$\lambda(p, X)$: Output given “present” state p
and input X

$\delta(p, X)$: Next state given p and X

IMPLICATION TABLE PROCEDURE

1. Construct a chart which contains a square for each pair of states.
2. Compare each pair of rows in the state table. If the outputs associated with states i and j are *different*, place an X in square $i-j$ to indicate that $i \not\equiv j$. If the outputs are the same, place the implied pairs in square $i-j$. (If the next states of i and j are m and n for some input x , then $m-n$ is an implied pair.) If the outputs and next states are the same (or if $i-j$ only implies itself), place a check (\checkmark) in square $i-j$ to indicate that $i \equiv j$.
3. Go through the table square-by-square. If square $i-j$ contains the implied pair $m-n$, and square $m-n$ contains an X, then $i \not\equiv j$, and an X should be placed in square $i-j$.
4. If any X's were added in step 3, repeat step 3 until no more X's are added.
5. For each square $i-j$ which does not contain an X, $i \equiv j$.

IMPLICATION TABLE EXAMPLE

B	B-D C-F	✗ due to different output			
C	✗	✗	— redundant		
D	C-G	B-D F-G	✗		
E	✗	✗	C-E	✗	
F	✗	✗	E-F D-E	✗	E-F C-D
G	✗	✗	E-G	✗	C-G E-F D-G
	A	B	C	D	E

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	D	F	1
C	F	E	0
D	B	G	1
E	F	C	0
F	E	D	0
G	F	G	0

IMPLICATION TABLE EXAMPLE (2)

B	B-D C-F				
C	X	X			
D	C-G	B-D F-G	X		
E	X	X	C-E	X	
F	X	X	E-F D-E	E-F C-D	
G	X	X	E-G	C-G	E-F D-G
	A	B	C	D	E

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	B	C	1
B	A	F	1
C	F	C	0
F	C	A	0

EQUIVALENT SEQUENTIAL CIRCUITS

Definition: Sequential circuit N_1 is equivalent to sequential circuit N_2 if for each state p in N_1 , there is a state q in N_2 such that $p \equiv q$, and conversely, for each state s in N_2 , there is a state t in N_1 such that $s \equiv t$, i.e.,

$$\forall p \in P, \exists q \in Q, p \equiv q \rightarrow N_1 \equiv N_2$$


$$\forall s \in Q, \exists t \in P, s \equiv t \rightarrow N_2 \equiv N_1$$

where P, Q : states of N_1, N_2




EXAMPLE $N_1 \equiv N_2$

	N_1			
	$X = 0$	1	$X = 0$	1
A	B	A	0	0
B	C	D	0	1
C	A	C	0	1
D	C	B	0	0

 

s_0	\times	$C-S_3$ $D-S_1$	$A-S_3$ $C-S_1$	\times
s_1	$B-S_3$ $A-S_0$	\times	\times	$C-S_3$ $B-S_0$
s_2	$B-S_0$ $A-S_2$	\times	\times	$C-S_0$ $B-S_2$
s_3	\times	$C-S_2$ $D-S_3$	$A-S_2$ $C-S_3$	\times
	A	B	C	D

	N_2			
	$X = 0$	1	$X = 0$	1
S_0	S_3	S_1	0	1
S_1	S_3	S_0	0	0
S_2	S_0	S_2	0	0
S_3	S_2	S_3	0	1

 

s_0	\times	$C-S_3$ $D-S_1$	$A-S_3$ $C-S_1$	\times
s_1	$B-S_3$ $A-S_0$	\times	\times	$C-S_3$ $B-S_0$
s_2	$B-S_0$ $A-S_2$	\times	\times	$C-S_0$ $B-S_2$
s_3	\times	$C-S_2$ $D-S_3$	$A-S_2$ $C-S_3$	\times
	A	B	C	D

STATE ASSIGNMENT


State Assignment: Assign unique binary codes to the states

- For m states, we need $\lceil \log_2 m \rceil$ bits (FF)

Example

- **Three Possible Assignments:**

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

 

ONE-HOT ENCODING (STATE ASSIGNMENT)

- ❖ Each state has only one 1, where the state variable whose value is 1 is regarded “hot”, e.g., 001, 010, 100.
- ❖ Feature
 - Often lead to simpler output expressions.
 - Consequently, faster circuit.
- ❖ Useful when applied to CPLD or FPGA with a flip-flop in each cell, i.e., many FFs available.



ONE-HOT ENCODING EXAMPLE (3 CONSECUTIVE 1 DETECTOR)


State Assignment:

$S_0 \rightarrow 001$

$S_1 \rightarrow 010$

$S_2 \rightarrow 100$

Present State			Input	Next State			Output
A	B	C	x	A	B	C	y
0	0	1	0	0	0	1	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	1	0
0	1	0	1	1	0	0	0
1	0	0	0	0	0	1	0
1	0	0	1	1	0	0	1

 

Input Equations:

$$D_A = C'x,$$

$$D_B = Cx,$$

$$D_C = x',$$

$$y = Ax$$

DESIGN SUMMARY

- To design a synchronous sequential circuit:
 - Obtain a state diagram
 - State reduction if necessary
 - Obtain State Table
 - State Assignment
 - Choose type of flip-flops
 - Use FF's excitation table to complete the table
 - Derive state equations
 - Use K-Maps
 - Obtain the FF input equations and the output equations
 - Draw the circuit diagram

