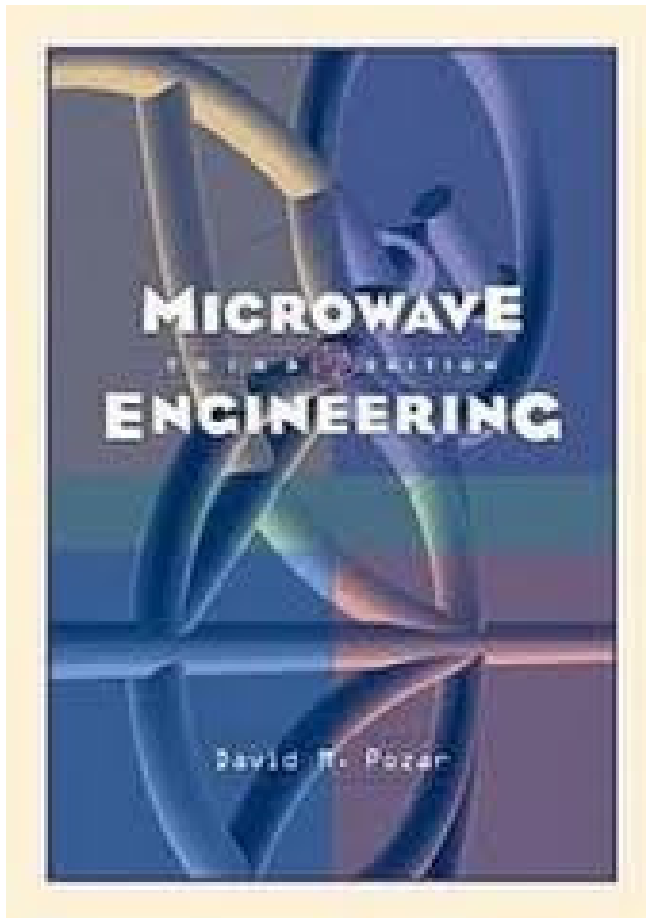


ECE 5317-6351

Microwave Engineering

Fall 2011

Prof. David R. Jackson
Dept. of ECE



Notes 14

Network Analysis
Multiport Networks


Multiport Networks

A general circuit can be represented by a multi-port network, where the “ports” are defined as access terminals at which we can define voltages and currents.


Examples:

Note: Equal and opposite currents are assumed on the two wires of a port.

1) One-port network

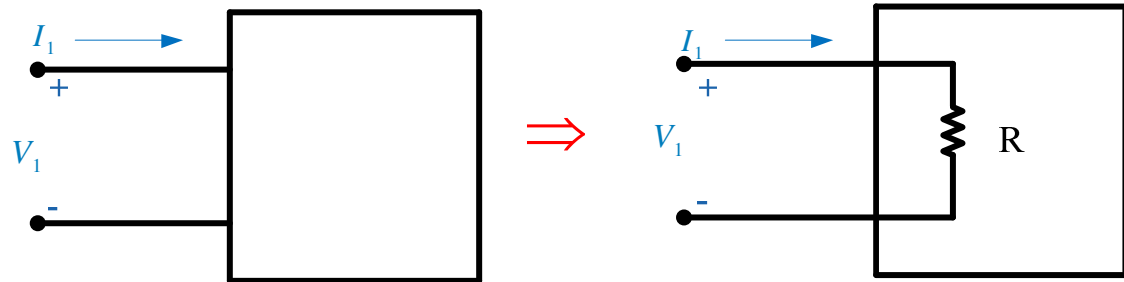

2) Two-port network

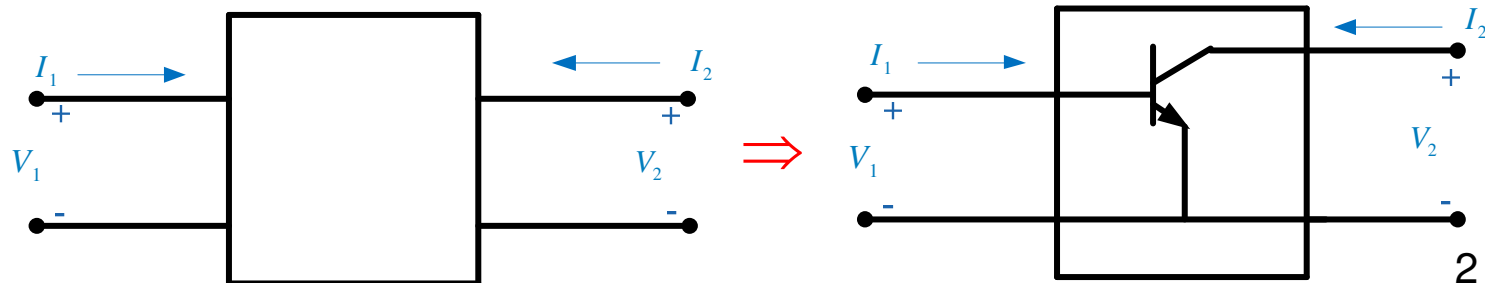

Multiport Networks (cont.)

3) N -port Network


To represent multi-port networks we use:

- Z (impedance) parameters
- Y (admittance) parameters
- h (hybrid) parameters
- $ABCD$ parameters

Not easily
measurable at
high frequency


- S (scattering) parameters

Measurable at high frequency

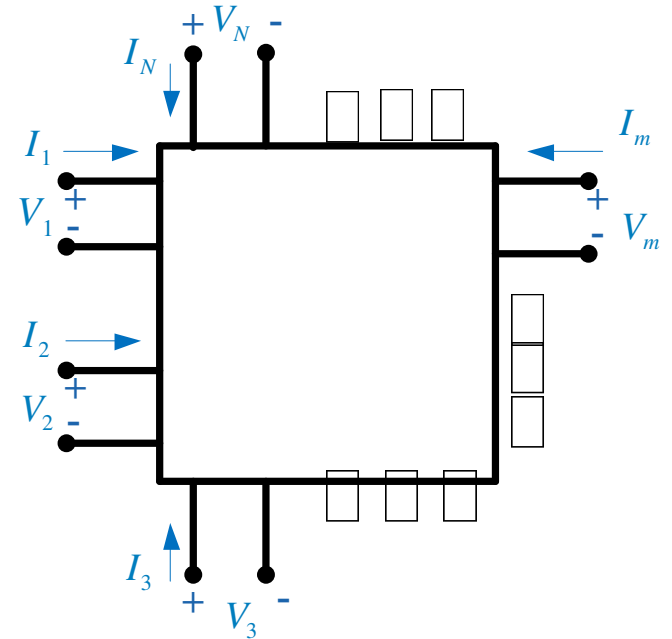

Poynting Theorem (Phasor Domain)

$$\int_V -\frac{1}{2}(\underline{E} \cdot \underline{J}^{i*}) dV = \oint_S \underline{S} \cdot \hat{n} dS + \int_V \left(\frac{1}{2} \omega \epsilon_c'' |\underline{E}|^2 + \frac{1}{2} \omega \mu'' |\underline{H}|^2 \right) dV + 2j\omega \int_V \left(\frac{1}{4} \mu' |\underline{H}|^2 - \frac{1}{4} \epsilon_c' |\underline{E}|^2 \right) dV$$

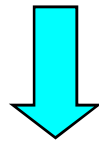


The last term is the VARS consumed by the region.

The notation $\langle \rangle$ denotes time-average.

$$P_s = P_f + \langle P_d \rangle + j(2\omega)(\langle W_m \rangle - \langle W_e \rangle)$$

Self Impedance

Consider a general **one-port** network

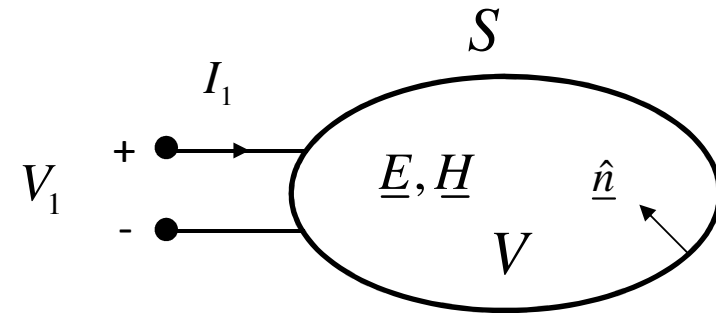

Complex power delivered to network:

$$P_{in} = \frac{1}{2} \oint_S (\underline{E} \times \underline{H}) \cdot \underline{\hat{n}} \, ds = P_d + j2\omega(W_m - W_e)$$

$$= \frac{1}{2} V_1 I_1^*$$

Average power
dissipated in [W]

$$P_d = \langle \mathbf{P}_d \rangle$$

Average electric
energy (in [J])
stored inside V

$$W_e = \langle \mathbf{W}_e \rangle$$

Average magnetic energy
(in [J]) stored inside V


$$W_m = \langle \mathbf{W}_m \rangle$$

Define Self Impedance (Z_{in})

$$Z_{in} \equiv \frac{V_1}{I_1} = \frac{V_1 I_1^*}{|I_1|^2} = \frac{\frac{1}{2} V_1 I_1^*}{\frac{1}{2} |I_1|^2} = \frac{P_{in}}{\frac{1}{2} |I_1|^2}$$
$$= R_{in} + jX_{in} = \frac{P_d + j2\omega(W_m - W_e)}{\frac{1}{2} |I_1|^2}$$

$$R_{in} = \frac{2P_d}{|I_1|^2}$$

$$X_{in} = \frac{4\omega(W_m - W_e)}{|I_1|^2}$$

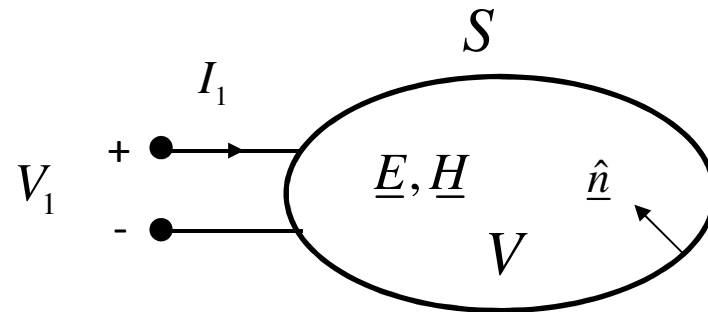

Self Impedance (cont.)

We can show that for physically realizable networks the following apply:

Please see the Pozar book for a proof.

$$V_1(-\omega) = V_1^*(\omega)$$

$$\Rightarrow Z_{in}(-\omega) = Z_{in}^*(\omega)$$

$$I_1(-\omega) = I_1^*(\omega)$$

$$\Rightarrow R_{in}(\omega) \text{ is an even function of } \omega$$


$$Z_{in}(\omega) = R_{in}(\omega) + jX_{in}(\omega)$$

$$X_{in}(\omega) \text{ is an odd function of } \omega$$

Note: Frequency is usually defined as a positive quantity. However, we consider the analytic continuation of the functions into the complex frequency plane.

Two-Port Networks

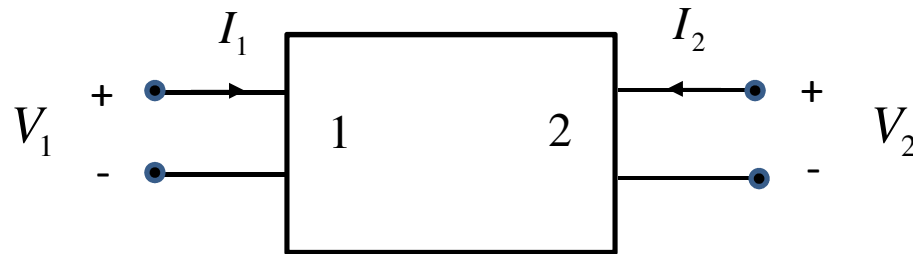Consider a general **2-port** linear network:



In terms of Z-parameters, we have (from superposition)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Impedance (Z) matrix

$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow [V] = [Z][I]$$

Elements of Z-Matrix: Z-Parameters

(open-circuit parameters)

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

Port 2 open circuited


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

Port 1 open circuited


$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

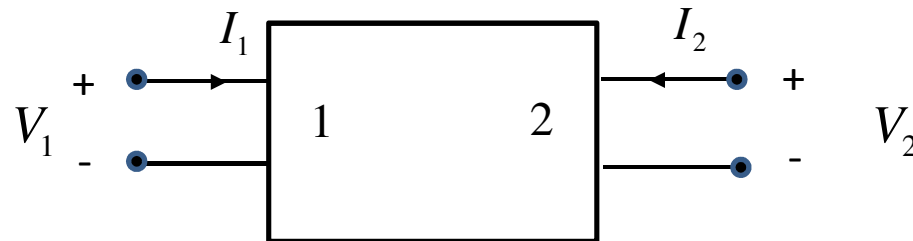

Z-Parameters (cont.)

$$Z_{ij} = \left. \frac{V_i}{I_j} \right|_{I_k=0 \quad k \neq j}$$

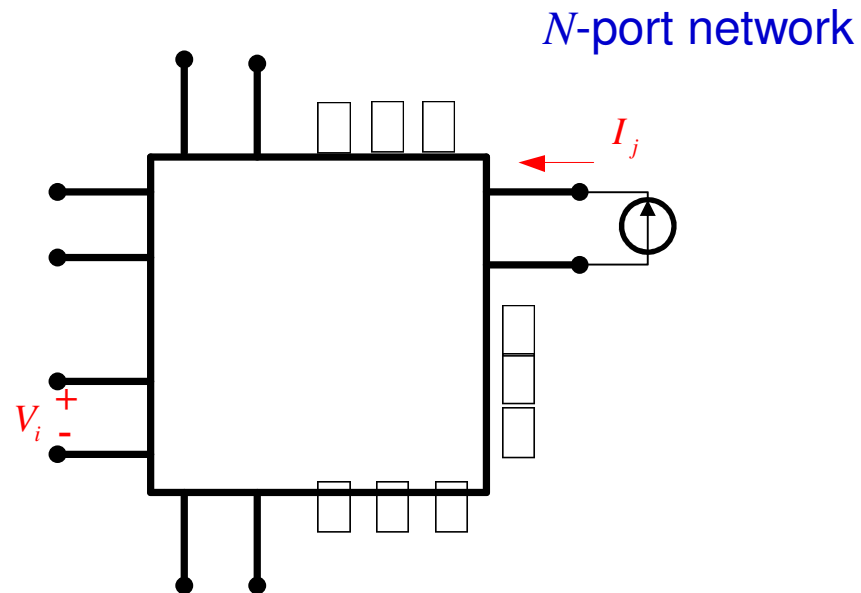


We inject a current into port j and measure the voltage (with an ideal voltmeter) at port i . All ports are open-circuited except j .

Z-Parameters (cont.)

Z-parameters are convenient for series connected networks.

$$\begin{aligned}
 \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} &= \begin{bmatrix} V_1^A \\ V_2^A \end{bmatrix} + \begin{bmatrix} V_1^B \\ V_2^B \end{bmatrix} \\
 &= \begin{bmatrix} Z^A \end{bmatrix} \begin{bmatrix} I^A \end{bmatrix} + \begin{bmatrix} Z^B \end{bmatrix} \begin{bmatrix} I^B \end{bmatrix} \\
 &= \left(\begin{bmatrix} Z^A \end{bmatrix} + \begin{bmatrix} Z^B \end{bmatrix} \right) \begin{bmatrix} I \end{bmatrix} \\
 &= \left(\begin{bmatrix} Z^A \end{bmatrix} + \begin{bmatrix} Z^B \end{bmatrix} \right) \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \\
 &= \begin{bmatrix} Z^A + Z^B \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}
 \end{aligned}$$

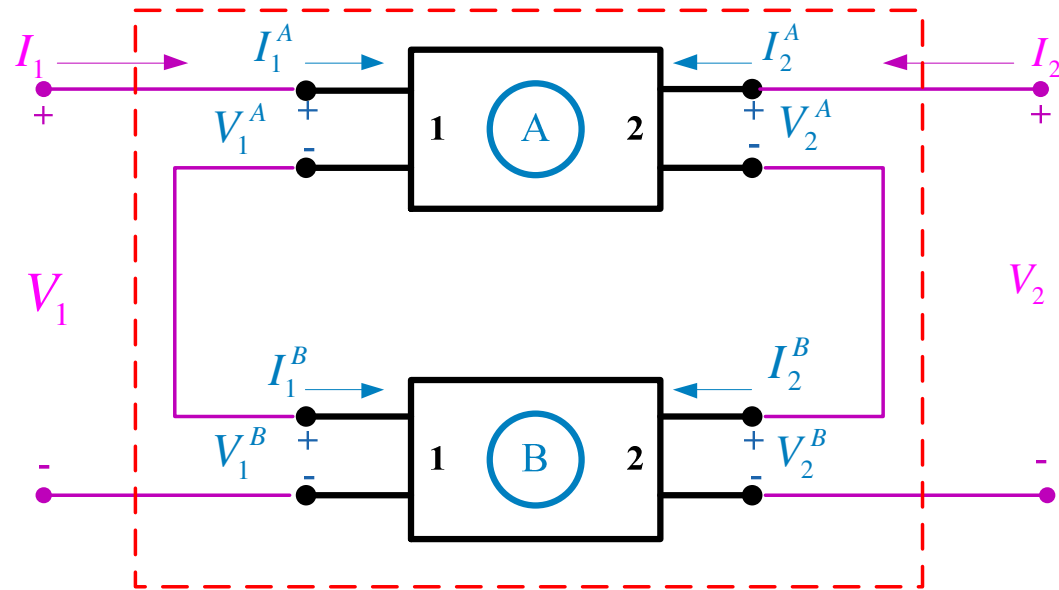


$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11}^A + Z_{11}^B & Z_{12}^A + Z_{12}^B \\ Z_{21}^A + Z_{21}^B & Z_{22}^A + Z_{22}^B \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Series $\Rightarrow$

$$\begin{aligned}
 I_1 &= I_1^A = I_1^B \\
 I_2 &= I_2^A = I_2^B
 \end{aligned}$$

Admittance (Y) Parameters

Consider a 2-port network:

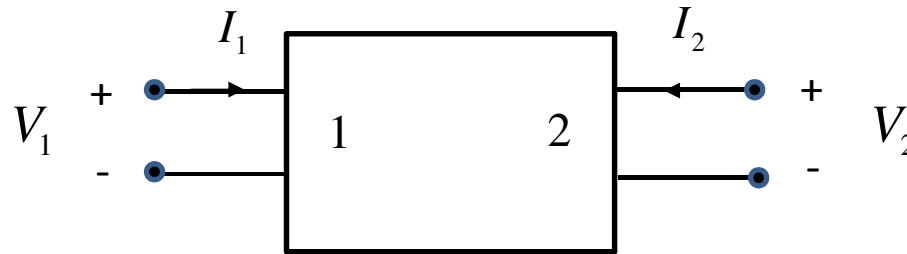

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Admittance
matrix

or


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow [I] = [Y][V]$$

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \quad k \neq j}$$

Short-circuit parameters

Y-Parameters (cont.)

$$Y_{ij} = \left. \frac{I_i}{V_j} \right|_{V_k=0 \quad k \neq j}$$

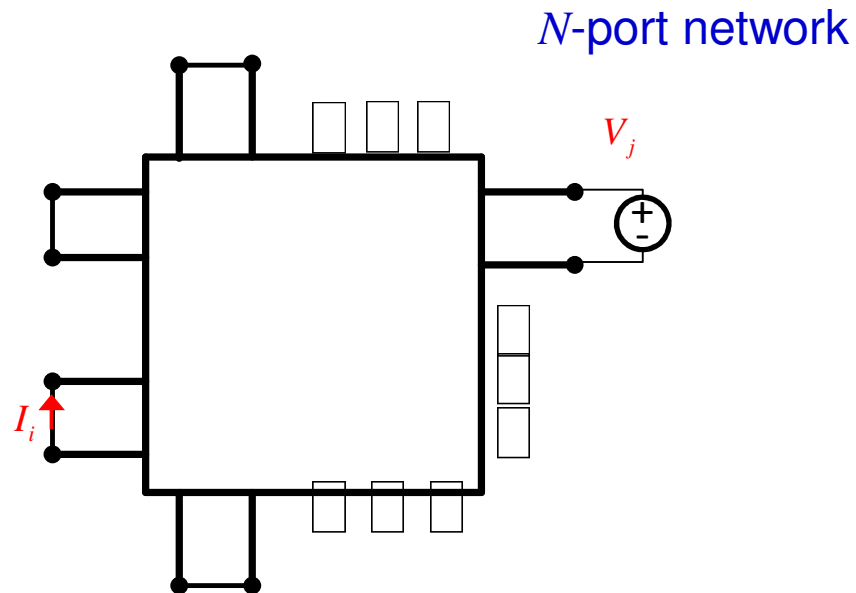


We apply a voltage across port j and measure the current (with an ideal current meter) at port i . All ports are short-circuited except j .

Admittance (Y) Parameters

Y -parameters are convenient for parallel connected networks.
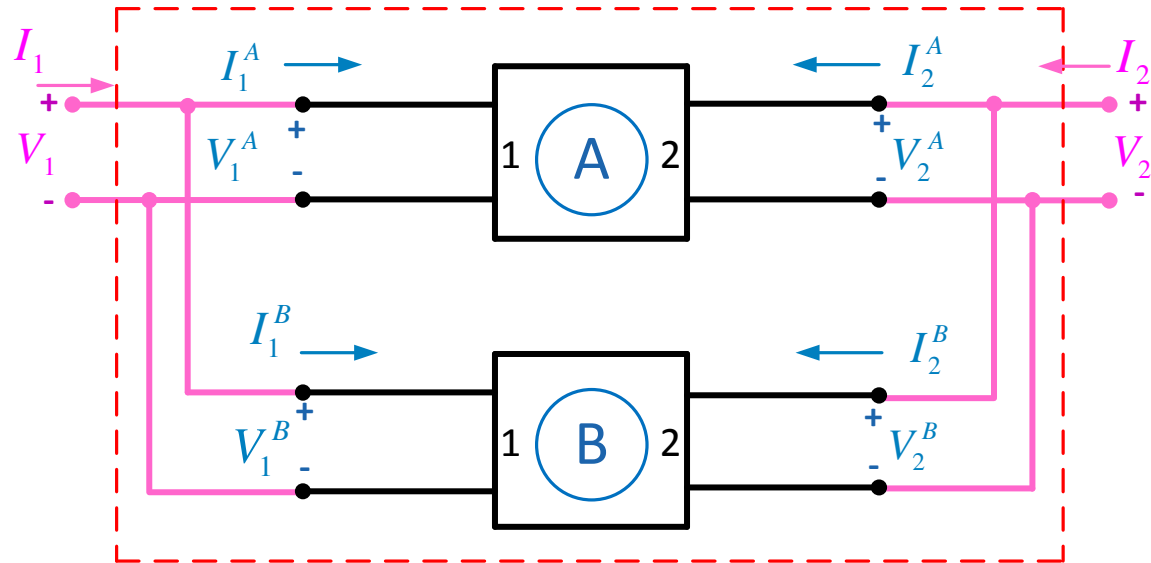
$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_1^A \\ I_2^A \end{bmatrix} + \begin{bmatrix} I_1^B \\ I_2^B \end{bmatrix}$$



$$= \begin{bmatrix} Y_{11}^A + Y_{11}^B & Y_{12}^A + Y_{12}^B \\ Y_{21}^A + Y_{21}^B & Y_{22}^A + Y_{22}^B \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Parallel $\Rightarrow V_1 = V_1^A = V_1^B$
 $V_2 = V_2^A = V_2^B$

Admittance (Y) Parameters

Relation between $[Z]$ and $[Y]$ matrices:

$$[V] = [Z][I]$$

$$[I] = [Y][V]$$

Hence

$$\begin{aligned}[V] &= [Z]([Y][V]) \\ &= ([Z][Y])[V]\end{aligned}$$

$$[Z][Y] = [U] = \text{Identity Matrix}$$

Therefore

$$[Y] = [Z]^{-1}$$

Reciprocal Networks

If a network does not contain non-reciprocal devices or materials* (i.e. ferrites, or active devices), then the network is “reciprocal.”

$$\Rightarrow Z_{ij} = Z_{ji} \quad (Y_{ij} = Y_{ji})$$

Note: The inverse of a symmetric matrix is symmetric.

$$\Rightarrow [Z] \text{ and } [Y] \text{ are symmetric}$$

* A reciprocal material is one that has reciprocal permittivity and permeability tensors.
A reciprocal device is one that is made from reciprocal materials

Example of a nonreciprocal material: a biased ferrite

(This is very useful for making isolators and circulators.)

Reciprocal Materials

$$\underline{D} = \underline{\underline{\epsilon}} \cdot \underline{E}$$

$$\underline{B} = \underline{\underline{\mu}} \cdot \underline{H}$$

$$\begin{bmatrix} D_x \\ D_y \\ D_z \end{bmatrix} = \begin{bmatrix} \epsilon_{xx} & \epsilon_{xy} & \epsilon_{xz} \\ \epsilon_{yx} & \epsilon_{yy} & \epsilon_{yz} \\ \epsilon_{zx} & \epsilon_{zy} & \epsilon_{zz} \end{bmatrix} \begin{bmatrix} E_x \\ E_y \\ E_z \end{bmatrix} \quad \begin{bmatrix} B_x \\ B_y \\ B_z \end{bmatrix} = \begin{bmatrix} \mu_{xx} & \mu_{xy} & \mu_{xz} \\ \mu_{yx} & \mu_{yy} & \mu_{yz} \\ \mu_{zx} & \mu_{zy} & \mu_{zz} \end{bmatrix} \begin{bmatrix} \mu_x \\ \mu_y \\ \mu_z \end{bmatrix}$$


Reciprocal: $\epsilon_{ij} = \epsilon_{ji}$, $\mu_{ij} = \mu_{ji}$

Ferrite: $\underline{\underline{\mu}} = \mu_0 \begin{bmatrix} \alpha & j\gamma & 0 \\ -j\gamma & \alpha & 0 \\ 0 & 0 & 1 \end{bmatrix}$ $\underline{\underline{\mu}}$ is not symmetric!


Reciprocal Networks (cont.)

We can show that the equivalent circuits for reciprocal 2-port networks are:

T-equivalent

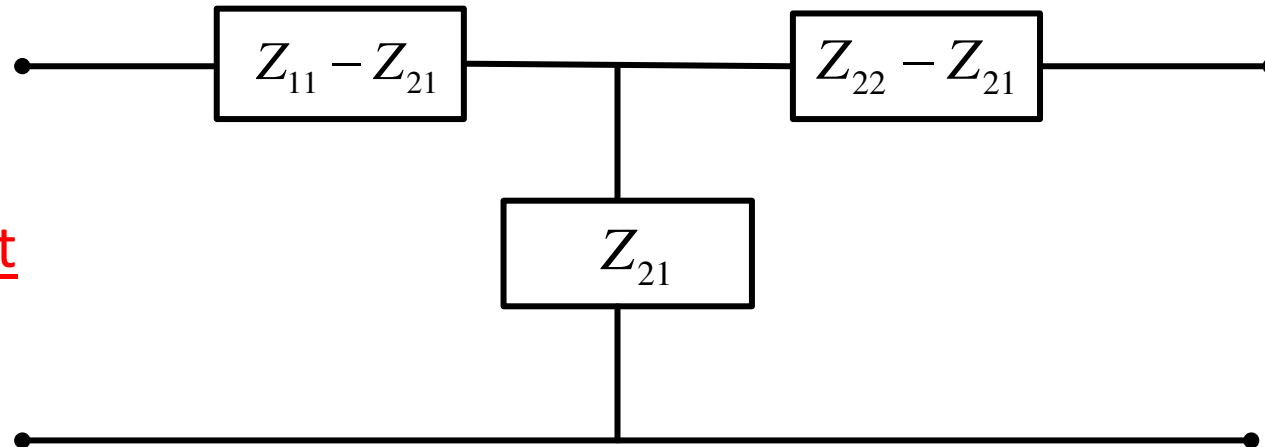

Pi-equivalent

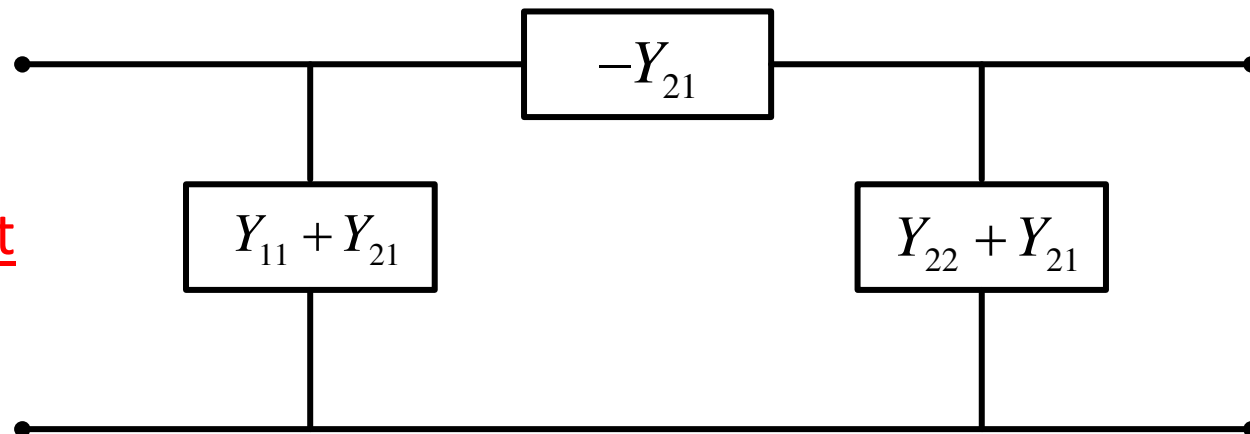

ABCD-Parameters

There are defined only for 2-port networks.

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2' \end{bmatrix}$$



$$I_2' = -I_2$$


$$A = \left. \frac{V_1}{V_2} \right|_{I_2' = 0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2' = 0}$$

$$B = \left. \frac{V_1}{I_2'} \right|_{V_2 = 0}$$

$$D = \left. \frac{I_1}{I_2'} \right|_{V_2 = 0}$$

Cascaded Networks

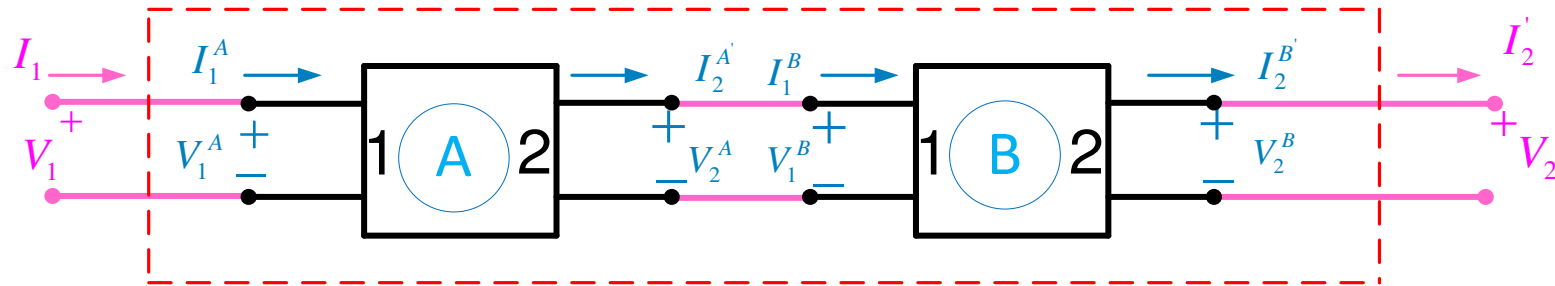

$$\begin{aligned} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} &= \begin{bmatrix} V_1^A \\ I_1^A \end{bmatrix} = [ABCD^A] \begin{bmatrix} V_2^A \\ I_2^A \end{bmatrix} \\ &= [ABCD^A] \begin{bmatrix} V_1^B \\ I_1^B \end{bmatrix} \\ &= [ABCD^A] [ABCD^B] \begin{bmatrix} V_2^B \\ I_2^B \end{bmatrix} \end{aligned}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = [ABCD^{AB}] \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


A nice property of the ABCD matrix is that it is easy to use with cascaded networks: you simply multiply the ABCD matrices together.

Scattering Parameters

- At high frequencies, Z , Y , h & ABCD parameters are difficult (if not impossible) to measure.
 - V and I are not uniquely defined
 - Even if defined, V and I are extremely difficult to measure (particularly I).
 - Required open and short-circuit conditions are often difficult to achieve.
- Scattering (S) parameters are often the best representation for multi-port networks at high frequency.

Scattering Parameters (cont.)

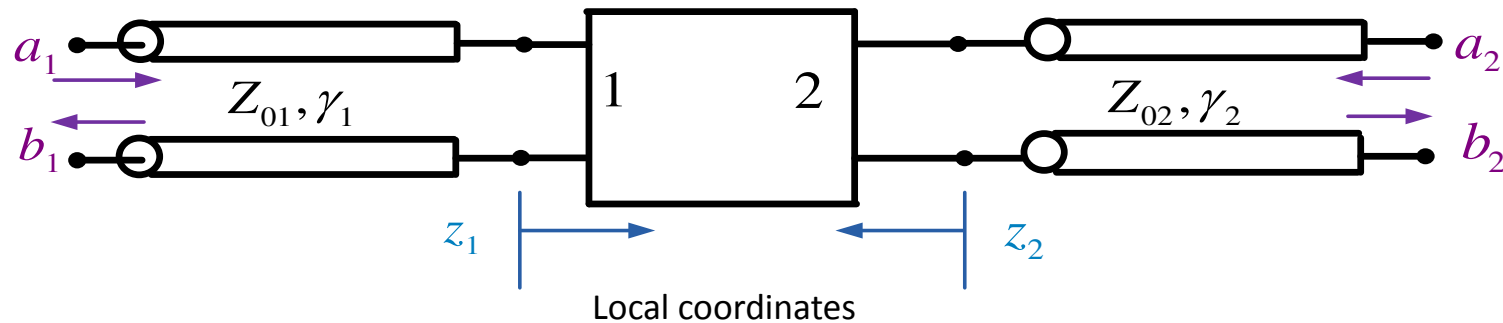S-parameters are defined assuming transmission lines are connected to each port.



On each transmission line:

$$V_i(z_i) = V_{i0}^+ e^{-\gamma_i z_i} + V_{i0}^- e^{+\gamma_i z_i} = V_i^+(z_i) + V_i^-(z_i)$$

$$I_i(z_i) = \frac{V_i^+(z_i)}{Z_{0i}} - \frac{V_i^-(z_i)}{Z_{0i}} \quad i = 1, 2$$

$$\text{Incoming wave function} \equiv a_i(z_i) \equiv V_i^+(z_i) / \sqrt{Z_{0i}}$$

$$\text{Outgoing wave function} \equiv b_i(z_i) \equiv V_i^-(z_i) / \sqrt{Z_{0i}}$$


For a One-Port Network

$$\Gamma_L = \frac{V_1^-(0)/\sqrt{Z_{01}}}{V_1^+(0)/\sqrt{Z_{01}}}$$

$$= \frac{b_1(0)}{a_1(0)}$$

$$= S_{11}$$
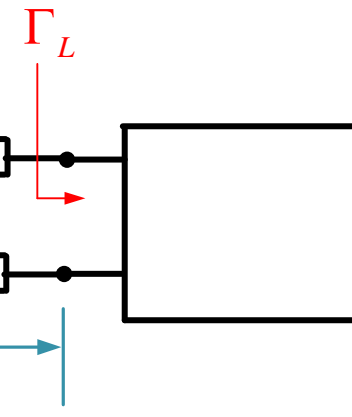
$$\Rightarrow b_1(0) = \Gamma_L a_1(0) \\ = S_{11} a_1(0)$$




For a one-port network, S_{11} is defined to be the same as Γ_L .

Incoming wave function $\equiv a_i(z_i) \equiv V_i^+(z_i)/\sqrt{Z_{0i}}$

Outgoing wave function $\equiv b_i(z_i) \equiv V_i^-(z_i)/\sqrt{Z_{0i}}$

For a Two-Port Network

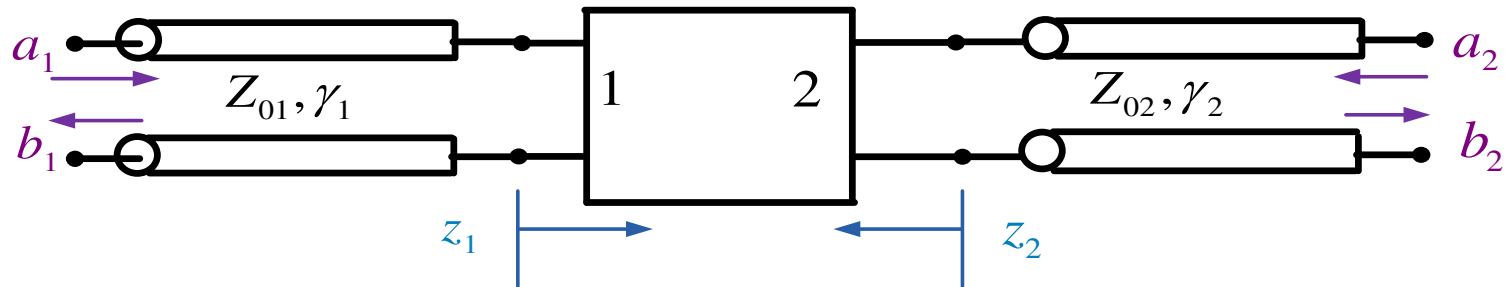

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$

$$\Rightarrow \begin{bmatrix} b_1(0) \\ b_2(0) \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1(0) \\ a_2(0) \end{bmatrix} \Rightarrow [b] = [S][a]$$

Scattering
matrix

Scattering Parameters

$$b_1(0) = S_{11}a_1(0) + S_{12}a_2(0)$$

$$b_2(0) = S_{21}a_1(0) + S_{22}a_2(0)$$


$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right _{a_2=0}$	 Output is matched	 input reflection coef. w/ output matched
$S_{12} = \left. \frac{b_1(0)}{a_2(0)} \right _{a_1=0}$	 Input is matched	 reverse transmission coef. w/ input matched
$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right _{a_2=0}$	 Output is matched	 forward transmission coef. w/ output matched
$S_{22} = \left. \frac{b_2(0)}{a_2(0)} \right _{a_1=0}$	 Input is matched	 output reflection coef. w/ input matched

Scattering Parameters (cont.)

For a general multiport network:


$$S_{ij} = \left. \frac{b_i(0)}{a_j(0)} \right|_{a_k=0, k \neq j}$$

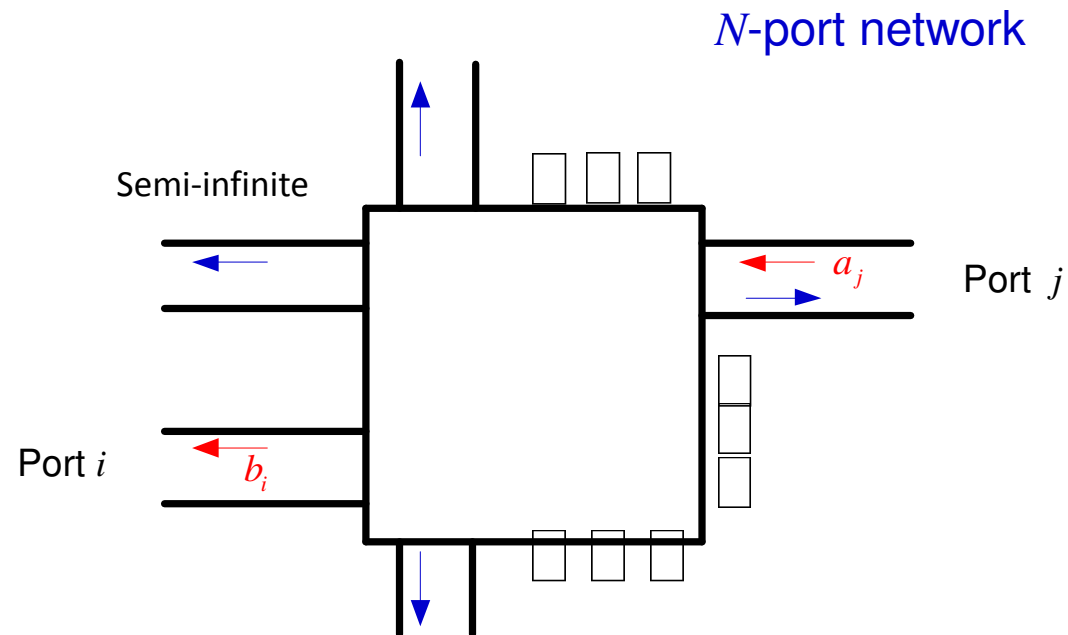All ports except j are semi-infinite (or matched)



Scattering Parameters (cont.)

Illustration of a three-port network

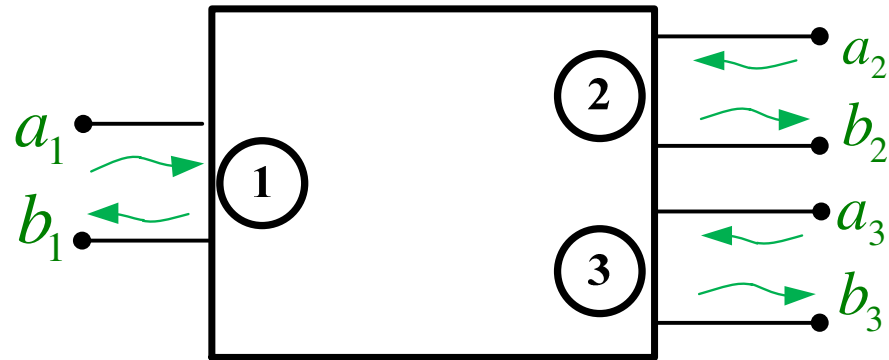

Scattering Parameters (cont.)

For **reciprocal** networks, the S -matrix is symmetric.


$$\Rightarrow S_{ij} = S_{ji} \quad i \neq j$$

Note: If all lines entering the network have the same characteristic impedance, then

$$S_{ij} = \left. \frac{V_i^-(0)}{V_j^+(0)} \right|_{V_k^+=0 \quad k \neq j}$$

Scattering Parameters (cont.)

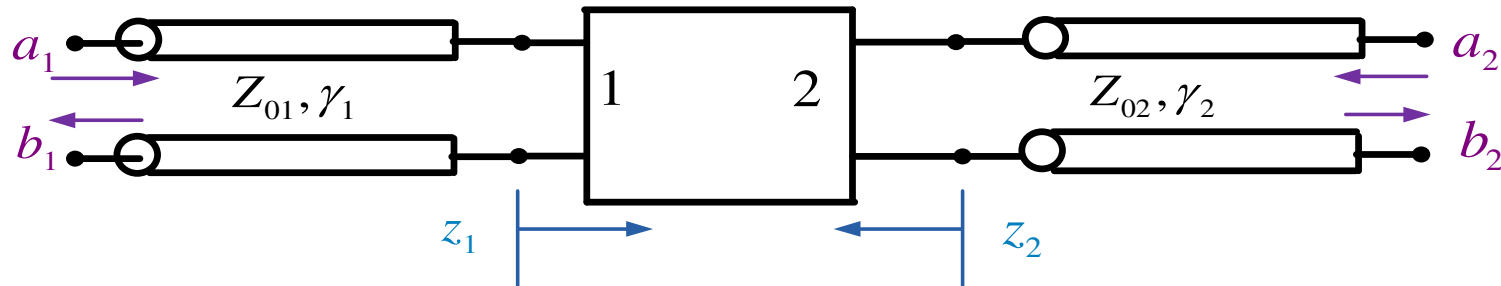Why are the wave functions (a and b) defined as they are?



$$P_i^+(0) = \frac{1}{2} \operatorname{Re} [V_i^+(0) I_i^{+*}(0)] = \frac{1}{2} \frac{|V_i^+(0)|^2}{Z_{0i}} \quad (\text{assuming lossless lines})$$

Note:

$$a_i(0) = V_i^+(0) / \sqrt{Z_{0i}}$$

$$\Rightarrow P_i^+(0) = \frac{1}{2} |a_i(0)|^2$$

Scattering Parameters (cont.)

Similarly,

$$P_i^-(0) = \frac{1}{2} \frac{|V_i^-(0)|^2}{Z_{0i}} = \frac{1}{2} |b_i(0)|^2$$

Also,

$$V_i^+(-l_i) = V_i^+(0) e^{+\gamma_i l_i}$$


$$V_i^-(-l_i) = V_i^-(0) e^{-\gamma_i l_i}$$

$$\Rightarrow P_i^+(-l_i) = \frac{1}{2} |a_i(-l_i)|^2 = \frac{1}{2} |a_i(0)|^2 e^{+2\alpha_i l_i}$$

$$P_i^-(-l_i) = \frac{1}{2} |b_i(-l_i)|^2 = \frac{1}{2} |b_i(0)|^2 e^{-2\alpha_i l_i}$$

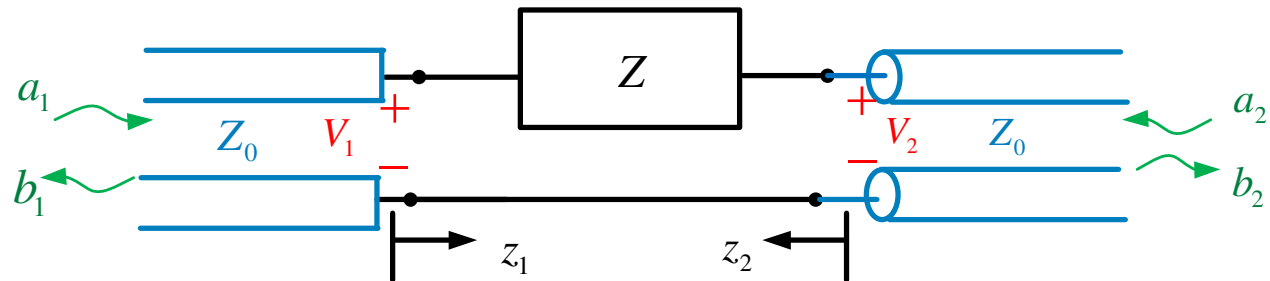
Example

Find the S parameters for a series impedance Z .



Note that **two** different coordinate systems are being used here!

Example (cont.)

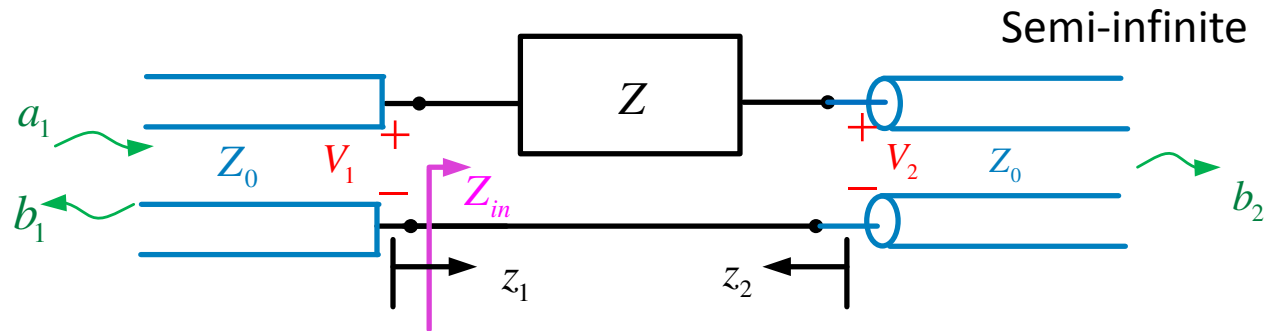

S_{11} Calculation:

$$S_{11} = \left. \frac{b_1(0)}{a_1(0)} \right|_{a_2=0} = \frac{V_1^-(0)}{V_1^+(0)} = \left. \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right|_{a_2=0} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0}$$


$$\Rightarrow S_{11} = \frac{Z}{Z + 2Z_0}$$

By symmetry:

$$S_{22} = S_{11}$$

Example (cont.)

S_{21} Calculation:

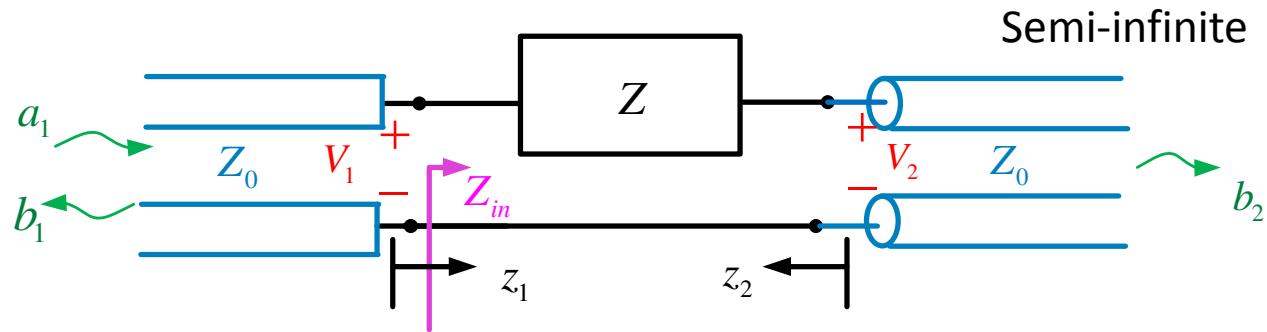

$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0}$$

$$= \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0}$$

$$V_1^+(0) = a_1(0) \sqrt{Z_0}$$


$$a_2 = 0 \Rightarrow V_2^-(0) = V_2(0)$$

$$V_2(0) = V_1(0) \left(\frac{Z_0}{Z + Z_0} \right)$$

$$V_1(0) = a_1 \sqrt{Z_0} (1 + S_{11})$$

$$\Rightarrow V_2^-(0) = V_2(0) = a_1 \sqrt{Z_0} (1 + S_{11}) \left(\frac{Z_0}{Z + Z_0} \right)$$

Example (cont.)

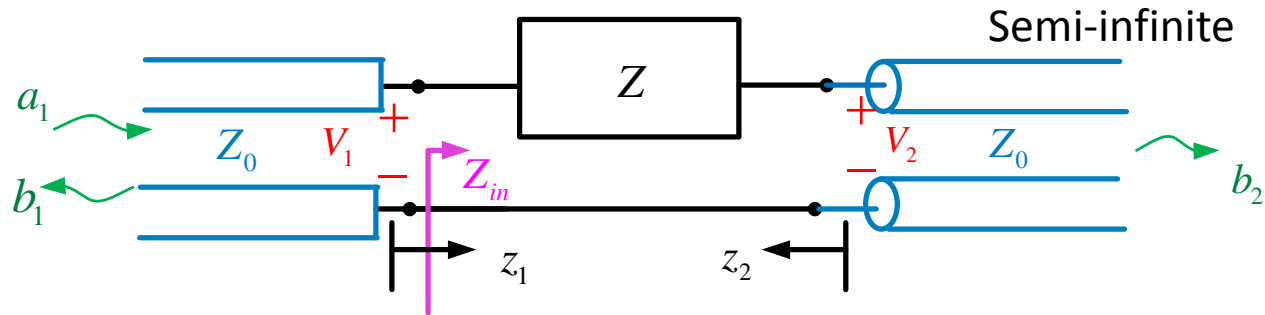

$$S_{21} = \frac{a_1(0)\sqrt{Z_0}(1+S_{11})\left(\frac{Z_0}{Z+Z_0}\right)}{a_1(0)\sqrt{Z_0}}$$

$$= (1+S_{11})\left(\frac{Z_0}{Z+Z_0}\right) = \left(1+\frac{Z}{Z+2Z_0}\right)\left(\frac{Z_0}{Z+Z_0}\right) = \left(\frac{2Z+2Z_0}{Z+2Z_0}\right)\left(\frac{Z_0}{Z+Z_0}\right)$$


Hence

$$S_{21} = \frac{2Z_0}{Z+2Z_0}$$

$$S_{12} = S_{21}$$

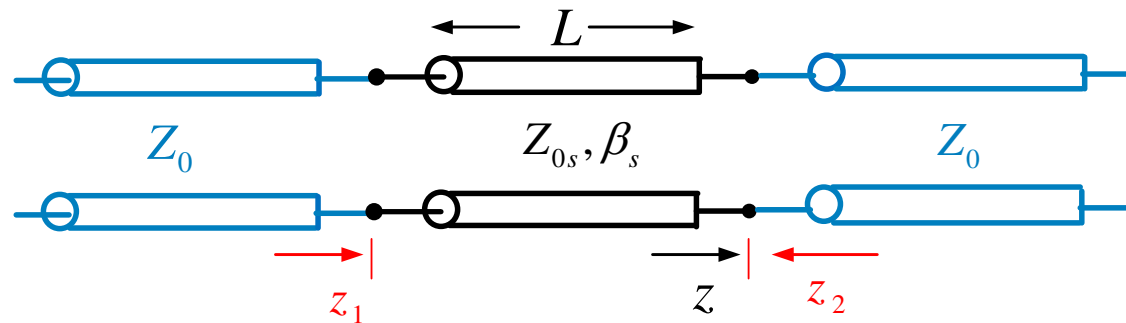Example


Find the S parameters for a length L of transmission line.



Note that **three** different coordinate systems are being used here!

Example (cont.)


S_{11} Calculation:

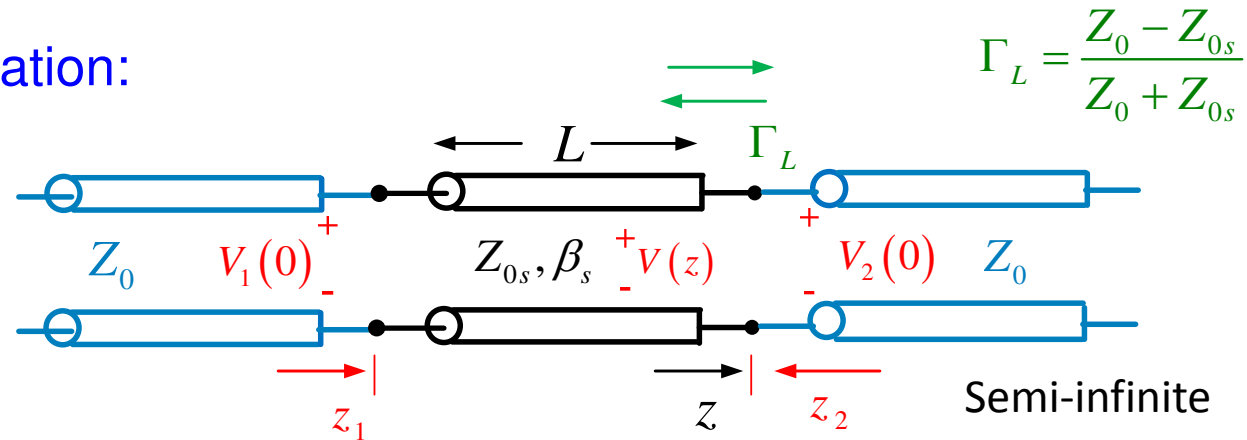

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{in}|_{a_2=0} - Z_0}{Z_{in}|_{a_2=0} + Z_0} = S_{22} \text{ (by symmetry)}$$

$$Z_{in}|_{a_2=0} = Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} = Z_{0s} \frac{(1 + \Gamma_L e^{-j2\beta_s L})}{(1 - \Gamma_L e^{-j2\beta_s L})}$$

Example (cont.)

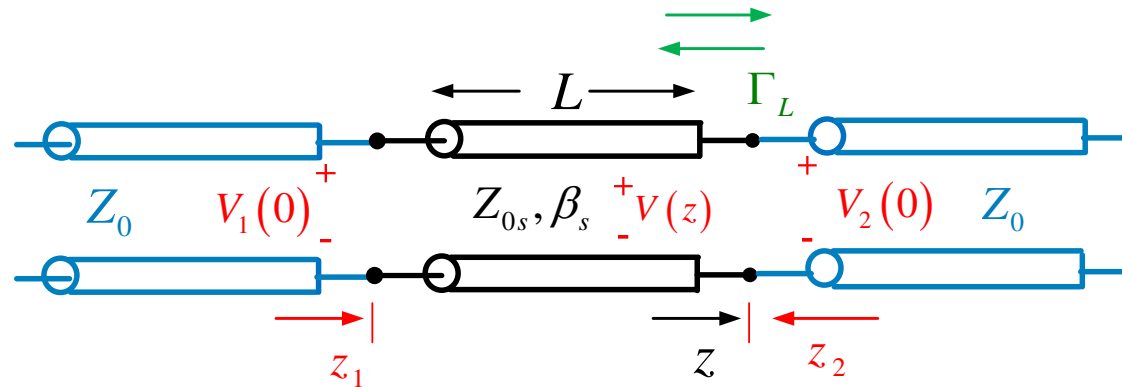


Hence

$$S_{11} = S_{22} = \frac{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} - Z_0}{Z_{0s} \frac{(Z_0 + jZ_{0s} \tan \beta_s L)}{(Z_{0s} + jZ_0 \tan \beta_s L)} + Z_0}$$

Note: If $Z_{0s} = Z_0 \Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$

Example (cont.)

S_{21} Calculation:

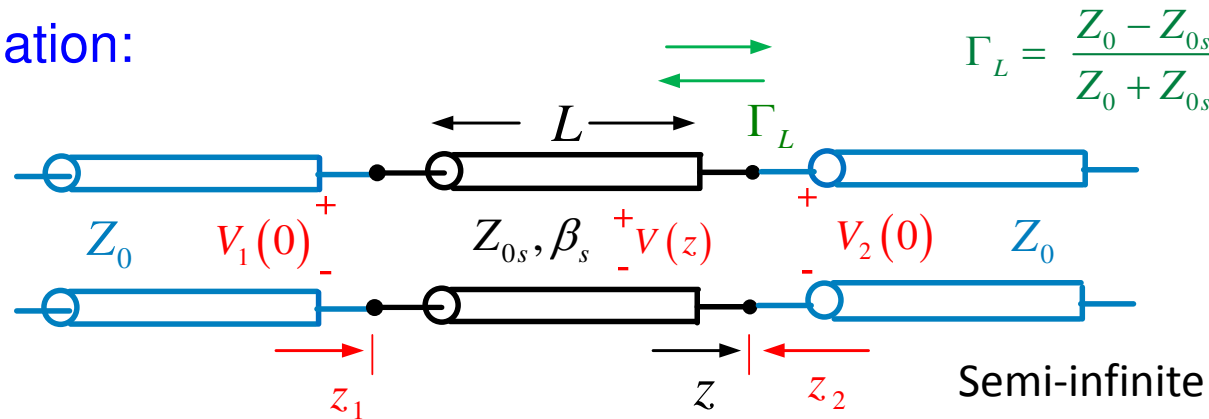

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \left. \frac{V_2^-(0)/\sqrt{Z_0}}{V_1^+(0)/\sqrt{Z_0}} \right|_{a_2=0}$$


$$V_1(0) = V_1^+(0)(1 + S_{11})$$

Hence, for the denominator of the S_{21} equation we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$

We now try to put the numerator of the S_{21} equation in terms of $V_1(0)$.

Example (cont.)

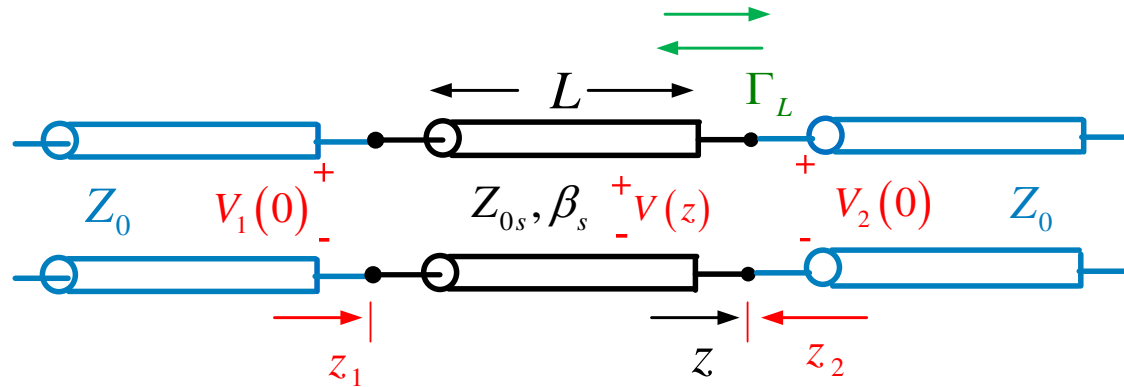

$$V_2^-(0) = V_2(0) = V(0) = V^+(0)(1 + \Gamma_L)$$

Next, use

$$V(z) = V^+(0)e^{-j\beta_s z} (1 + \Gamma_L e^{+j2\beta_s z})$$


$$\Rightarrow V_1(0) = V(-L) = V^+(0)e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})$$

$$\Rightarrow V^+(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})}$$

Hence, we have

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Example (cont.)

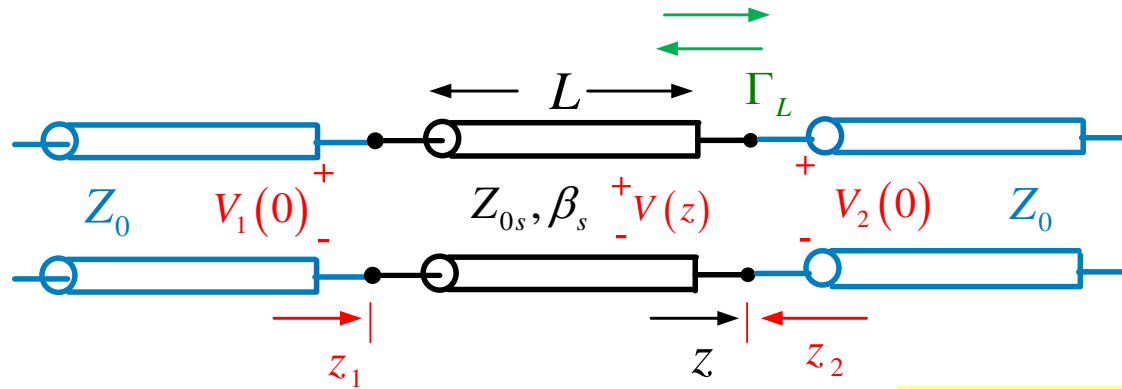

$$V_2^-(0) = \frac{V_1(0)}{e^{+j\beta_s L} (1 + \Gamma_L e^{-j2\beta_s L})} (1 + \Gamma_L)$$

Therefore, we have

$$V_1^+(0) = \frac{V_1(0)}{1 + S_{11}}$$


$$S_{21} = \left. \frac{V_2^-(0)}{V_1^+(0)} \right|_{a_2=0} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}}$$

so

$$S_{21} = \frac{(1 + S_{11})(1 + \Gamma_L) e^{-j\beta_s L}}{1 + \Gamma_L e^{-j2\beta_s L}} = S_{12} \text{ by symmetry}$$

Example (cont.)

Special cases:

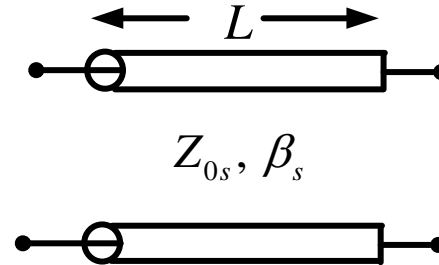

$$a) \quad Z_{0s} = Z_0 \Rightarrow S_{11} = S_{22} = 0, \quad \Gamma_L = 0$$

$$S_{21} = S_{12} = e^{-j\beta_s L}$$

$$[S] = \begin{bmatrix} 0 & e^{-j\beta_s L} \\ e^{-j\beta_s L} & 0 \end{bmatrix}$$

$$b) \quad L = \frac{\lambda_g}{2} \Rightarrow \beta_s L = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{2} = \pi$$

$$\Rightarrow Z_{in}|_{a_2=0} = Z_0 \Rightarrow S_{11} = S_{22} = 0$$


$$e^{-j\beta_s L} = -1 \Rightarrow S_{21} = -1$$

$$[S] = \begin{bmatrix} 0 & -1 \\ -1 & 0 \end{bmatrix}$$

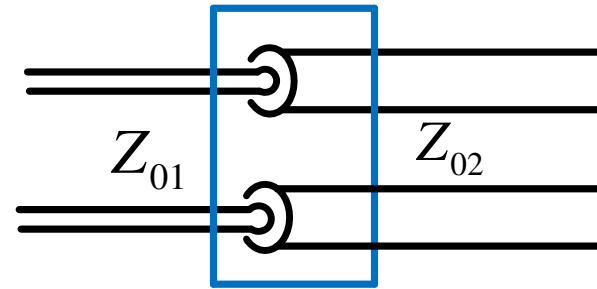Example

Find the S parameters for a step-impedance discontinuity.

$$S_{11} = \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}}$$
$$S_{22} = \frac{Z_{01} - Z_{02}}{Z_{02} + Z_{01}} = -S_{11}$$




$$S_{21} = \left. \frac{b_2(0)}{a_1(0)} \right|_{a_2=0} = \left. \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}} \right|_{a_2=0}$$

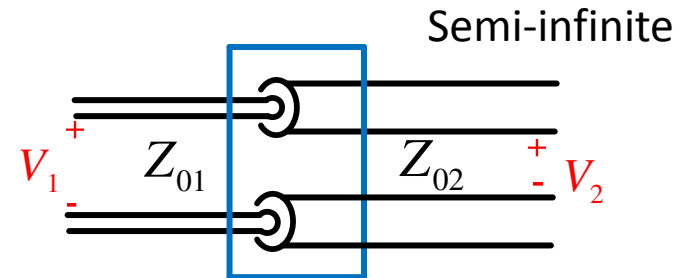Example (cont.)

S_{21} Calculation:

Because of continuity of the voltage across the junction, we have:



$$V_2^-(0)\Big|_{a_2=0} = V_2(0)\Big|_{a_2=0} = V_1(0)\Big|_{a_2=0} = V_1^+(0)(1 + S_{11})$$

$$S_{21} = \frac{\frac{V_2^-(0)}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}}\Bigg|_{a_2=0} = \frac{\frac{V_1^+(0)(1 + S_{11})}{\sqrt{Z_{02}}}}{\frac{V_1^+(0)}{\sqrt{Z_{01}}}}\Bigg|_{a_2=0}$$

$$1 + S_{11} = 1 + \frac{Z_{02} - Z_{01}}{Z_{02} + Z_{01}} = \frac{2Z_{02}}{Z_{02} + Z_{01}}$$

so

$$S_{21} = (1 + S_{11})\sqrt{\frac{Z_{01}}{Z_{02}}}$$

Hence

$$S_{21} = S_{12} = 2\frac{\sqrt{Z_{01}Z_{02}}}{Z_{01} + Z_{02}}$$

Properties of the S Matrix

❖ For **reciprocal** networks, the S -matrix is symmetric.

$$\Rightarrow [S] = [S]^T$$

Note :

$$\text{If } [A][B] = [U]$$

then

$$[B][A] = [U]$$

❖ For **lossless** networks, the S -matrix is unitary.

$$\Rightarrow [S]^T [S]^* = [S]^* [S]^T = [U]$$

Identity matrix

Equivalently,

$$[S]^{T*} = [S]^{-1}$$

$$\text{Notation: } [S]^\dagger = [S]^H = [S]^{T*}$$

$$\text{so } [S]^\dagger = [S]^{-1}$$

N -port network

$$\text{Take } (i, j) \text{ element } \Rightarrow \sum_{k=1}^N S_{ik}^T S_{kj}^* = \sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij} \quad \delta_{ij} = \begin{cases} 1; i = j \\ 0; i \neq j \end{cases}$$

Properties of the S Matrix (cont.)

Example:

$$[S] = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

$$\text{Unitary} \Rightarrow S_{11}S_{11}^* + S_{21}S_{21}^* + S_{31}S_{31}^* = 1$$

$$S_{12}S_{12}^* + S_{22}S_{22}^* + S_{32}S_{32}^* = 1$$

$$S_{13}S_{13}^* + S_{23}S_{23}^* + S_{33}S_{33}^* = 1$$

$$S_{11}S_{12}^* + S_{21}S_{22}^* + S_{31}S_{32}^* = 0$$

$$S_{11}S_{13}^* + S_{21}S_{23}^* + S_{31}S_{33}^* = 0$$


$$S_{12}S_{13}^* + S_{22}S_{23}^* + S_{32}S_{33}^* = 0$$

The column vectors form an orthogonal set.

The rows also form orthogonal sets (see the note on the previous slide).

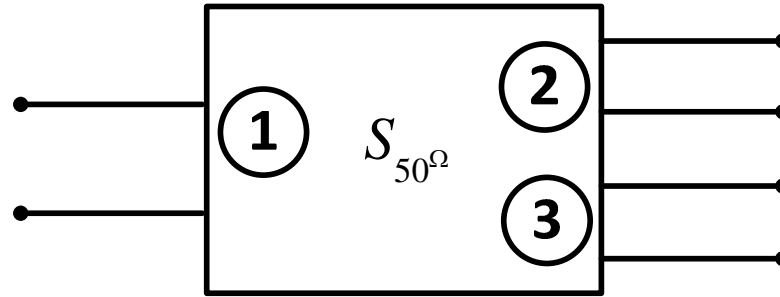Example

$$\left[S_{50\Omega} \right] = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$



Not unitary → **Not lossless**

(For example, column 2 dotted with the conjugate of column three is not zero.)


- 1) Find the input impedance looking into port 1 when ports 2 and 3 are terminated in 50 $[\Omega]$ loads.
- 2) Find the input impedance looking into port 1 when port 2 is terminated in a 75 $[\Omega]$ load and port 3 is terminated in a 50 $[\Omega]$ load.

Example (cont.)

1 If ports 2 and 3 are terminated in 50 [Ω]: ($a_2 = a_3 = 0$)

$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3$$

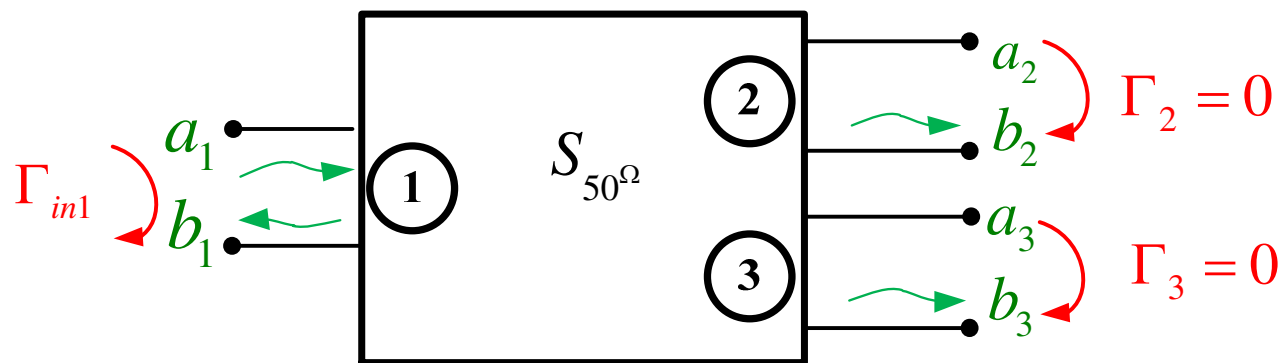
$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = S_{11} = 0 \quad \Rightarrow \quad Z_{in1} = 50[\Omega]$$



Example (cont.)

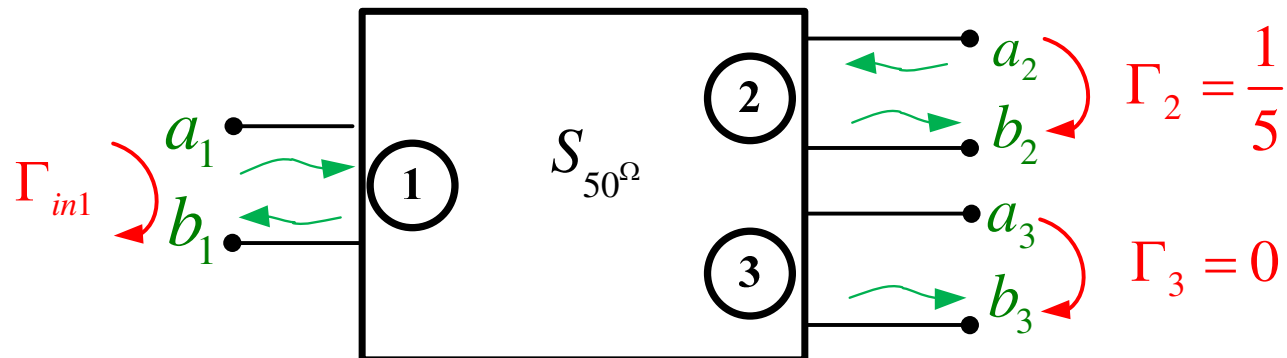
2) If port 2 is terminated in 75 [Ω] and port 3 in 50 [Ω]:

$$\Rightarrow \Gamma_2 = \frac{a_2}{b_2} = \frac{75-50}{75+50} = \frac{1}{5}$$



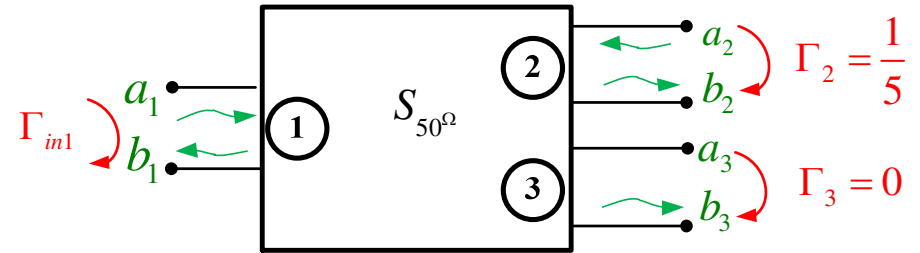Example (cont.)

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix} = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix}$$



$$\Rightarrow \Gamma_{in1} = \frac{b_1}{a_1} = \cancel{S_{11}} + S_{12} \frac{a_2}{a_1} + S_{13} \cancel{\frac{a_3}{a_1}}$$

$$b_2 / a_1 = S_{21} + \cancel{S_{22} \left(\frac{a_2}{a_1} \right)} + \cancel{S_{23} \left(\frac{a_3}{a_1} \right)}$$


$$= S_{12} \left(\Gamma_2 \frac{b_2}{a_1} \right) = S_{12} (\Gamma_2 S_{21}) = \left(\frac{-j}{\sqrt{2}} \right) \left(\frac{1}{5} \right) \left(\frac{-j}{\sqrt{2}} \right) = -\frac{1}{10}$$

$$a_2 = \Gamma_2 b_2$$

$$\Rightarrow Z_{in1} = 50 \left(\frac{1 + \Gamma_{in1}}{1 - \Gamma_{in1}} \right) = 44.55 [\Omega]$$

Transfer (T) Matrix

For cascaded 2-port networks:

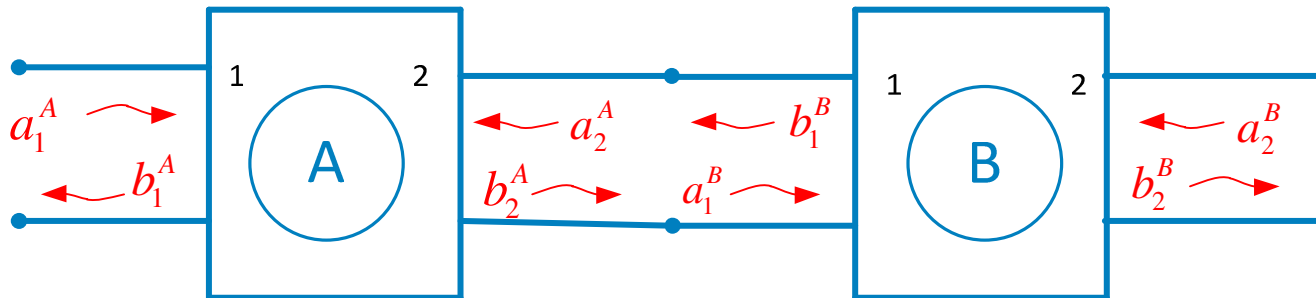

T Matrix:

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$

$$= [T] \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$

$$[T] = \begin{bmatrix} \frac{1}{S_{21}} & \frac{-S_{22}}{S_{21}} \\ \frac{S_{11}}{S_{21}} & S_{12} - \frac{S_{11}S_{22}}{S_{21}} \end{bmatrix}$$

$$[S] = \begin{bmatrix} \frac{-T_{21}}{T_{22}} & \frac{1}{T_{22}} \\ T_{11} - \frac{T_{12}^2}{T_{22}} & \frac{T_{12}}{T_{22}} \end{bmatrix}$$

(Derivation omitted)

Transfer (T) Matrix (cont.)

$$\Rightarrow \begin{bmatrix} a_1^A \\ b_1^A \end{bmatrix} = [T^A] \begin{bmatrix} b_2^A \\ a_2^A \end{bmatrix}$$

$$\text{But } \begin{bmatrix} b_2^A \\ a_2^A \end{bmatrix} = \begin{bmatrix} a_1^B \\ b_1^B \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} a_1^A \\ b_1^A \end{bmatrix} = [T^A] \begin{bmatrix} a_1^B \\ b_1^B \end{bmatrix}$$

$$\text{Hence } \begin{bmatrix} a_1^A \\ b_1^A \end{bmatrix} = \underbrace{[T^A][T^B]}_{[T^{AB}]} \begin{bmatrix} b_2^B \\ a_2^B \end{bmatrix}$$

The T matrix of a cascaded set of networks is the product of the T matrices.

Conversion Between Parameters

TABLE 4.2 Conversions Between Two-Port Network Parameters

	<i>S</i>	<i>Z</i>	<i>Y</i>	<i>ABCD</i>
<i>S</i> ₁₁	<i>S</i> ₁₁	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> ₁₂	<i>S</i> ₁₂	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> ₂₁	<i>S</i> ₂₁	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
<i>S</i> ₂₂	<i>S</i> ₂₂	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
<i>Z</i> ₁₁	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> ₁₁	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
<i>Z</i> ₁₂	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> ₁₂	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
<i>Z</i> ₂₁	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> ₂₁	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
<i>Z</i> ₂₂	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> ₂₂	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
<i>Y</i> ₁₁	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	<i>Y</i> ₁₁	$\frac{D}{B}$
<i>Y</i> ₁₂	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	<i>Y</i> ₁₂	$\frac{BC - AD}{B}$
<i>Y</i> ₂₁	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	<i>Y</i> ₂₁	$\frac{-1}{B}$
<i>Y</i> ₂₂	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	<i>Y</i> ₂₂	$\frac{A}{B}$
<i>A</i>	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{11}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	<i>A</i>
<i>B</i>	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	<i>B</i>
<i>C</i>	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	<i>C</i>
<i>D</i>	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	<i>D</i>

$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21};$$

$$|Y| = Y_{11}Y_{22} - Y_{12}Y_{21};$$

$$\Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21};$$

$$\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21};$$


$$Y_0 = 1/Z_0$$

Example

Derive S_{ij} from the Z parameters.


(The result is given inside row 1, column 2, of the previous table.)

S_{11} Calculation:

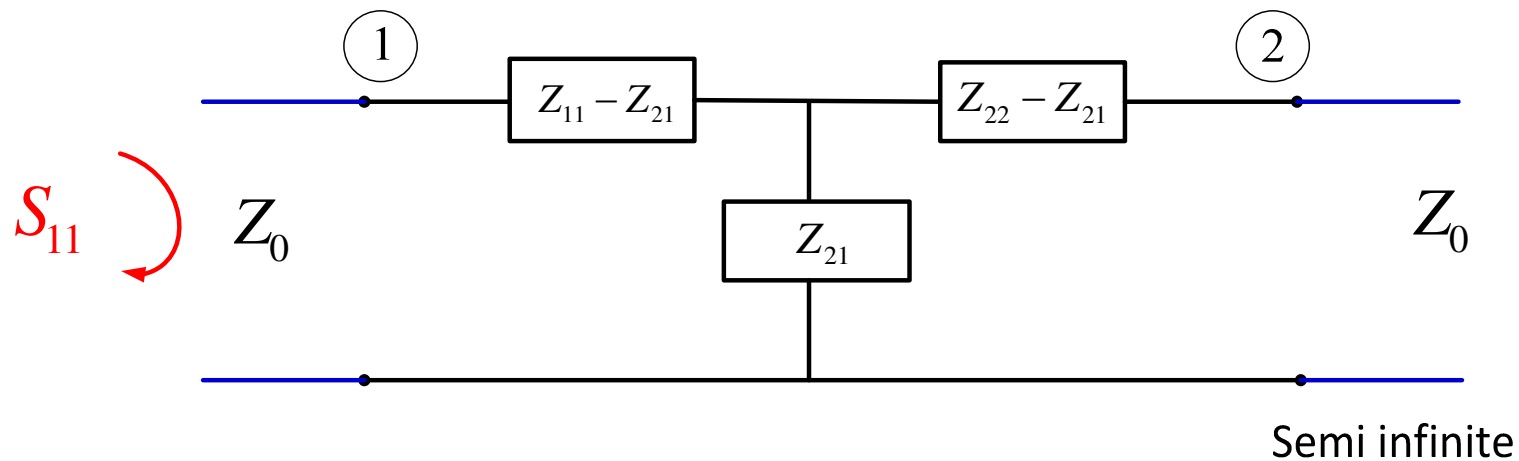


$$S_{11} = \Gamma_{in1} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \quad Z_{in} = (Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]$$

Example (cont.)

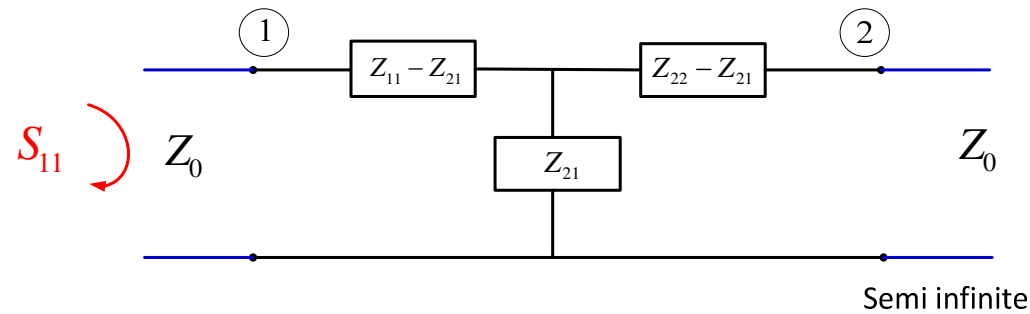

$$\begin{aligned}
 Z_{in} &= (Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0] \\
 &= (Z_{11} - Z_{21}) + \frac{Z_{21}(Z_{22} + Z_0 - Z_{21})}{Z_{22} + Z_0} \\
 &= \frac{(Z_{11} - Z_{21})(Z_{22} + Z_0) + Z_{21}(Z_{22} + Z_0 - Z_{21})}{Z_{22} + Z_0} \\
 &= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - Z_{21}Z_{22} - Z_{21}Z_0 + Z_{21}Z_{22} + Z_{21}Z_0 - Z_{21}^2}{Z_{22} + Z_0} \\
 &= \frac{Z_{11}Z_{22} + Z_{11}Z_0 - Z_{21}^2}{Z_{22} + Z_0}
 \end{aligned}$$

Example (cont.)

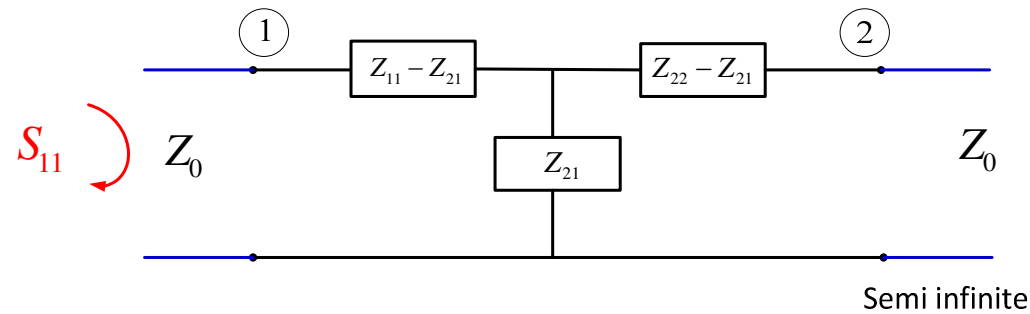


$$Z_{in} = \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2}{Z_{22} + Z_0}$$

$$S_{11} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

so


$$S_{11} = \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 - Z_0(Z_0 + Z_{22})}{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 + Z_0(Z_0 + Z_{22})}$$

Example (cont.)

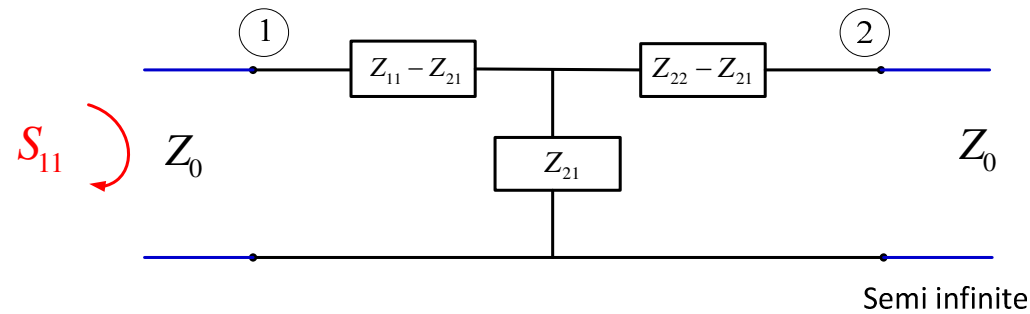

$$\begin{aligned}
 S_{11} &= \frac{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 - Z_0(Z_0 + Z_{22})}{Z_{11}(Z_0 + Z_{22}) - Z_{21}^2 + Z_0(Z_0 + Z_{22})} \\
 &= \frac{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 - Z_0^2 - Z_0Z_{22}}{Z_{11}Z_0 + Z_{11}Z_{22} - Z_{21}^2 + Z_0^2 + Z_0Z_{22}} \\
 &= \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}
 \end{aligned}$$

Example (cont.)

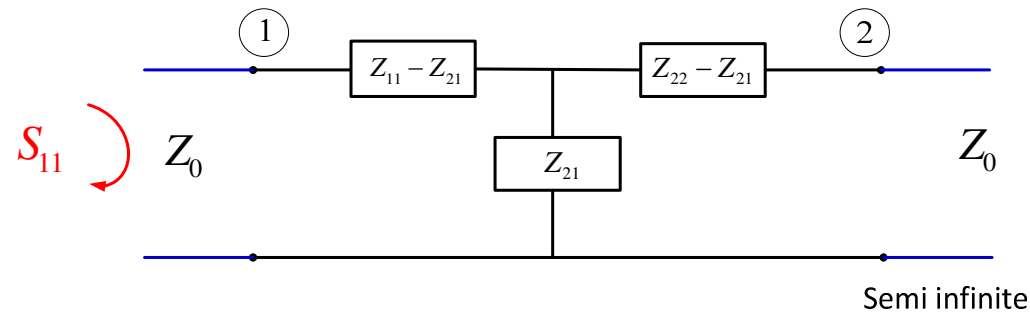


$$S_{11} = \frac{(Z_0 + Z_{22})(Z_{11} - Z_0) - Z_{21}^2}{(Z_0 + Z_{22})(Z_{11} + Z_0) - Z_{21}^2}$$

Note: to get S_{22} , simply let $Z_{11} \rightarrow Z_{22}$ in the previous result.

$$S_{22} = \frac{(Z_0 + Z_{11})(Z_{22} - Z_0) - Z_{21}^2}{(Z_0 + Z_{11})(Z_{22} + Z_0) - Z_{21}^2}$$

Example (cont.)

S_{21} Calculation:

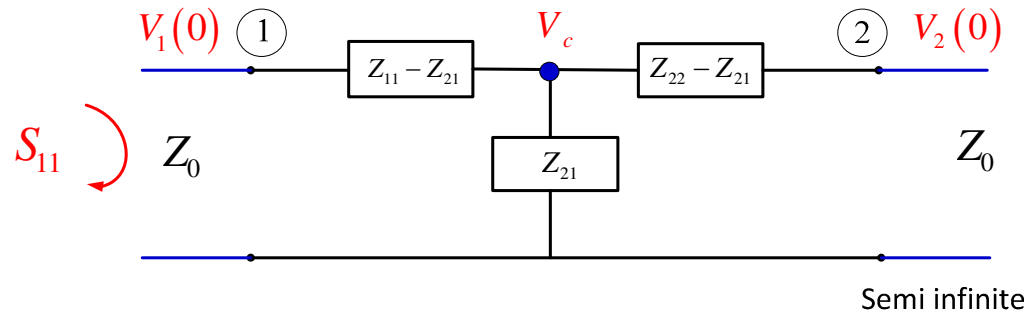

Assume $V_1^+(0) = 1 \text{ [V]}$


$$V_1(0) = 1 + S_{11} \quad S_{21} = V_2^-(0) = V_2(0)$$

Use voltage divider equation twice:

$$V_c = V_1(0) \left(\frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right)$$

$$V_2(0) = V_c \left(\frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

Example (cont.)

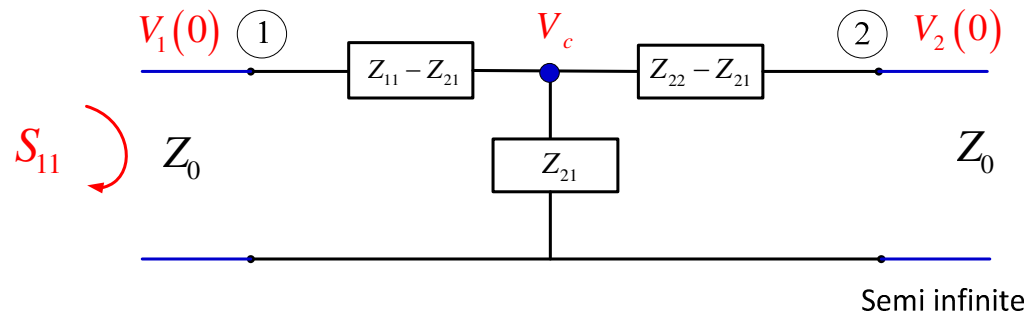

Hence

$$S_{21} = (1 + S_{11}) \left(\frac{(Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]}{(Z_{11} - Z_{21}) + (Z_{21}) \parallel [(Z_{22} - Z_{21}) + Z_0]} \right) \left(\frac{Z_0}{(Z_{22} - Z_{21}) + Z_0} \right)$$

After simplifying, we should get the result in the table.

(You are welcome to check it!)