

LE 325 Assignment #5

1. It is found that the attenuation on a $50\text{-}\Omega$ *distortionless* transmission line is 0.01 (dB/m) . The line has a capacitance of 0.1 (pF/m) .

- Find the resistance, inductance, and conductance per meter of the line.
- Find the velocity of wave propagation.
- Determine the percentage to which the amplitude of a voltage traveling wave decreases in 1 km and in 5 km .

2. Given a coaxial cable with (inner,outer) radii of $(16,60)$ mils ($1000\text{ mils} = 1\text{ inch}$) and filled with polyethylene ($\epsilon_r = 2.26$) (this is the RG-58/U cable). Assume that the wire conductors are *perfect*. Determine the characteristic impedance, attenuation constant and phase constant at 10 MHz if the loss tangent of polyethylene at 10 MHz is approximately 10^{-3} . Compare with the values computed if polyethylene is considered *lossless*.

3. A lossless transmission line is 80 cm long and operates at a frequency of 600 MHz . The line parameters are $L = 0.25\text{ }\mu\text{H/m}$ and $C = 100\text{ pF/m}$. The voltage source $V_g = 10\text{ V}$ and the generator impedance $Z_g = 50\text{ }\Omega$. Find

- the characteristic impedance
- the phase constant
- the velocity on the line
- the input impedance for $Z_L = 100\text{ }\Omega$
- the current at the load
- the power delivered to the load

4. A lossless transmission line is 100 m long and operates at a frequency of 100 MHz . The line parameters are $L = 5\text{ }\mu\text{H/m}$ and $C = 2\text{ nF/m}$. The voltage source $V_g = 30\text{ V}$ with the generator impedance $Z_g = 50\text{ }\Omega$ is connected to a $100\text{-}\Omega$ load via this transmission line. Find

- the input impedance
- the current at the load
- the power delivered to the line
- the power delivered to the load