

1. Since the impedance function is given by

$$Z(\omega) = -\frac{j}{\omega C_2} \frac{\omega^2 - 1/L_1 C_1}{\omega^2 - \frac{C_1 + C_2}{L_1 C_1 C_2}} \text{ or } Z(s) = \frac{1}{s C_2} \frac{s^2 + 1/L_1 C_1}{s^2 + \frac{C_1 + C_2}{L_1 C_1 C_2}}$$

To construct the series resonant circuit, first notice that there are two poles, namely, at $s = 0$ and $s = j(C_1 + C_2)/L_1 C_1 C_2$ and thus the circuit consists of a series capacitor and a parallel LC resonator. Let C_0 denote the series capacitor, and C_p, L_p denote the capacitor and inductor of the parallel LC resonator, respectively, then

$$C_0 = \frac{1}{k_0} = \frac{1}{sZ(s)} \Big|_{s=0} = \left[\frac{1}{C_2} \frac{s^2 + 1/L_1 C_1}{s^2 + \frac{C_1 + C_2}{L_1 C_1 C_2}} \right]^{-1} \Big|_{s=0} = C_1 + C_2$$

$$C_p = \frac{1}{2k_i} = \frac{s}{(s^2 + \omega_i^2)Z(s)} \Big|_{s=j\omega_i} = \left[\frac{s^2 C_2}{s^2 + 1/L_1 C_1} \right] \Big|_{s=j\omega_2} = -\frac{C_1 + C_2}{L_1 C_1} \left[-\frac{C_1 + C_2}{L_1 C_1 C_2} + \frac{1}{L_1 C_1} \right]^{-1} = \frac{(C_1 + C_2)C_2}{C_1}$$

$$L_p = \frac{1}{\omega_2^2 C_p} = \left[\frac{C_1 + C_2}{L_1 C_1 C_2} \frac{(C_1 + C_2)C_2}{C_1} \right]^{-1} = \frac{L_1 C_1^2}{(C_1 + C_2)^2}$$

2. Since the admittance function is given by

$$Y(\omega) = -\frac{j}{\omega L_2} \frac{\omega^2 - 1/L_1 C_1}{\omega^2 - \frac{L_1 + L_2}{C_1 L_1 L_2}} \text{ or } Y(s) = \frac{1}{s L_2} \frac{s^2 + 1/L_1 C_1}{s^2 + \frac{L_1 + L_2}{C_1 L_1 L_2}}$$

This has poles at $s = 0$ and $s = j(L_1 + L_2)/L_1 L_2 C_1$ and thus the circuit consists of a parallel inductor and a series LC resonator. Let L_0 denote the parallel inductor, and C_s, L_s denote the capacitor and inductor of the series LC resonator, respectively, then

$$L_0 = \frac{1}{h_0} = \frac{1}{sY(s)} \Big|_{s=0} = \left[\frac{1}{L_2} \frac{s^2 + 1/L_1 C_1}{s^2 + \frac{L_1 + L_2}{C_1 L_1 L_2}} \right]^{-1} \Big|_{s=0} = L_1 + L_2$$

$$L_s = \frac{1}{2h_i} = \frac{s}{(s^2 + \omega_i^2)Y(s)} \Big|_{s=j\omega_i} = \left[\frac{s^2 L_2}{s^2 + 1/L_1 C_1} \right] \Big|_{s=j\omega_2} = -\frac{L_1 + L_2}{L_1 C_1} \left[-\frac{L_1 + L_2}{L_1 L_2 C_1} + \frac{1}{L_1 C_1} \right]^{-1} = \frac{(L_1 + L_2)L_2}{L_1}$$

$$C_s = \frac{1}{\omega_2^2 L_s} = \left[\frac{L_1 + L_2}{L_1 L_2 C_1} \frac{(L_1 + L_2)L_2}{L_1} \right]^{-1} = \frac{C_1 L_1^2}{(L_1 + L_2)^2}$$

3. Let V_3 be the voltage at the node between Z_1 and Z_2 , then use KCL,

$$\frac{V_1 - V_3}{Z_1} = \frac{V_3}{Z_2'} + \frac{V_3 - V_2}{Z_2} \rightarrow -\frac{V_2}{Z_2} + \left(\frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \right) V_3 = \frac{V_1}{Z_1}$$

$$\frac{V_2 - V_3}{Z_2} = \frac{V_1 - V_2}{Z_1'} \rightarrow \left(\frac{1}{Z_1'} + \frac{1}{Z_2} \right) V_2 - \frac{V_3}{Z_2} = \frac{V_1}{Z_1'}. \text{ Thus,}$$

$$\begin{bmatrix} -\frac{1}{Z_2} & \frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \\ \frac{1}{Z_1'} + \frac{1}{Z_2} & -\frac{1}{Z_2} \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = V_1 \begin{bmatrix} \frac{1}{Z_1} \\ \frac{1}{Z_1'} \end{bmatrix}$$

Using Cramer's rule yields

$$V_2 = V_1 \frac{\begin{vmatrix} \frac{1}{Z_1} & \frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \\ \frac{1}{Z_1'} & -\frac{1}{Z_2} \end{vmatrix}}{\begin{vmatrix} -\frac{1}{Z_2} & \frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \\ \frac{1}{Z_1'} + \frac{1}{Z_2} & -\frac{1}{Z_2} \end{vmatrix}} = V_1 \frac{-\frac{1}{Z_1 Z_2} - \left(\frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \right) \frac{1}{Z_1'}}{\frac{1}{Z_2^2} - \left(\frac{1}{Z_1} + \frac{1}{Z_2'} + \frac{1}{Z_2} \right) \left(\frac{1}{Z_1'} + \frac{1}{Z_2} \right)} = V_1 \frac{Z_1 Z_2 + Z_2' (Z_1 + Z_1' + Z_2)}{Z_1 Z_2' + (Z_1 + Z_2') (Z_1' + Z_2)}$$

With port 2 short-circuited,

$$Z_{in} = Z_1' // [Z_1 + (Z_2 // Z_2')] = Z_1' // \left[Z_1 + \frac{Z_2 Z_2'}{Z_2 + Z_2'} \right] = \frac{Z_1' \left(Z_1 + \frac{Z_2 Z_2'}{Z_2 + Z_2'} \right)}{Z_1' + Z_1 + \frac{Z_2 Z_2'}{Z_2 + Z_2'}} = \frac{Z_1 Z_1' (Z_2 + Z_2') + Z_1' Z_2 Z_2'}{(Z_1' + Z_1) (Z_2 + Z_2') + Z_2 Z_2'}$$