

2. Coaxial cable.

$$C = \frac{2\pi\epsilon}{\ln(b/a)} = 95 \text{ pF/m}; L = \frac{\mu\epsilon}{C} = 264.3 \text{ nH/m}$$

The loss tangent is 10^{-3} at 10 MHz, thus

$$\frac{\sigma}{\omega\epsilon} = 10^{-3} \rightarrow \sigma = 1.2556 \mu\text{S/m}. \text{ It follows that}$$

$$G = \frac{\sigma}{\epsilon} C = 5.97 \mu\text{S/m}$$

Then, $Z_0 = 52.75 + j0.026 \Omega$, $\gamma = .002 + j0.3148$

If it is lossless ($G=0$), $Z_0 = 52.75 \Omega$, $\gamma = j0.3148$

$$3. Z_0 = \sqrt{\frac{L}{C}} = 50; \beta = \omega\sqrt{LC} = 6\pi; u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = 200 \text{ m}/\mu\text{s}$$

$$Z_{in} = 49.1045 + j35.0258, V_i = 7.2424 + j1.3034 \text{ V}, I_i = 0.1103 - j0.0521, P_{av, line} = 0.3655 \text{ W}$$

$$V_0^+ = 6.3788 - j0.6517, V_0^- = 0.8636 + j1.9551, V_L = -7.3915 - j4.2962, I_L = -0.0739 - j0.0430$$

$$P_{av, load} = 0.3655 \text{ W}$$

$$4. Z_0 = \sqrt{\frac{L}{C}} = 50; \beta = \omega\sqrt{LC} = 20\pi$$

$$Z_{in} = 100, V_i = 20 \text{ V}, I_i = 0.2, P_{av, line} = 2 \text{ W}$$

$$V_0^+ = 15, V_0^- = 5, V_L = 20, I_L = 0.2, P_{av, load} = 2 \text{ W}$$