

Two-Port Symmetry

The open-circuit and short-circuit impedances of a two-port are defined as

$$Z_{1o} = \left. \frac{V_1}{I_1} \right|_{I_2=0}; Z_{2o} = \left. \frac{V_2}{I_2} \right|_{I_1=0}; Z_{1s} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; Z_{2s} = \left. \frac{V_2}{I_2} \right|_{V_1=0}.$$

The subscripts o and s denote the open-circuit and short-circuit, respectively, which specifies the condition at the other port. For example, Z_{1o} is an impedance measurement at port 1 with port 2 open-circuited.

Transmission Parameters in Terms of Open-circuit and Short-circuit Parameters

Given the transmission parameters A , B , C , and D , the following relationships hold:

$$V_1 = AV_2 - BI_2; I_1 = CV_2 - DI_2.$$

Therefore,

$$Z_{1o} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{A}{C}; Z_{2o} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{D}{C}; Z_{1s} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{B}{D}; Z_{2s} = \left. \frac{V_2}{I_2} \right|_{V_1=0} = \frac{B}{A}.$$

Assume that the network is reciprocal (i.e., $AD - BC = 1$), then one can obtain

$$A = \pm \sqrt{\frac{Z_{1o}}{Z_{2o} - Z_{2s}}}; B = \pm Z_{2o} \sqrt{\frac{Z_{1o}}{Z_{2o} - Z_{2s}}}; C = \pm \sqrt{\frac{1}{Z_{1o}(Z_{2o} - Z_{2s})}}; D = \pm \frac{Z_{2o}}{\sqrt{Z_{1o}(Z_{2o} - Z_{2s})}}.$$

Input Impedance in Terms of Two-Port Parameters

Here, assume that the output port (port 2) is terminated by a load impedance, Z_L , then the input impedance is given by the ratio V_1/I_1 , which can be determined in terms of two-port parameters and Z_L .

(i) In terms of Z -parameters

Recall that

$$V_1 = Z_{11}I_1 + Z_{12}I_2; V_2 = Z_{21}I_1 + Z_{22}I_2 \text{ and } V_2 = -Z_L I_2.$$

Hence, $-Z_L I_2 = Z_{21}I_1 + Z_{22}I_2$ or $Z_{21}I_1 = -(Z_L + Z_{22})I_2$. It follows that

$$I_2 = \frac{-Z_{21}I_1}{Z_L + Z_{22}} \text{ and } V_1 = Z_{11}I_1 + Z_{12}I_2 = Z_{11}I_1 - \frac{Z_{12}Z_{21}I_1}{Z_L + Z_{22}} = \left(Z_{11} - \frac{Z_{12}Z_{21}}{Z_L + Z_{22}} \right) I_1.$$

Therefore,

$$Z_{in} = \frac{V_1}{I_1} = Z_{11} - \frac{Z_{12}Z_{21}}{Z_L + Z_{22}} = \frac{Z_{11}Z_L - Z_{12}Z_{21} + Z_{11}Z_{22}}{Z_L + Z_{22}}.$$

If the output port is open-circuited, then

$$Z_{in,oc} = \left. \frac{V_1}{I_1} \right|_{Z_L=\infty} = \left. \frac{Z_{11}Z_L - Z_{12}Z_{21} + Z_{11}Z_{22}}{Z_L + Z_{22}} \right|_{Z_L=\infty} = Z_{11}.$$

Likewise, if the output port is short-circuited, then

$$Z_{in,sc} = \left. \frac{V_1}{I_1} \right|_{Z_L=0} = \left. \frac{Z_{11}Z_L - Z_{12}Z_{21} + Z_{11}Z_{22}}{Z_L + Z_{22}} \right|_{Z_L=0} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}} = \frac{\Delta Z}{Z_{22}}.$$

(ii) In terms of $ABCD$ parameters

From $V_1 = AV_2 - BI_2$, $I_1 = CV_2 - DI_2$ and $V_2 = -Z_L I_2$,

$$I_1 = C(-Z_L I_2) - DI_2 = -(CZ_L + D)I_2.$$

It follows that

$$I_2 = \frac{-I_1}{CZ_L + D} \text{ and } V_1 = AV_2 - BI_2 = A(-Z_L I_2) - BI_2 = -(AZ_L + B)I_2 = \frac{AZ_L + B}{CZ_L + D} I_1.$$

Therefore,

$$Z_{in} = \frac{V_1}{I_1} = \frac{AZ_L + B}{CZ_L + D}.$$

$Z_{in,oc}$ and $Z_{in,sc}$ then become

$$Z_{in,oc} = \left. \frac{V_1}{I_1} \right|_{Z_L=\infty} = \frac{A}{C}; \quad Z_{in,sc} = \left. \frac{V_1}{I_1} \right|_{Z_L=0} = \frac{B}{D}.$$

Output Impedance in Terms of Two-Port Parameters

Here, assume that the input port (port 1) is terminated by a load impedance, Z_L , then the output impedance is given by the ratio V_2/I_2 , which can be determined in terms of two-port parameters and Z_L .

(i) In terms of Z -parameters

From $V_1 = Z_{11}I_1 + Z_{12}I_2$; $V_2 = Z_{21}I_1 + Z_{22}I_2$ and $V_1 = -Z_L I_1$, it can be shown that

$$Z_{out} = \frac{V_2}{I_2} = \frac{Z_{22}Z_L - Z_{12}Z_{21} + Z_{11}Z_{22}}{Z_L + Z_{11}}.$$

$Z_{out,oc}$ and $Z_{out,sc}$ then become

$$Z_{out,oc} = Z_{22}; \quad Z_{out,sc} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{11}} = \frac{\Delta Z}{Z_{11}}.$$

(ii) In terms of $ABCD$ parameters

From $V_1 = AV_2 - BI_2$, $I_1 = CV_2 - DI_2$ and $V_1 = -Z_L I_1$, it can be shown that

$$Z_{out} = \frac{V_2}{I_2} = \frac{DZ_L + B}{CZ_L + A}.$$

$Z_{out,oc}$ and $Z_{out,sc}$ then become

$$Z_{out,oc} = \frac{D}{C}; \quad Z_{out,sc} = \frac{B}{A}.$$